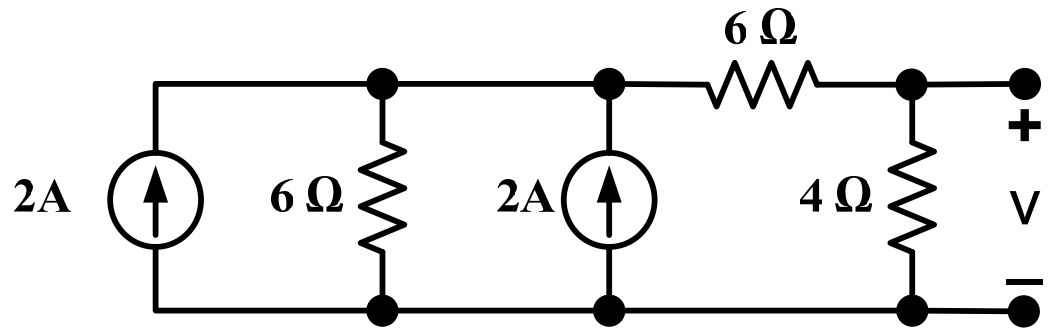



Question 1:

Use only source transformation to compute the voltage V in the circuit shown below.









Source Transformation - Masoud (4)

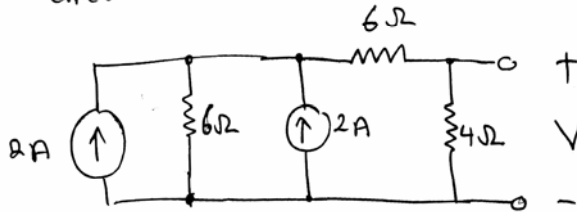- Use the source transformation method to compute the voltage V in the circuit shown below:



Solution:

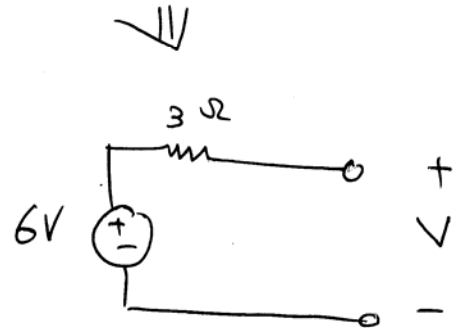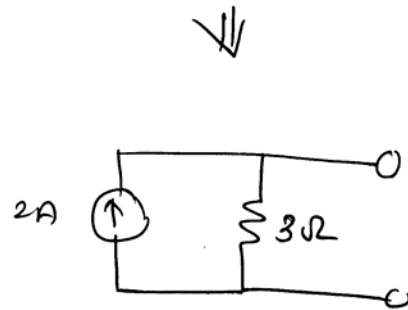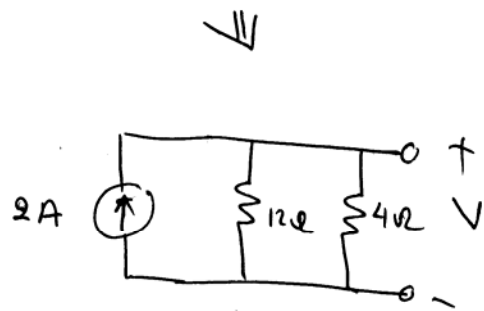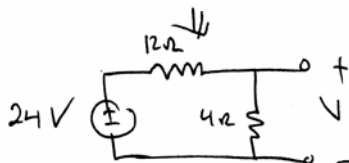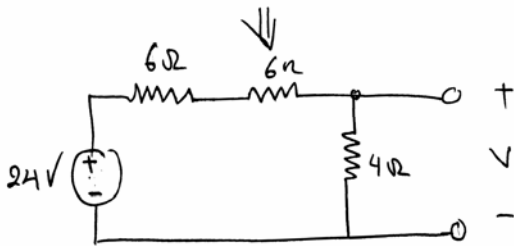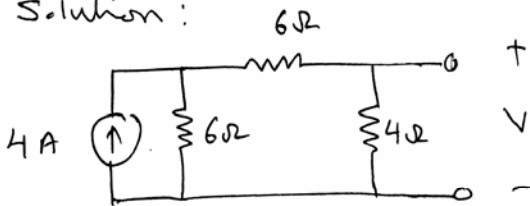


$\therefore V = 6 \text{ Volts.}$

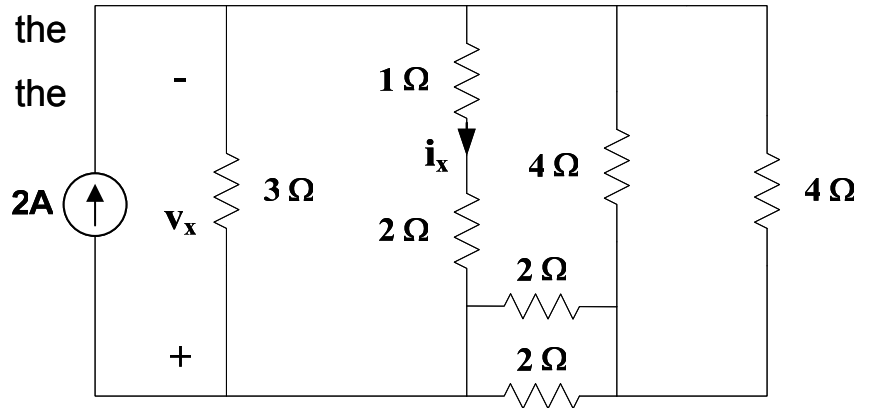Question 2:

Apply circuit reduction method for the circuit shown below to obtain the following:

- The voltage v_x .
- The current i_x .
- The power **supplied** by the independent current source.




Total 10 points

$$V_x = \frac{-2}{\frac{1}{3} + \frac{1}{3} + \frac{1}{3}} = -2V \quad (2)$$

$$i_x = \frac{-V_x}{3} = \frac{2}{3}A \quad (2)$$

$$P_{2A} = -2V_x = 4W \quad (2)$$


Circuit reduction

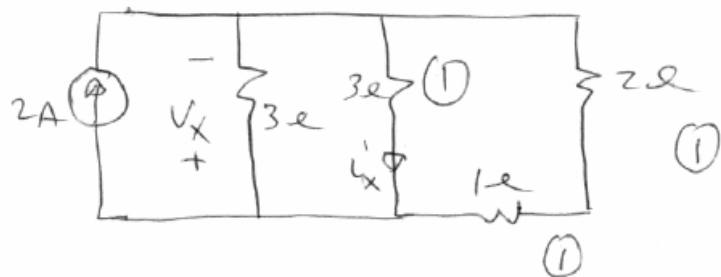

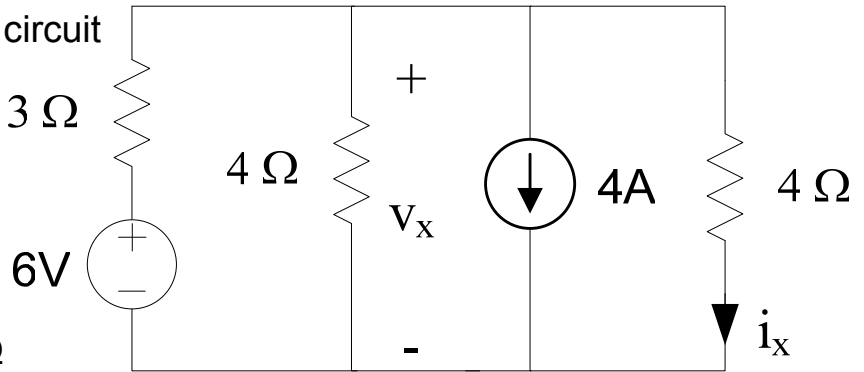Question 3:

Use the direct method for the circuit shown below to obtain the following:

- The voltage v_x .
- The current i_x .
- The power **absorbed by** the $3\ \Omega$ resistor.



Total 10 points

$$\text{KVL: } v_x = 4i_x \quad (1)$$


$$\Rightarrow i_x = \frac{v_x}{4} = \frac{4i_x}{4} = i_x \quad (1)$$

KVL for the outer loop

$$6 = 3(4 + 2i_x) + 4i_x \quad (2)$$

$$\Rightarrow i_x = \frac{-6}{10} = -\frac{3}{5} \text{ A} \quad (2)$$
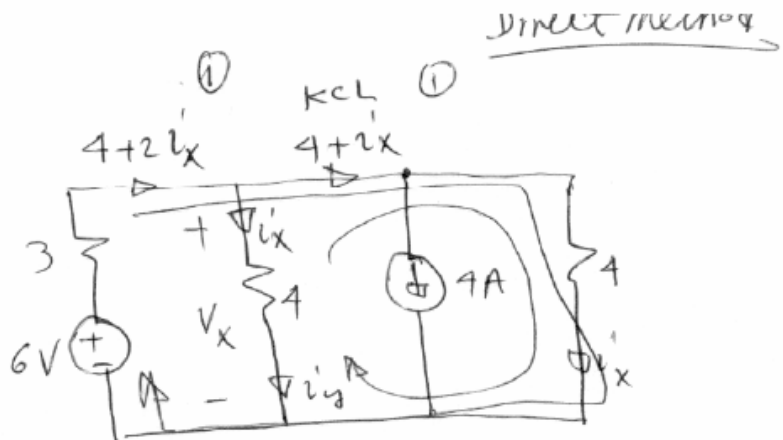
$$v_x = 4i_x = -\frac{12}{5} \text{ V} \quad (2)$$



The power absorbed by the $3\ \Omega$ resistor:
Find the voltage across the $3\ \Omega$ resistor which is:

$$V_{3\Omega} = 6 - v_x = 6 + \frac{12}{5} = \frac{42}{5}$$

$$P_{3\Omega} = \frac{V_{3\Omega}^2}{3} = \frac{588}{25} = 23.52 \text{ watt}$$

Or find the current passing through the $3\ \Omega$ resistor which is:

$$I_{3\Omega} = 4 + 2i_x = 4 - \frac{6}{5} = \frac{14}{5}$$

$$P_{3\Omega} = 3I_{3\Omega}^2 = 3 \times \frac{196}{25} = \frac{588}{25} = 23.52 \text{ watt}$$