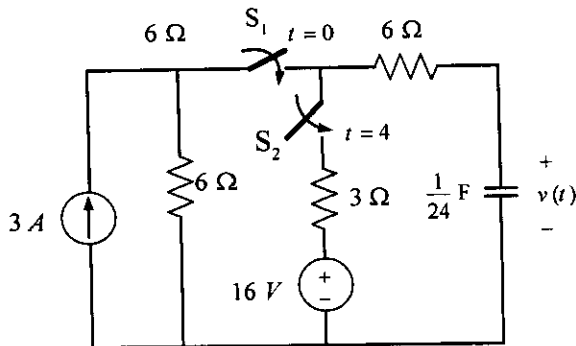


EE 201-02-Winter 2011(102)
QZ5


Ser	ID	Name	KEY
-----	----	------	-----



For the circuit shown above the capacitor initially is uncharged, switch S_1 close at $t=0$, then after 4 seconds switch S_2 close at $t=4$, find $v(t)$ for all time?

For $t \leq 0$ $\Rightarrow v(0^-) = 0 = v(0^+)$

For $0 \leq t \leq 4$

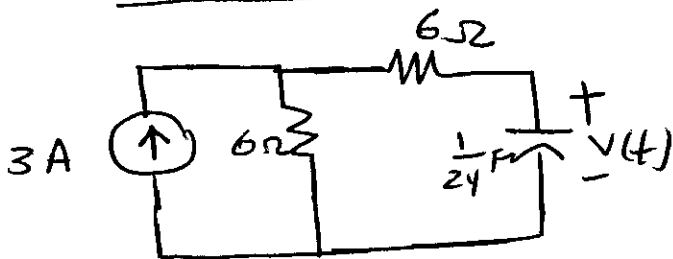


$$v(t) = v(\infty) + [v(0^+) - v(\infty)] e^{-t/\tau_1}$$

$$v(\infty) = (3)(6) = 18 \text{ V}$$

$$v(0^+) = v(0^-) = 0 \text{ V}$$

$$\tau_1 = R_{eq} C_{eq}$$

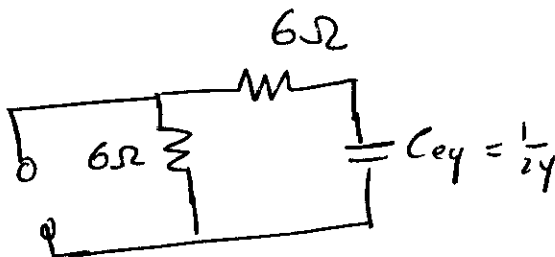

R_{eq} (seen by the capacitor)

$$= 6 + 6 = 12 \Omega$$

$$\tau_1 = 12 \frac{1}{24} = \frac{1}{2} \text{ s}$$




$$\Rightarrow v(t) = 18 + [0 - 18] e^{-2t} \text{ V}$$


$$= 18 [1 - e^{-2t}] \text{ V}$$

(Continue) \Rightarrow

For $t \geq 4$

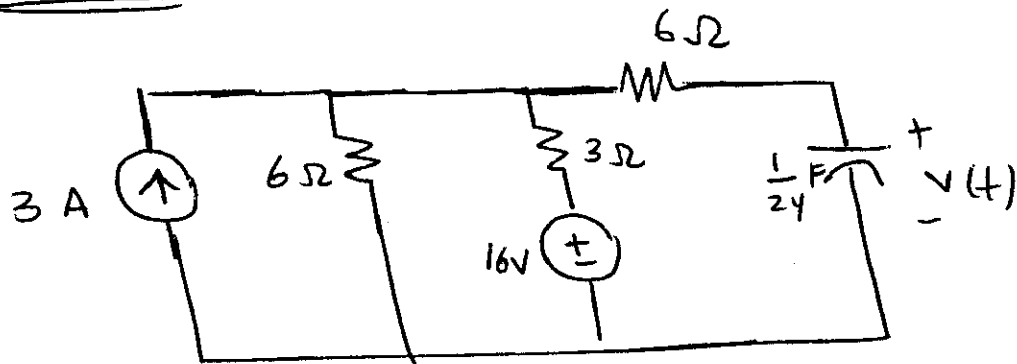
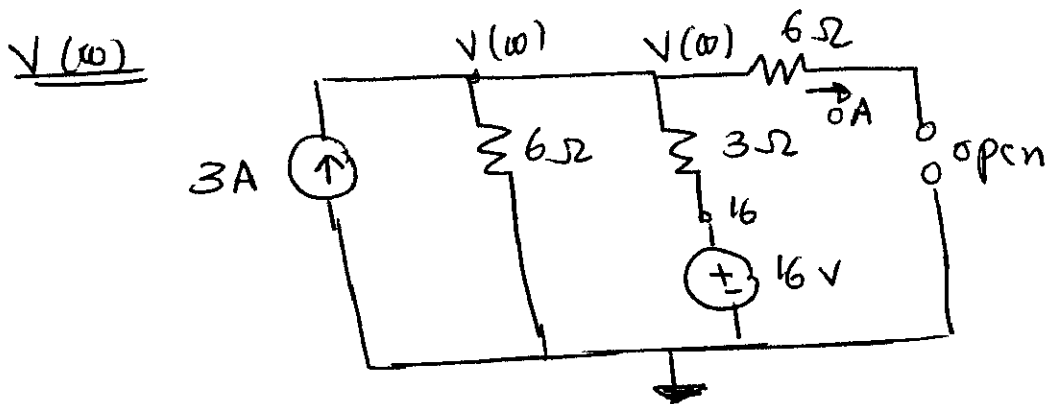
$$v(t) = v(\infty) + [v(4^+) - v(\infty)] e^{-\frac{(t-4)}{\tau_2}}$$



KCL $-3 + \frac{v(\infty)}{6} + \frac{v(\infty) - 16}{3} = 0$


solving $v(\infty) = \frac{50}{3} = 16.67 \text{ V}$

$$v(4^+) = v(4^-) = 18 \left[1 - \underbrace{e^{-2(4)}}_{\approx 0} \right] \approx 18$$

$\tau_2 = R_{eq2} C_{eq}$

$$R_{eq2} = 6 + (3 \parallel 16) = 8 \Omega$$
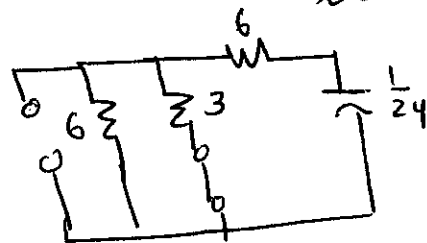
$$\tau_2 = 8 \cdot \frac{1}{24} = \frac{1}{3} \text{ s}$$




$$v(t) = 16.67 + [18 - 16.67] e^{-3(t-4)}$$

$$= 16.67 + 1.3 e^{-3(t-4)} \quad \checkmark$$

EE 201-01-Winter 2011(102)
QZ5


Ser	ID	Name	KEY
-----	----	------	-----

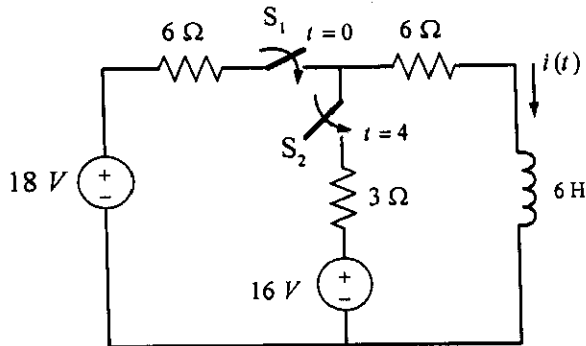

For the circuit shown above, switch S_1 close at $t=0$, then after 4 seconds switch S_2 close at $t=4$, find $i(t)$ for all time?

For $t \leq 0$ $i(t) = 0$ $i(0^-) = i(0^+) = 0$ A

For $0 \leq t \leq 4$

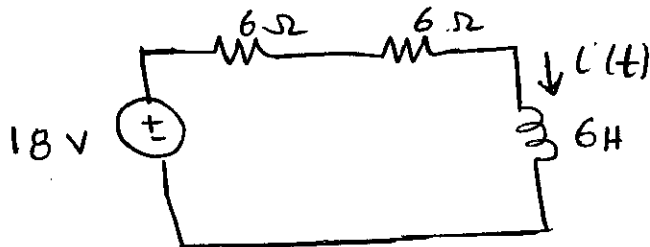

$$i(t) = i(\infty) + [i(0^+) - i(\infty)] e^{-t/\tau_1}$$

$$i(\infty) = \frac{18}{6+6} = \frac{3}{2} = 1.5 \text{ A}$$

$$i(0^+) = i(0^-) = 0 \text{ A}$$

$$\tau_1 = \frac{L_{eq}}{R_{eq}}$$

R_{eq} , (seen by the inductor)

$$= 6 + 6 = 12 \Omega$$


$$\tau_1 = \frac{6}{12} = \frac{1}{2} \text{ s}$$

$$\Rightarrow i(t) = 1.5 + [0 - 1.5] e^{-2t} \text{ A}$$


$$= 1.5 [1 - e^{-2t}] \text{ A}$$

(continue)

For $t \geq 4$

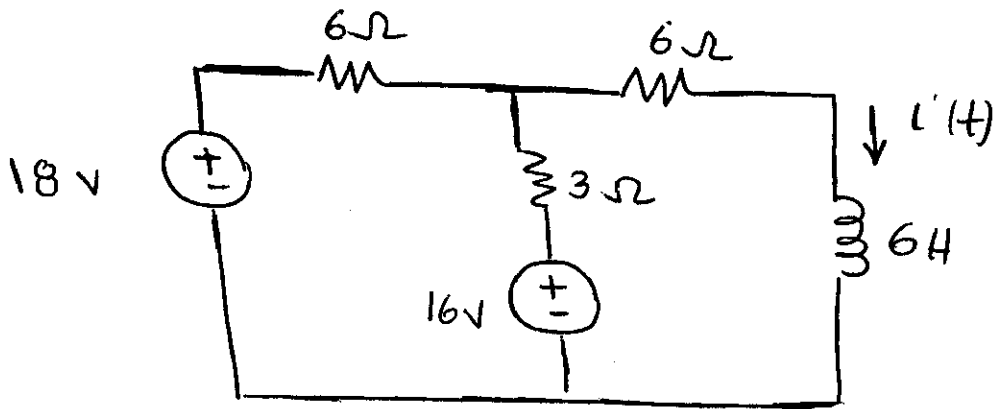
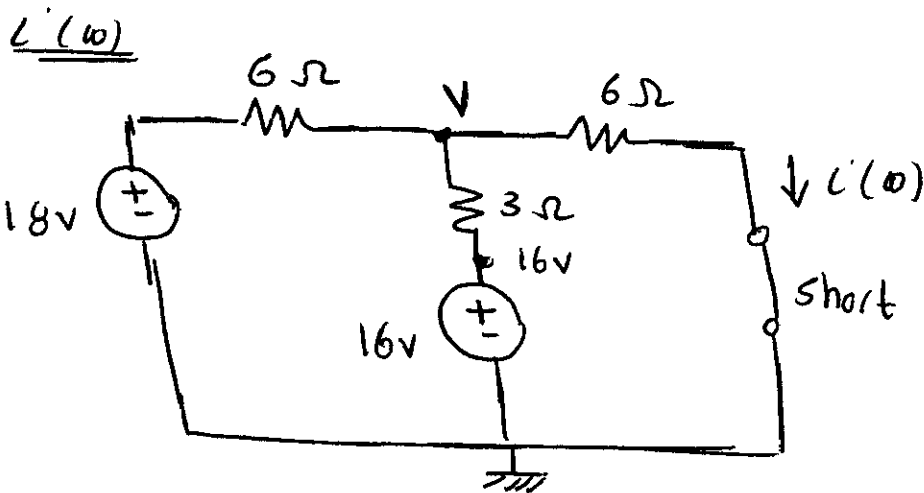
$$i'(t) = i'(\infty) + [i'(4^+) - i'(\infty)] e^{-t/\tau_2}$$



KCL


$$\frac{V-18}{6} + \frac{V-16}{3} + \frac{V}{6} = 0 \Rightarrow V = \frac{25}{2} \text{ V}$$

$$i'(\infty) = \frac{V}{6} = \frac{25/2}{6} = \frac{25}{12} = 2.08 \text{ A}$$

$$i'(4^+) = i'(4^-) = 1.5 [1 - \underbrace{e^{-2(4)}}_{\approx 0}] \approx 1.5$$

$$\tau_2 = \frac{L_{eq}}{R_{eq2}}$$
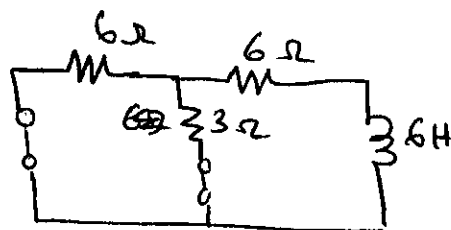
$$\tau_2 = \frac{6}{8} = \frac{3}{4} \text{ s}$$



$$R_{eq2} \text{ (seen by inductor)} = 6 + (6/3) = 8 \Omega$$

$$i'(t) = 2.08 + [1.5 - 2.08] e^{-\frac{4(t-4)}{3}}$$

$$= 2.08 + 0.583 e^{-\frac{4(t-4)}{3}} \text{ A}$$