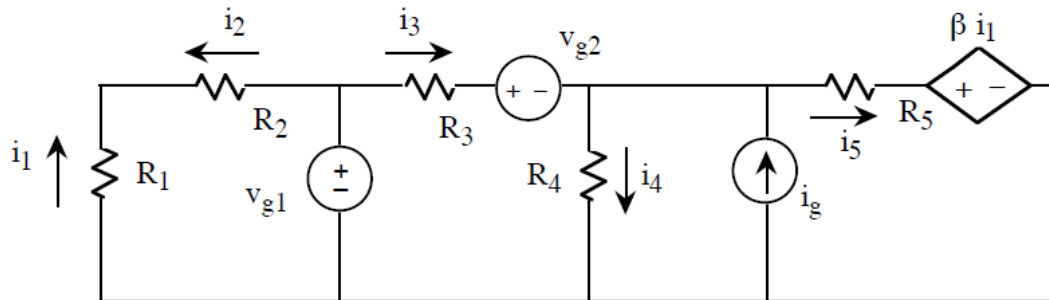



Problem 1

In the circuit below, the currents in each element are labeled as shown. Using the passive sign convention, label the potential difference across each element and show its polarity.



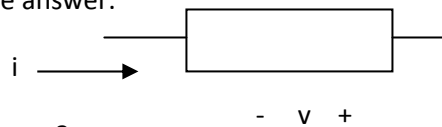Problem 2

Use the circuit diagram shown below to answer the following questions. Some of the questions have multiple answers. Circle the answer.



a) Is the circuit element producing power?

YES NO CAN'T TELL

b) If $v=5V$ and $i=-2\text{ mA}$, is the passive sign convention satisfied?

YES NO CAN'T TELL

c) If $v=-5V$ and $i=-2\text{ mA}$, is the passive sign convention satisfied?

YES NO CAN'T TELL

d) If $v=-2V$ and $i=5\text{ mA}$, then the circuit element is

Current Source Voltage Source Resistor

e) If $v=3V$ and $i=7\text{ mA}$, then the circuit element is

Current Source Voltage Source Resistor

f) If $v=0\text{ V}$ and $i=-7\text{ mA}$, then the circuit element is

Current Source Voltage Source Resistor

g) If $v=-12\text{ V}$ and $i=0\text{ mA}$, then the circuit element is

Current Source Voltage Source Resistor

h) Which of the following circuit elements can either absorb or dissipate power?

Current Source Voltage Source Resistor

i) Which of the following circuit elements can be safely connected in series with another circuit element of the same type?

Current Source Voltage Source Resistor

j) Which of the following circuit elements can be safely connected in parallel with another circuit element of the same type?


Current Source Voltage Source Resistor

Problem 3

The value of the gain of the dependent source is


$r =$ _____ Volts / Amp.

- a. 8 b. 10
- c. 12 d. 16
- e. 20 f. 24
- g. None of the above

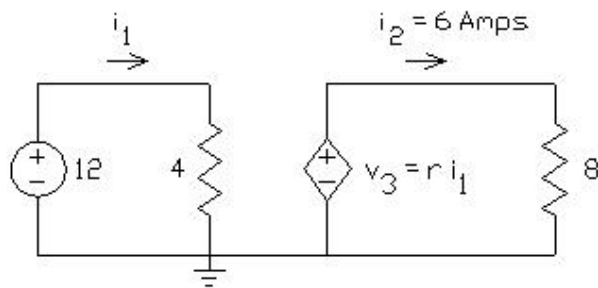

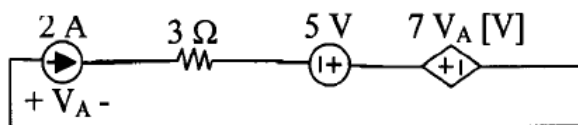Problem 4


Find the power associated with the dependent voltage source (P_{DEP}).



$P_{DEP} =$ _____ [W]


Problem 5

- (a) How many nodes are there?
- (b) How many branches are there?
- (c) If we move from B to F to E to C, have we formed a path? A loop?

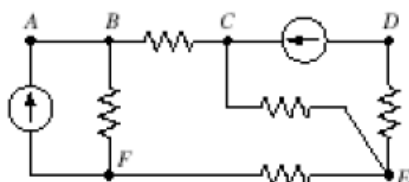

Problem 6

- (a) Find i_x if $i_y = 2 \text{ A}$ and $i_z = 0 \text{ A}$.
 (b) Find i_y if $i_x = 2 \text{ A}$ and $i_z = 2 i_y$.
 (c) Find i_z if $i_x = i_y = i_z$.

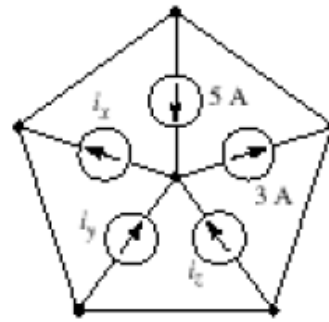

Problem 7

Find the power absorbed by each of the six circuit elements

