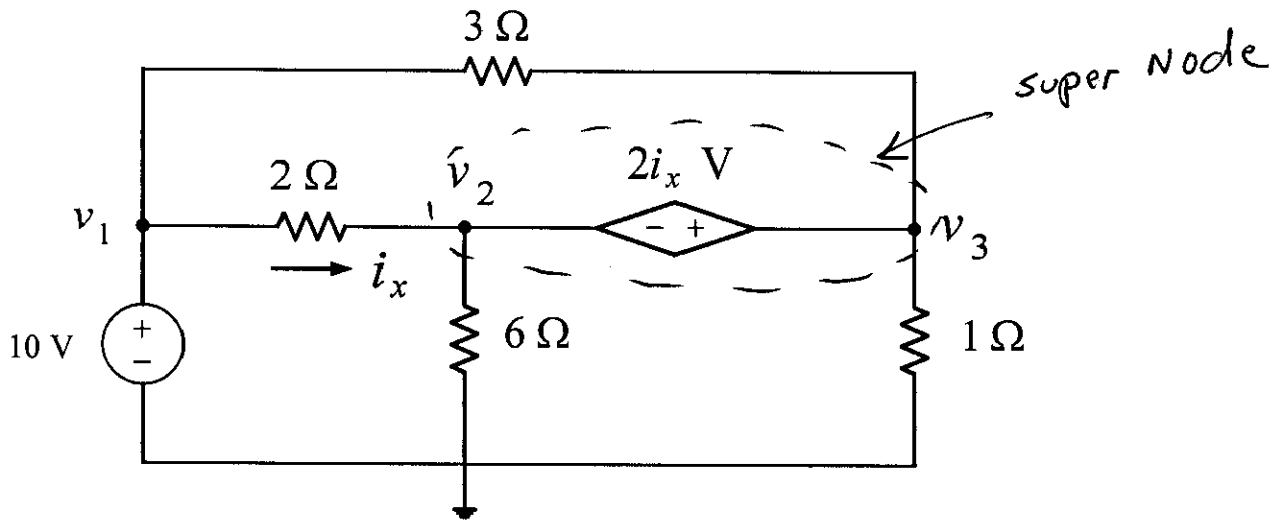


EE 201-01 – Fall 2011(111)
Quiz 2

SER	ID	NAME	KEY
-----	----	------	-----



For the circuit shown above use the Node voltage method to find the followings:

- (a) v_1, v_2, v_3 ?
 (b) Power absorb by the 6Ω resistor ?

(a) $v_1 = 10$ V by inspection

KCL ON SN $\frac{v_2 - 10}{2} + \frac{v_2}{6} + \frac{v_3}{1} + \frac{v_3 - 10}{3} = 0$

$\Rightarrow 2v_2 + 4v_3 = 25$ — (1)

$v_3 - v_2 = 2i_x' = 2 \left(\frac{10 - v_2}{2} \right) = 10 - v_2$

$\Rightarrow v_3 = 10$

from (1) $\Rightarrow v_2 = \frac{25 - 4(10)}{2} = -7.5$ V

$\Rightarrow \boxed{v_1 = 10 \quad v_2 = -7.5 \quad v_3 = 10}$

(b) $P_{6\Omega} = \frac{v_2^2}{6} = \frac{(-7.5)^2}{6} = \boxed{9.375 \text{ W}}$