
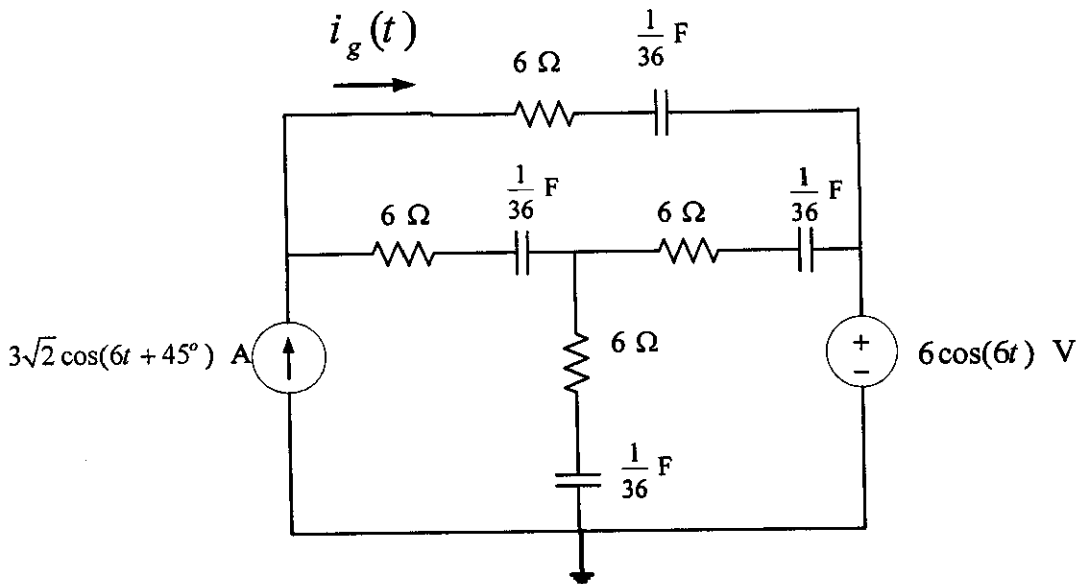


SER	ID	NAME	KEY
-----	----	------	-----

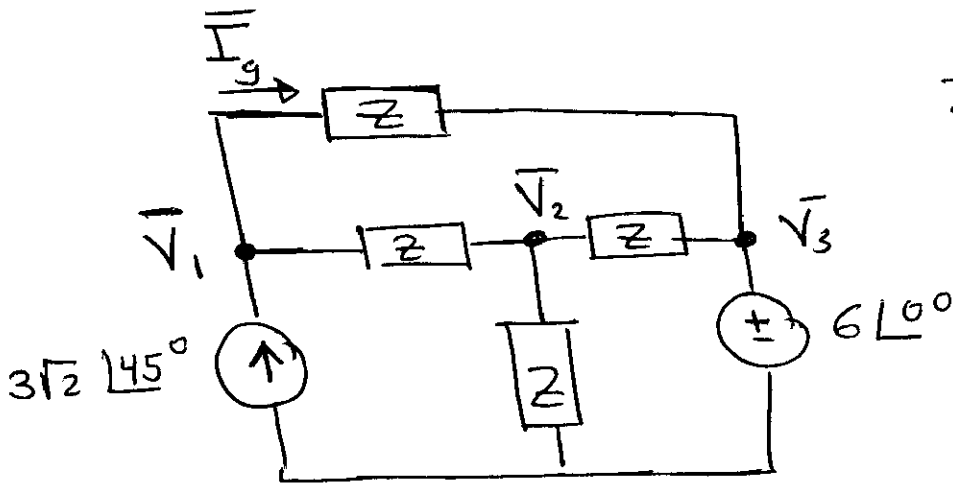

For the circuit shown above, find  $i_g(t)$  ?



$$Z = 6 - j6 \Omega$$

$$= 6\sqrt{2} \angle -45^\circ \Omega$$

$$\bar{V}_3 = 6 \angle 0^\circ \text{ V}$$

(by inspection)

KCL at  $\bar{V}_2$

$$\frac{\bar{V}_2 - 6 \angle 0^\circ}{Z} + \frac{\bar{V}_2}{Z} + \frac{\bar{V}_2 - \bar{V}_1}{Z} = 0$$

$$\Rightarrow 3\bar{V}_2 - \bar{V}_1 + 3\bar{V}_2 = 6 \angle 0^\circ \quad \text{--- (1)}$$

KCL at  $\bar{V}_1$

$$\frac{\bar{V}_1 - \bar{V}_2}{Z} + \frac{\bar{V}_1 - 6 \angle 0^\circ}{Z} = 3\sqrt{2} \angle 45^\circ$$

$$\Rightarrow 2\bar{V}_1 - \bar{V}_2 = 3\sqrt{2} \angle 45^\circ Z + 6 \angle 0^\circ$$

$$2\bar{V}_1 - \bar{V}_2 = 42 \angle 0^\circ \quad \text{--- (2)}$$

Solving for  $\bar{V}_1$  (No need to solve for  $\bar{V}_2$ )

$$\bar{V}_1 = \frac{132}{5} \angle 0^\circ \text{ V}$$

$$\begin{aligned}\Rightarrow \bar{I}_g &= \frac{\bar{V}_1 - \bar{V}_3}{Z} \\ &= \frac{\frac{132}{5} \angle 0^\circ - 6 \angle 0^\circ}{6\sqrt{2} \angle -45^\circ} \\ &= \frac{17}{10} \sqrt{2} \angle 45^\circ \text{ A} \\ &= 2.4 \angle 45^\circ \text{ A}\end{aligned}$$

$$\Rightarrow i_g(t) = 2.4 \cos(6t + 45^\circ) \text{ A}$$