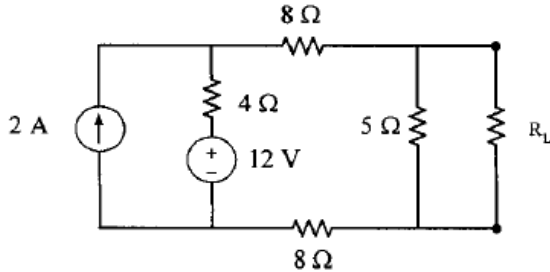



Problem 1:



For the circuit shown above find the maximum power absorb by the load resistor R_L ?

since $P_{max} = \frac{V_{oc}^2}{4R_{th}} \Rightarrow$ we need Thevenin equivalent

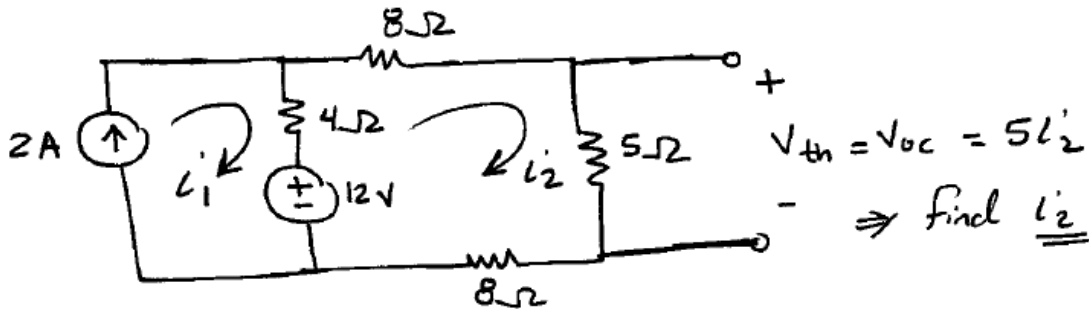
step ① Remove the load R_L and find $V_{th} = V_{oc}$



$i_1 = 2A$ by inspection

KVL on mesh ② $-12 + 4(i_2 - i_1) + 8i_2 + 5i_2 + 8i_2 = 0$
 $\Rightarrow i_2 = 0.8A \Rightarrow \boxed{V_{oc} = V_{th} = 4V}$

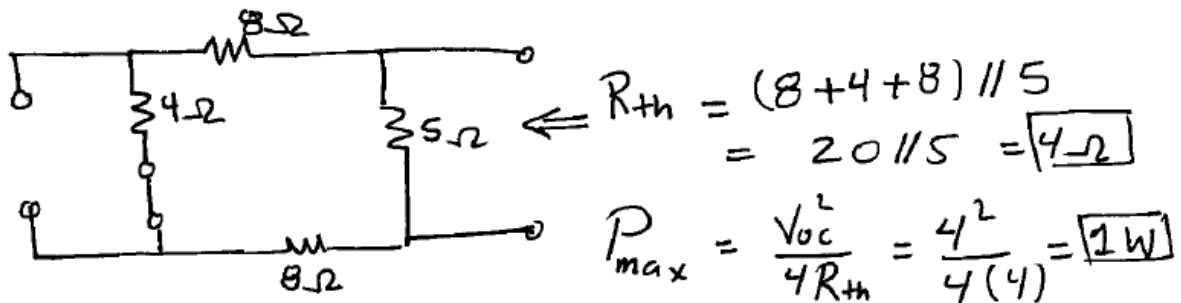step ② Deactivate independent sources to find R_{th}



$$R_{th} = (8+4+8) \parallel 5 = 20 \parallel 5 = \boxed{4\Omega}$$


$$P_{max} = \frac{V_{oc}^2}{4R_{th}} = \frac{4^2}{4(4)} = \boxed{1W}$$

Problem 2:

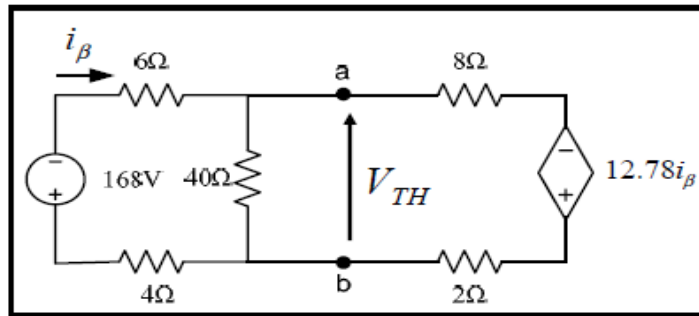a) We need to calculate the Thevenin equivalent circuit.

First, we calculate V_{TH} using node-voltage:


$$\begin{cases} \frac{V_{TH} + 168}{4 + 6} + \frac{V_{TH}}{40} + \frac{V_{TH} + 12.78i_{\beta}}{2 + 8} = 0 \\ i_{\beta} = -\frac{V_{TH} + 168}{4 + 6} \end{cases} \Rightarrow V_{TH} = 48.05 \text{ V}$$



Then, we calculate the short-circuit current I_{SC} using the circuit below:

$$\begin{cases} i_{\beta} = \frac{-168}{4 + 6} = -16.8 \text{ A} \\ i_1 = \frac{-12.78i_{\beta}}{2 + 8} = 21.47 \text{ A} \end{cases} \Rightarrow I_{SC} = i_{\beta} + i_1 = 4.67 \text{ A} \Rightarrow R_{TH} = \frac{V_{TH}}{I_{SC}} = 10.29 \Omega$$

$$R_L = R_{TH} = 10.29 \Omega$$


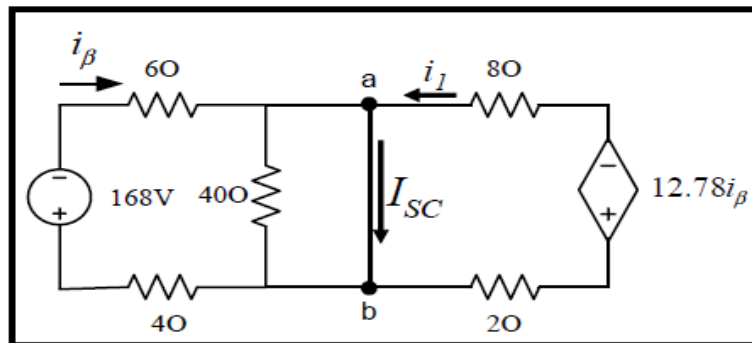


b) $P_{\max} = \frac{V_{TH}^2}{4R_L} = 56.10 \text{ W}$


Problem 3:

superposition \Rightarrow Deactivate all independent sources except one source remain active.


20V active

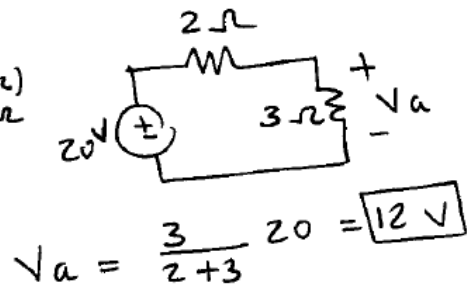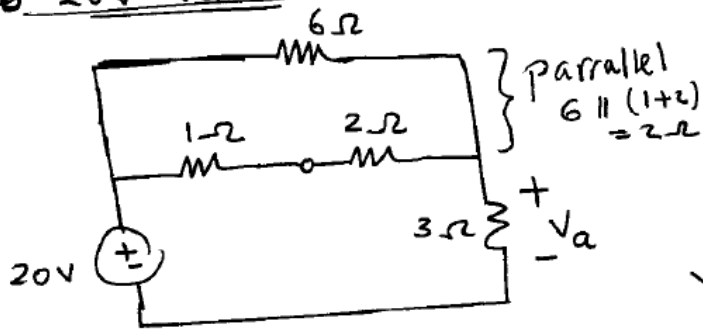

15A active


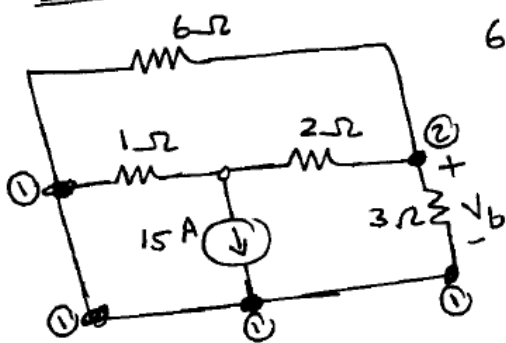


$6\Omega \parallel 3\Omega$

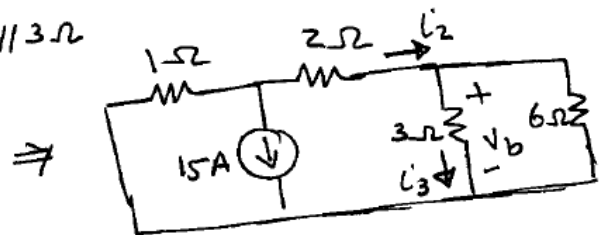

$$V_b = 3 i_3 \Rightarrow \text{find } i_3$$
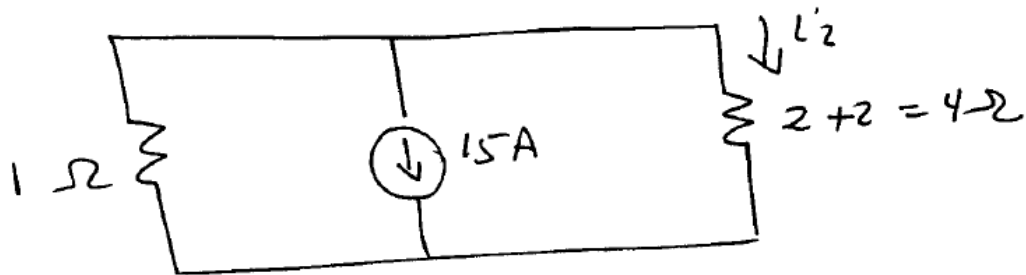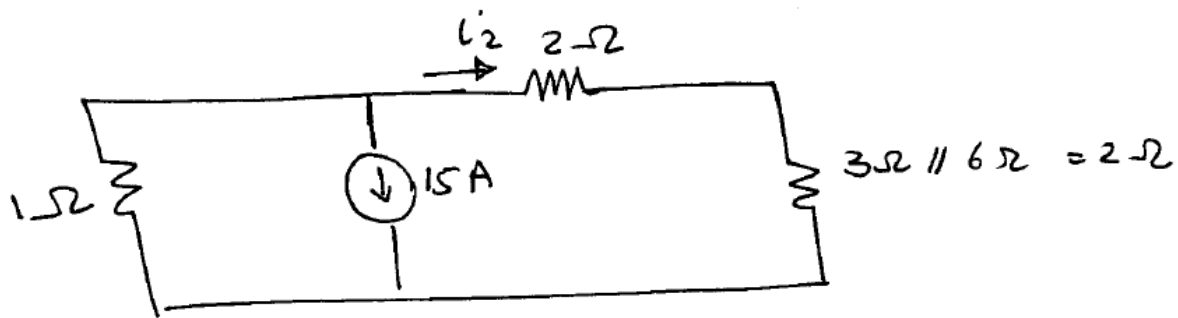
$$i_3 = \frac{6}{6+3} i_2 \Rightarrow \text{find } i_2$$




$$l'_2 = \frac{1}{1+4} (-15) = -3A$$




$$\Rightarrow l'_3 = \frac{6}{6+3} l'_2 = \frac{6}{9} (-3) = -2A$$

$$\Rightarrow V_b = 3 l'_3 = 3(-2) = \boxed{-6V}$$

15A active

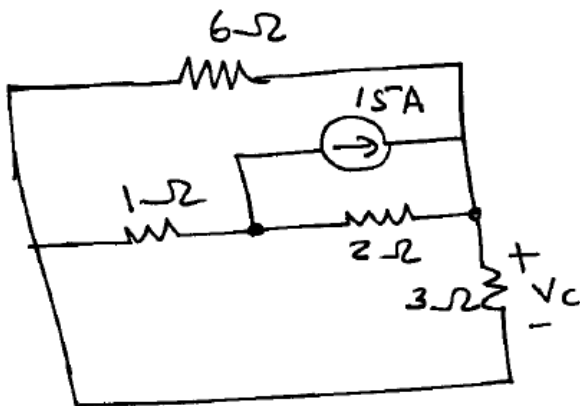

$$6\Omega \parallel 3\Omega$$

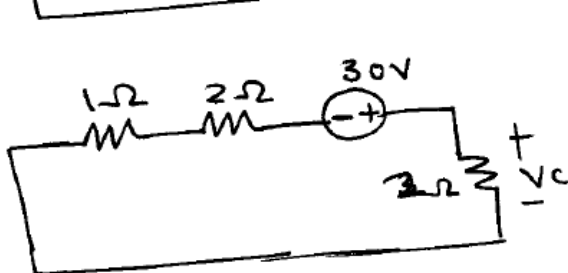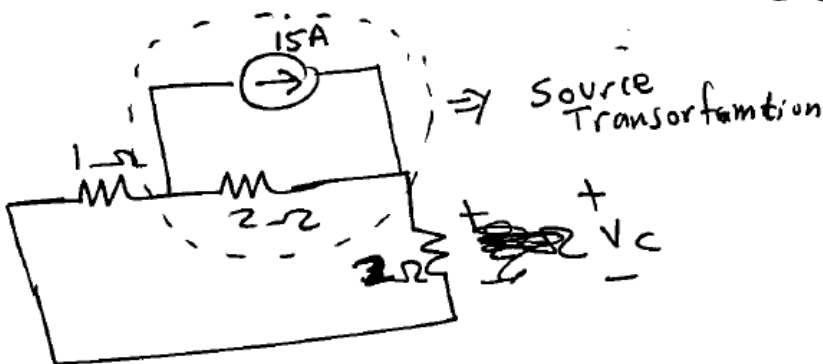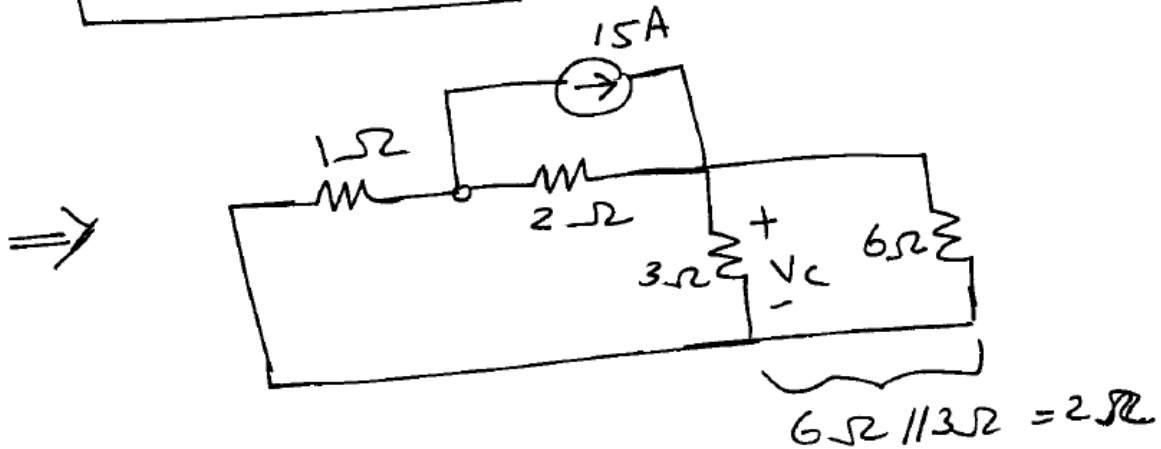


$$V_c = \frac{2}{1+2+2} (30) = \boxed{12V}$$

$$\Rightarrow V = V_a + V_b + V_c = 12 - 6 + 12 = \boxed{18V}$$

Problem4:

4A active

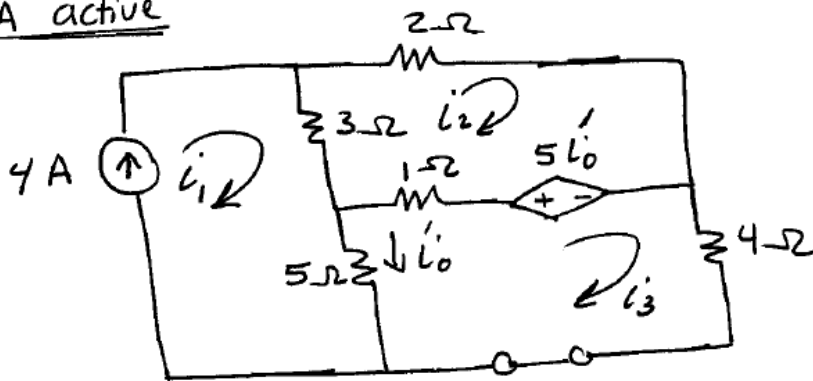

$i_1 = 4A$ by inspection

KVL mesh (2)

$$3(i_2 - i_1) + 2i_2 - 5i'_0 + 1(i_2 - i_3) = 0$$

$$-3i_1 + 6i_2 - 1i_3 - 5i'_0 = 0$$

$$i_1 = 4A \quad i'_0 = i_1 - i_3 = 4 - i_3$$

$$\Rightarrow 6i_2 + 4i_3 = 32 \quad \text{--- (1)}$$

KVL on mesh (3)


$$1(i_3 - i_2) + 5i'_0 + 4i_3 - 5i'_0 = 0$$

$$-i_2 + 5i_3 = 0 \quad \text{--- (2)}$$

solving (1), (2) For $i_3 \Rightarrow i_3 = 0.941 A$

$$\Rightarrow i'_0 = 4 - i_3 = \boxed{3.05 A}$$

20V active

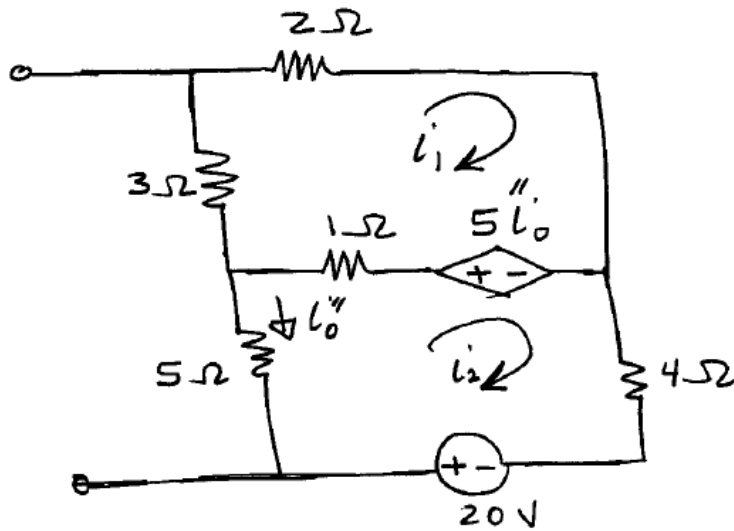

KVL on mesh ①

$$2i_1 - 5i_0'' + 1(i_1 - i_2) + 3i_1 = 0$$

$$6i_1 - i_2 - 5i_0'' = 0$$

$$i_0'' = -i_2$$

$$\Rightarrow 6i_1 + 4i_2 = 0 \quad \text{--- ①}$$

KVL on mesh ②

$$5i_0'' + 4i_2 - 20 - 5i_0'' + 1(i_2 - i_1) = 0$$

$$-i_1 + 5i_2 = 20 \quad \text{--- ②}$$

solving ① and ② for $i_2 \Rightarrow i_2 = 3.53 \text{ A}$

$$\Rightarrow i_0'' = -i_2 = -3.53 \text{ A}$$

$$\Rightarrow i_0 = i_0' + i_0'' = -0.48 \text{ A}$$

Problem 5: $L_{eq}=L$

Problem 6: $C_{eq}= 4F$