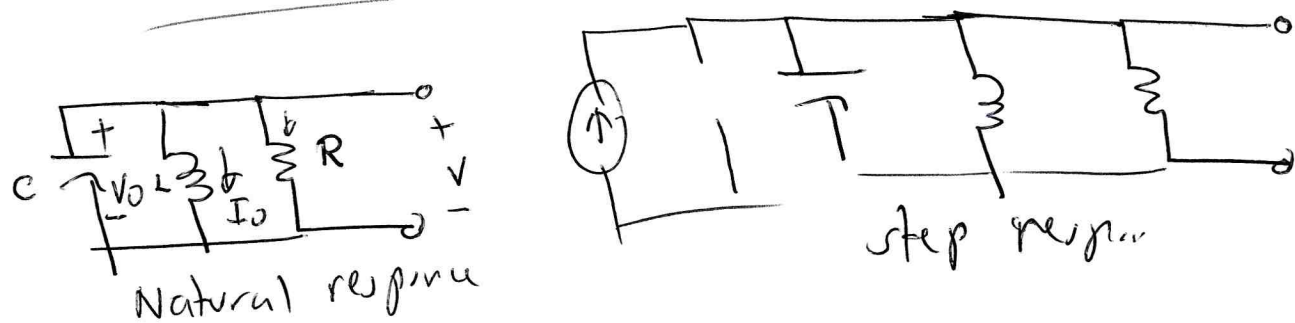




In this chapter we also extend the natural response and step response to circuits containing both inductors and capacitors and resistors.

we will consider two simple structures:


The parallel RLC



The series RLC

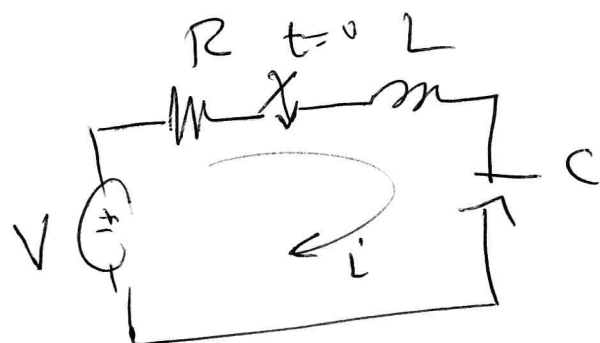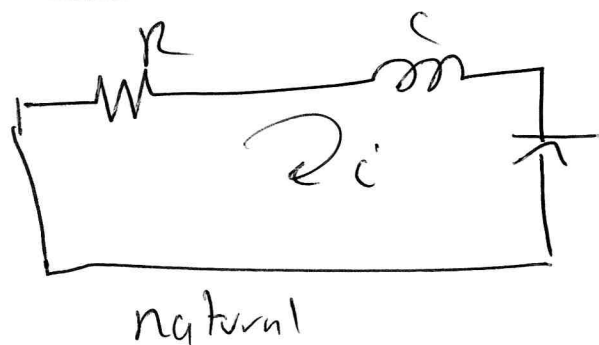

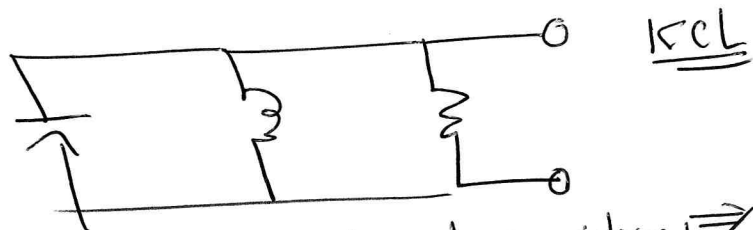8.10 The natural response of parallel RLC



$$\frac{v}{R} + \frac{1}{L} \int_0^t v d\tau + I_0 + C \frac{dv}{dt} = 0$$

$$\frac{1}{R} \frac{dv}{dt} + \frac{v}{L} + C \frac{d^2v}{dt^2} = 0$$

eliminate the integral $\Rightarrow$

normalize the equation by dividing by C

$$\Rightarrow \frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0$$

This is a 2nd order differential equation
(highest order derivative is 2)

Constant Coefficients $\frac{1}{RC}$ $\frac{1}{LC}$

In this chapter we call such circuits ~~as~~ were
the highest order of derivative is 2
second order circuits

The general solution of the second-order
differential equation

In equation $\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0$

we can not solve it by separating the
variables and integrating as we were able
to do with 1st order equations in chapter 7.

The classical approach to solve the 2nd order
equation is to assume that the solution
is of exponential form

$$v(t) = A e^{st}$$

where A and s are unknown constants

(3)

Q: what type of a function that will satisfied the 2nd order differential equation

$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0$$

A: We are seeking a function such that when we add to its 2nd derivative a constant multiplied by the 1st derivative $(\frac{d^2 v}{dt^2})$ $(\frac{1}{RC} \frac{dv}{dt})$

and also add to it a constant multiplied by the function $(\frac{1}{LC} v)$

we get zero

The only function that satisfies this is of exponential nature similar to the one that satisfies the 1st order differential equation

$$v(t) = A e^{st}$$

where A and s are unknown constants

Now we substitute the proposed solution (4)
 $v(t) = A e^{-st}$
into the 2nd order differential equation

$$\frac{d^2 v(t)}{dt^2} + \frac{1}{Rc} \frac{dv(t)}{dt} + \frac{v(t)}{Lc} = 0$$

we get

$$A s^2 e^{st} + \frac{As}{Rc} e^{st} + \frac{A e^{st}}{Lc} = 0$$

simplifying

$$A e^{st} \left(s^2 + \frac{s}{Rc} + \frac{1}{Lc} \right) = 0$$

a solution to this is

$$A = 0$$

which can not be since
that will make the
solution $v(t) = A e^{st} = 0 \forall t$
which is a physical impossible
since energy is stored in either
the inductor or capacitor

$$e^{st} = 0$$

which can not for any
finite value of st

That will leave the only solution

$$s^2 + \frac{s}{Rc} + \frac{1}{Lc} = 0$$

This equation is called the "characteristic equation"
of the differential equation

The roots of this quadratic equation (5) determine the mathematical character of $v(t)$, this is why it is called the characteristic equation.

The two roots of the characteristic equation are

$$s_1 = -\frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

$$s_2 = -\frac{1}{2RC} - \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

If either root s_1 or s_2 substitute into the proposed solution $v(t) = A e^{st}$ it will satisfy the given differential equation

$$\frac{d^2v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0$$

This result holds regardless of the value of A $A e^{st} \left(s^2 + \frac{s}{RC} + \frac{1}{LC} \right) = 0$

this will equal zero for s_1 or s_2 regardless of the value of A

$\Rightarrow$ Will satisfy the solution $v(t) = A e^{st}$ regardless of A

Therefore,

$$v_1(t) = A_1 e^{s_1 t} \quad \text{and} \quad v_2(t) = A_2 e^{s_2 t}$$

(6)

will satisfies the differential equation

$$\frac{d^2 v}{dt^2} + \frac{1}{RC} \frac{dv}{dt} + \frac{v}{LC} = 0$$

i.e $v_1(t) = A_1 e^{s_1 t}$

$$\Rightarrow A_1 e^{s_1 t} \left(s_1^2 + \frac{s_1}{RC} + \frac{1}{LC} \right) = 0$$

$$\underbrace{\hspace{10em}}_{=0}$$

$$\Rightarrow v_1(t) = A_1 e^{s_1 t} \text{ is a solution}$$

Similarly

$$\Rightarrow A_2 e^{s_2 t} \left(s_2^2 + \frac{s_2}{RC} + \frac{1}{LC} \right) = 0$$

$$\underbrace{\hspace{10em}}_{=0}$$

$$\Rightarrow v_2(t) = A_2 e^{s_2 t} \text{ is a solution.}$$

~~We also~~ Also $v(t) = v_1(t) + v_2(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$
is a solution

IF

Also the sum of the two solutions,

$$v(t) = v_1(t) + v_2(t) \text{ is a solution}$$

$$= A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

substituting $v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$ into the differential equation we ~~get~~ we get.

$$\frac{dv(t)}{dt} = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}$$

$$\frac{d^2 v(t)}{dt^2} = A_1 s_1^2 e^{s_1 t} + A_2 s_2^2 e^{s_2 t}$$

substituting into the differential equation, we get

$$A_1 e^{s_1 t} \underbrace{\left(s_1^2 + \frac{1}{RC} s_1 + \frac{1}{LC} \right)}_{=0} + A_2 e^{s_2 t} \underbrace{\left(s_2^2 + \frac{1}{RC} s_2 + \frac{1}{LC} \right)}_{=0} = 0$$

$\Rightarrow v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$ is a solution to the differential equation

$\Rightarrow v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$ is the natural response of the parallel RLC

Therefore,

$U_1(t) = A_1 e^{s_1 t}$ is a solution

$U_2(t) = A_2 e^{s_2 t}$ is a solution

$U(t) = U_1(t) + U_2(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$ is a solution

However $U(t) = U_1(t) + U_2(t)$ is the general

solution
the roots of the characteristic equation $s^2 + \frac{s}{RC} + \frac{1}{LC} = 0$

$$s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$

are determined by the circuit parameters
 R, L and C

the initial conditions I_0 and V_0 (current
on the inductor) and V_0 (voltage across the
capacitor) determine the constants
 A_1 and A_2 .

The behavior of the solution $U(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$
depends on the values of s_1 and s_2

We write s_1 and s_2 as

9

$$s_{1,2} = - \underbrace{\frac{1}{2RC}}_{\alpha} \pm \sqrt{\underbrace{\left(\frac{1}{2RC}\right)^2}_{\alpha^2} - \underbrace{\frac{1}{LC}}_{\omega_0^2}}$$

where, $\alpha = \frac{1}{2RC}$ $\omega_0 = \frac{1}{\sqrt{LC}}$

$$\Rightarrow s_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}$$

$$s_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

Since, $\underbrace{s_1, s_2}_{\text{dimensionless}} = e^{\underbrace{s_1 t}_{\text{dimensionless}}}$

$\Rightarrow s_1$ and s_2 have ^{the} dimension of the reciprocal of time or frequency

$\Rightarrow \alpha$ and ω_0 also have dimension of ~~to~~ reciprocal of time or frequency

To distinguish among the frequencies s_1, s_2, α and ω_0

s_1 and s_2 referred to as complex frequencies
note s_1, s_2 can be complex

α neper frequency
 ω_0 resonant frequency

we will see the significant of ~~this~~ ¹⁰
this terminology as we move through
the chapter

All these frequencies have the dimension
of angular frequency per time ~~unit~~ or
radian/second (rad/s).

The nature of the roots s_1 and s_2
depend on the values of α and ω_0
or LRC.

There are three possible outcomes

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

1st If $\omega_0^2 < \alpha^2 \Rightarrow$ both ^{s_1 and s_2} roots will be
real and distinct

The voltage response is said to be
overdamped as will be discussed later

2nd If $\omega_0^2 > \alpha^2 \Rightarrow$ both s_1 and s_2 will be
Complex Conjugate

The voltage response is said to be
underdamped

3rd If $\omega_0^2 = \alpha^2 \Rightarrow s_1$ and s_2 will be equal
and real

The voltage response is said to be
critically damped

~~To find~~

$\alpha = \frac{1}{2RC}$ can be found from the circuit parameter R and C

The constants D_1 and D_2 can be found as follows:

$$v(0^+) = V_0 = D_2 \quad \text{--- (1)}$$


$$\frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C} = D_1 - \alpha D_2 \quad \text{--- (2)}$$

In practice, it is rarely we encounter critical damp because that require

$$\alpha = \frac{1}{2RC} = \omega_0 = \frac{1}{\sqrt{LC}}$$

which is difficult to select real components R, L, C that will satisfies $\alpha = \omega_0$.

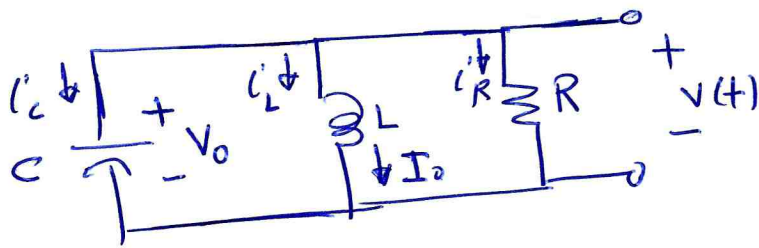8.2 The Forms of the Natural Response of a Parallel RLC Circuit



By KCL $\frac{d^2 v(t)}{dt^2} + \frac{1}{RC} \frac{dv(t)}{dt} + \frac{v(t)}{LC} = 0$

2nd-order diff. eqn.

$$v(t) = v_1(t) + v_2(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}}$$
$$= -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

$$\alpha = \frac{1}{2RC} \quad \text{Neper freq}$$
$$\omega_0 = \frac{1}{\sqrt{LC}} \quad \text{resonant freq}$$

s_1, s_2 Complex freq.

(1) IF $\alpha^2 > \omega_0^2$ s_1, s_2 are real and distinct
the response $v(t)$ is overdamped.

(2) IF $\alpha^2 < \omega_0^2$ s_1, s_2 are Complex Conjugate
the response $v(t)$ is underdamped

(3) IF $\alpha^2 = \omega_0^2$ $s_1 = s_2 = -\alpha = -\frac{1}{2RC}$
the voltage response $v(t)$ is critically damped.

$$v(t) = A_1 e^{s_1 t} + \cancel{A_2 e^{s_1 t}} A_2 e^{s_2 t}$$

s_1 and s_2 are determined as

~~$$s_{1,2} = -\alpha \pm$$~~

$$s_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \frac{1}{LC}} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

s_1, s_2 can be determined from RLC

A_1, A_2 can be determined from matching ~~the~~ $v(t)$ to the initial conditions $v(0), i'(0)$

We will analyze the natural response for the three type of damping.

(I) The overdamped Voltage Response

The roots s_1, s_2 are real and distinct ($\alpha^2 > \omega_0^2$)

The A_1, A_2 are determined from the initial conditions as follows:

$$v(0^+) = V_0 = A_1 + A_2 \quad - \textcircled{1}$$

We need a 2nd question ~~relat~~ relating A_1 and A_2

$$\frac{dv(t)}{dt} = A_1 s_1 e^{s_1 t} + A_2 s_2 e^{s_2 t}$$

$$\frac{dv(0^+)}{dt} = s_1 A_1 + s_2 A_2$$

Know how to find $\frac{dv(0^+)}{dt}$

Since,

$$i_c(t) = C \frac{dv(t)}{dt}$$

$$\Rightarrow i_c(0^+) = C \frac{dv(0^+)}{dt}$$

$$\Rightarrow \frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C}$$

From the circuit, by KCL,

$$i_c(t) + i_L(t) + i_R(t) = 0$$

$$\Rightarrow i_c(0^+) + i_L(0^+) + i_R(0^+) = 0$$

$$i_L(0^+) = I_0 \quad (\text{The initial condition}).$$

$$i_R(0^+) = \frac{v(0^+)}{R} = \frac{V_0}{R}$$

$$\Rightarrow i_c(0^+) = -\frac{V_0}{R} - I_0$$

$$\Rightarrow \frac{dv(0^+)}{dt} = \frac{i_c(0^+)}{C} = -\frac{V_0}{RC} - \frac{I_0}{C} = \cancel{s_1 A_1} + s_2 A$$

$$\Rightarrow s_1 A_1 + s_2 A_2 = -\frac{V_0}{RC} - I_0 \quad - (2)$$

The 2nd equation needed

note: s_1 and s_2 are determined from RLC

~~So~~
solving ① and ② we find A_1, A_2

$$\Rightarrow v(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

Example 8.2

Example 8.2 Finding the Overdamped Natural Response of a Parallel RLC Circuit

For the circuit in Fig. 8.6, $v(0^+) = 12$ V, and $i_L(0^+) = 30$ mA.

- Find the initial current in each branch of the circuit.
- Find the initial value of dv/dt .
- Find the expression for $v(t)$.
- Sketch $v(t)$ in the interval $0 \leq t \leq 250$ ms.

Solution

- The inductor prevents an instantaneous change in its current, so the initial value of the inductor current is 30 mA:

$$i_L(0^-) = i_L(0) = i_L(0^+) = 30 \text{ mA}.$$

The capacitor holds the initial voltage across the parallel elements to 12 V. Thus the initial current in the resistive branch, $i_R(0^+)$, is $12/200$, or 60 mA. Kirchhoff's current law requires the sum of the currents leaving the top node to equal zero at every instant. Hence

$$\begin{aligned} i_C(0^+) &= -i_L(0^+) - i_R(0^+) \\ &= -90 \text{ mA}. \end{aligned}$$

Note that if we assumed the inductor current and capacitor voltage had reached their dc values at the instant that energy begins to be released, $i_C(0^-) = 0$. In other words, there is an instantaneous change in the capacitor current at $t = 0$.

- Because $i_C = C(dv/dt)$,

$$\frac{dv(0^+)}{dt} = \frac{-90 \times 10^{-3}}{0.2 \times 10^{-6}} = -450 \text{ kV/s}.$$

- The roots of the characteristic equation come from the values of R , L , and C . For the values specified and from Eqs. 8.14 and 8.15 along with 8.16 and 8.17,

$$\begin{aligned} s_1 &= -1.25 \times 10^4 + \sqrt{1.5625 \times 10^8 - 10^8} \\ &= -12,500 + 7500 = -5000 \text{ rad/s}, \end{aligned}$$

$$\begin{aligned} s_2 &= -1.25 \times 10^4 - \sqrt{1.5625 \times 10^8 - 10^8} \\ &= -12,500 - 7500 = -20,000 \text{ rad/s}. \end{aligned}$$

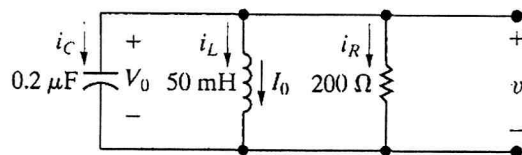


Figure 8.6 ▲ The circuit for Example 8.2.

Because the roots are real and distinct, we know that the response is overdamped and hence has the form of Eq. 8.18. We find the co-efficients A_1 and A_2 from Eqs. 8.23 and 8.24. We've already determined s_1 , s_2 , $v(0^+)$, and $dv(0^+)/dt$, so

$$12 = A_1 + A_2,$$

$$-450 \times 10^3 = -5000A_1 - 20,000A_2.$$

We solve two equations for A_1 and A_2 to obtain $A_1 = -14$ V and $A_2 = 26$ V. Substituting these values into Eq. 8.18 yields the overdamped voltage response:

$$v(t) = (-14e^{-5000t} + 26e^{-20,000t}) \text{ V}, \quad t \geq 0.$$

As a check on these calculations, we note that the solution yields $v(0) = 12$ V and $dv(0^+)/dt = -450,000$ V/s.

- Figure 8.7 shows a plot of $v(t)$ versus t over the interval $0 \leq t \leq 250$ ms.

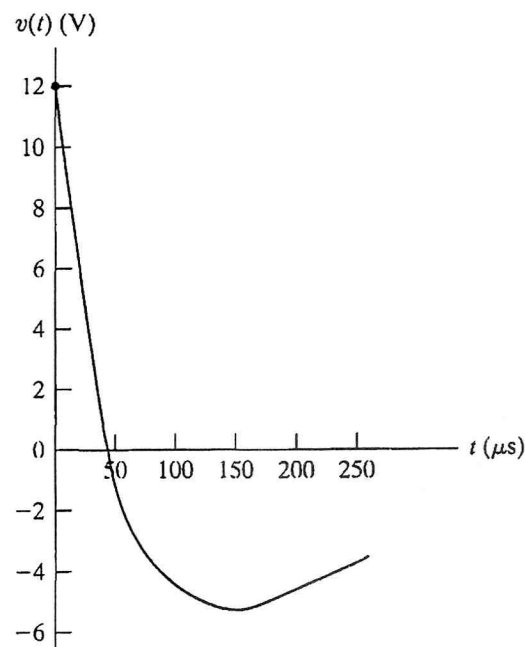


Figure 8.7 ▲ The voltage response for Example 8.2.

(II) The underdamped Voltage Response
 $\omega_0^2 > \alpha^2 \Rightarrow s_1 \text{ and } s_2 \text{ are Complex Conjugates}$

$$\begin{aligned} s_1 &= -\alpha + \sqrt{\alpha^2 - \omega_0^2} \\ &= -\alpha + \sqrt{-(\omega_0^2 - \alpha^2)} \\ &= -\alpha + j\sqrt{\omega_0^2 - \alpha^2} \\ &= -\alpha + j\omega_d \end{aligned}$$

where $\omega_d = \sqrt{\omega_0^2 - \alpha^2}$ is a frequency
called "damped radian frequency"

similarly $s_2 = -\alpha - j\omega_d$

$$\begin{aligned} \Rightarrow v(t) &= A_1 e^{s_1 t} + A_2 e^{s_2 t} \\ &= A_1 e^{-(\alpha - j\omega_d)t} + A_2 e^{-(\alpha + j\omega_d)t} \\ &= e^{-\alpha t} (A_1 e^{j\omega_d t} + A_2 e^{-j\omega_d t}) \end{aligned}$$

Using Euler identities: $e^{j\theta} = \cos\theta + j\sin\theta$
 $e^{-j\theta} = \cos\theta - j\sin\theta$

$$\begin{aligned} \Rightarrow v(t) &= e^{-\alpha t} [A_1 (\cos\omega_d t + j\sin\omega_d t) + A_2 (\cos\omega_d t - j\sin\omega_d t)] \\ &= e^{-\alpha t} [(A_1 + A_2) \cos\omega_d t + j(A_1 - A_2) \sin\omega_d t] \end{aligned}$$


Let,

$$B_1 = (A_1 + A_2)$$

$$B_2 = j(A_1 - A_2)$$

$$\Rightarrow v(t) = e^{-\alpha t} [B_1 \cos \omega_d t + B_2 \sin \omega_d t]$$

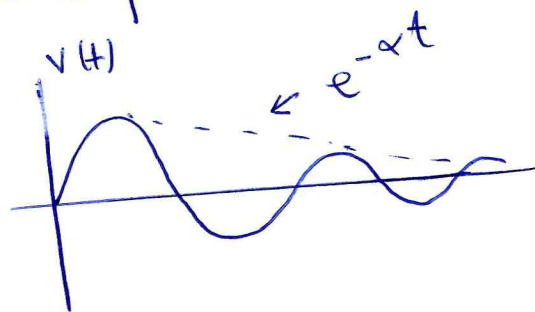It is clear that the natural response for this case is exponentially damped and oscillatory in nature



The constants B_1 and B_2 are real because $v(t)$ is real (the left hand side) therefore the right hand side is also real

In the ~~underdamped~~ underdamped case A_1 and A_2 are Complex Conjugate (Can be shown) P. 8.12, 8.13

Therefore ~~$A_1 + A_2$~~ is real

example

$$\begin{aligned} \text{Therefore } A_1 + A_2 &= A_1 + A_1^* = 2 \operatorname{Re}(A_1) \\ A_1 - A_2 &= A_1 - A_1^* = j 2 \operatorname{Im}(A_1) \end{aligned}$$

$$\begin{aligned} \Rightarrow B_1 &= A_1 + A_2 \text{ is } \cancel{\text{real}} = 2 \operatorname{Re}(A_1) \\ B_2 &= j(A_1 - A_2) = -2 \operatorname{Im}(A_1) \end{aligned}$$

$$v(t) = B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t$$

$$\alpha = \frac{1}{2RC} \quad \omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{\frac{1}{LC} - \left(\frac{1}{2RC}\right)^2}$$

can be determined from RLC

B_1 and B_2 can be determined from initial conditions $v(0^+) = V_0$ and $i(0^+) = I_0$

as follows:

$$v(0^+) = V_0 = B_1 e^{-0} \cos(0) + B_2 e^{-0} \sin(0) = B_1 \quad \text{--- (1)}$$

$$\frac{dv(t)}{dt} = -\alpha B_1 e^{-\alpha t} \cos \omega_d t - \omega_d B_1 e^{-\alpha t} \sin \omega_d t - \alpha B_2 e^{-\alpha t} \sin \omega_d t + \omega_d B_2 e^{-\alpha t} \cos \omega_d t$$

$$\frac{dv(t)}{dt} = -\alpha B_1 - 0 - 0 + \omega_d B_2 = -\alpha B_1 + \omega_d B_2$$

It was shown that $\frac{dv(0^+)}{dt} = -\frac{V_0}{RC} - \frac{I_0}{C}$

$$\Rightarrow -\alpha B_1 + \omega_d B_2 = -\frac{V_0}{RC} - \frac{I_0}{C} \quad \text{--- (2)}$$


solving (1), (2) we obtain B_1 and B_2

Ex 8.4

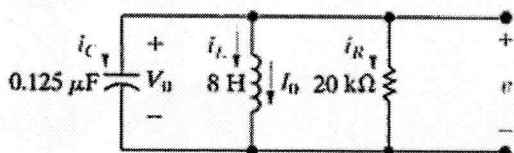Example 8.4 Finding the Underdamped Natural Response of a Parallel RLC Circuit

In the circuit shown in Fig. 8.8, $V_0 = 0$, and $I_0 = -12.25$ mA.

- Calculate the roots of the characteristic equation.
- Calculate v and dv/dt at $t = 0^+$.
- Calculate the voltage response for $t \geq 0$.
- Plot $v(t)$ versus t for the time interval $0 \leq t \leq 11$ ms.



② Therefore, the response is underdamped. Now,

$$\omega_d = \sqrt{\omega_0^2 - \alpha^2} = \sqrt{10^6 - 4 \times 10^4} = 100\sqrt{96} = 979.80 \text{ rad/s,}$$

$$s_1 = -\alpha + j\omega_d = -200 + j979.80 \text{ rad/s,}$$

$$s_2 = -\alpha - j\omega_d = -200 - j979.80 \text{ rad/s.}$$

For the underdamped case, we do not ordinarily solve for s_1 and s_2 because we do not use them explicitly. However, this example emphasizes why s_1 and s_2 are known as complex frequencies.

- b) Because v is the voltage across the terminals of a capacitor, we have

$$v(0) = v(0^+) = V_0 = 0.$$

Because $v(0^+) = 0$, the current in the resistive branch is zero at $t = 0^+$. Hence the current in the capacitor at $t = 0^+$ is the negative of the inductor current:

$$i_C(0^+) = -(-12.25) = 12.25 \text{ mA.}$$

Therefore the initial value of the derivative is

$$\frac{dv(0^+)}{dt} = \frac{(12.25)(10^{-3})}{(0.125)(10^{-6})} = 98,000 \text{ V/s.} = \frac{L i_C(0)}{C}$$

we use α and ω_d

$$v(t) = e^{-\alpha t} [B_1 \cos \omega_d t + B_2 \sin \omega_d t]$$

① Solution

a) Because

$$\alpha = \frac{1}{2RC} = \frac{10^6}{2(20)(0.125)} = 200 \text{ rad/s,}$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \sqrt{\frac{10^6}{(8)(0.125)}} = 10^3 \text{ rad/s,}$$

we have

$$v(0^+) = V_0 = B_1 \quad \omega_0^2 > \alpha^2 \quad \frac{dv(0^+)}{dt} = -\alpha B_1 + \omega_d B_2$$

③ c) From Eqs. 8.30 and 8.31, $B_1 = 0$ and

$$B_2 = \frac{98,000}{\omega_d} \approx 100 \text{ V.}$$

Substituting the numerical values of α , ω_d , B_1 , and B_2 into the expression for $v(t)$ gives

$$v(t) = 100e^{-200t} \sin 979.80t \text{ V, } t \geq 0.$$

d) Figure 8.9 shows the plot of $v(t)$ versus t for the first 11 ms after the stored energy is released. It clearly indicates the damped oscillatory nature of the underdamped response. The voltage $v(t)$ approaches its final value, alternating between values that are greater than and less than the final value. Furthermore, these swings about the final value decrease exponentially with time.

