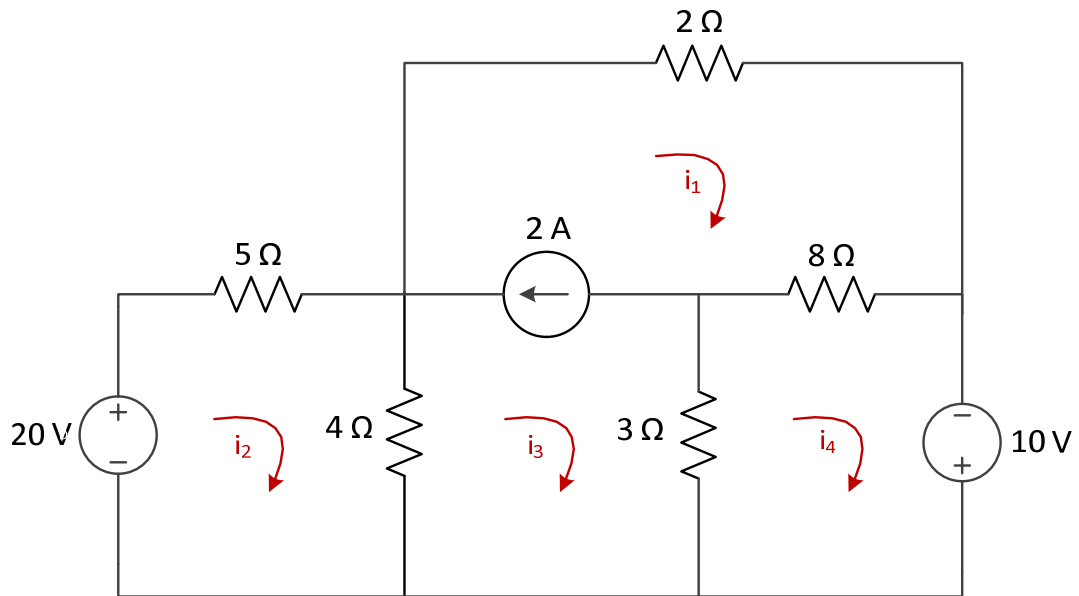


Q1 - a (15 points)



Write the mesh equations for i_1 , i_2 , i_3 , and i_4 in the matrix form

$$\begin{bmatrix} \\ \\ \\ \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} \\ \\ \\ \end{bmatrix}$$

(Note: Don't solve for the mesh currents i_1 , i_2 , i_3 , and i_4)

Solution

From the super-mesh

$$2i_1 + 8(i_1 - i_4) + 3(i_3 - i_4) + 4(i_3 - i_2) = 0$$

$$10i_1 - 4i_2 + 7i_3 - 11i_4 = 0 \quad \text{----(1)}$$

$$i_1 - i_3 = 2 \quad \text{----- (2)}$$

Mesh-2

$$-20 + 5i_2 + 4(i_2 - i_3) = 0$$

$$9i_2 + -4i_3 = 20 \quad \text{----(3)}$$


Mesh-4

$$-10 + 3(i_4 - i_3) + 8(i_4 - i_1) = 0$$

$$-8i_1 - 3i_3 + 11i_4 = 10 \quad \text{----(4)}$$

$$\begin{bmatrix} 10 & -4 & 7 & -11 \\ 1 & 0 & -1 & 0 \\ 0 & 9 & -4 & 0 \\ -8 & 0 & -3 & 11 \end{bmatrix} \begin{bmatrix} i_1 \\ i_2 \\ i_3 \\ i_4 \end{bmatrix} = \begin{bmatrix} 0 \\ 2 \\ 20 \\ 10 \end{bmatrix}$$

Q1 – b (15points)

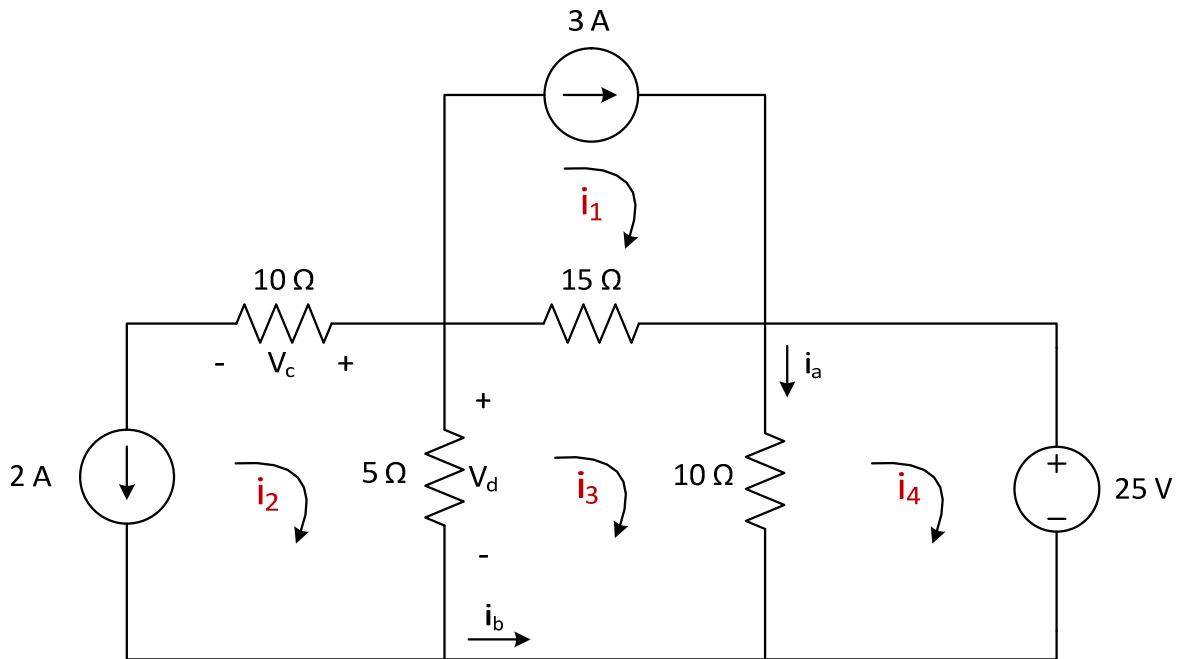

Given that

$$i_3 = 0.5 \text{ A}$$
$$i_4 = -2 \text{ A}$$

- Solve for i_1 and i_2
- Calculate the branch currents (i_a and i_b)
- Calculate the voltages (V_c and V_d)
- Calculate the power delivered by the 3 A current source.

Solution

a)

$$i_1 = 3 \text{ A}$$

$$i_2 = -2 \text{ A}$$

b)

$$i_a = i_3 - i_4 = 0.5 + 2 = 2.5 \text{ A}$$

$$i_b = i_d + 2 = (i_2 - i_3) + 2 = (-2 - 0.5) + 2 = -0.5 \text{ A}$$

c)

$$V_c = -10 (i_2) = -10 (-2) = 20 \text{ V}$$


$$V_d = 5 (i_2 - i_3) = 5(-2 - 0.5) = -12.5 \text{ V}$$

d)

$$V_{15\Omega} = 15(i_1 - i_3) = 15(3 - 0.5) = 15(2.5) = 37.5 \text{ V} \quad)$$

$$P_{3A} = -(3)(37.5) = -112.5 \text{ W}$$

Q2 (20)

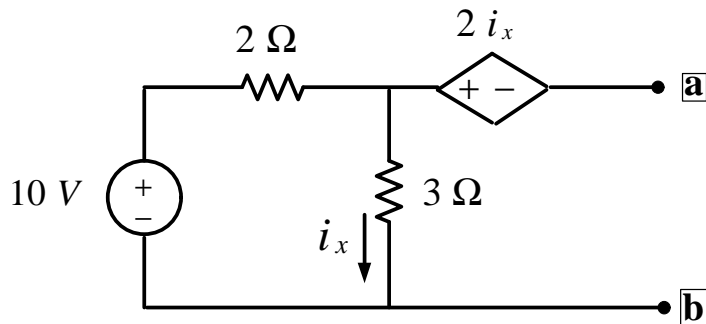


For the circuit shown above , find the followings :

- The open circuit voltage between terminals **a** and **b** ?
- The short circuit current through the terminals **a** and **b** ?
- The Thevenin equivalent resistant between terminals **a** and **b** ?
- The load resistant R_L between terminals **a** and **b** that will absorb the maximum power ?
- The maximum power absorbed by the load resistant R_L in part (d) ?

Solution


(a) (6)

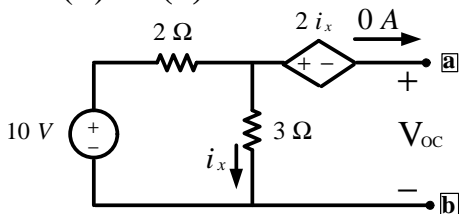

KVL on loop 1 $-10 + 5i_x = 0 \Rightarrow i_x = 2A$

KVL on loop 2 $-3i_x + 2i_x + V_{oc} = 0 \Rightarrow V_{oc} = 2V$

(b) (6)

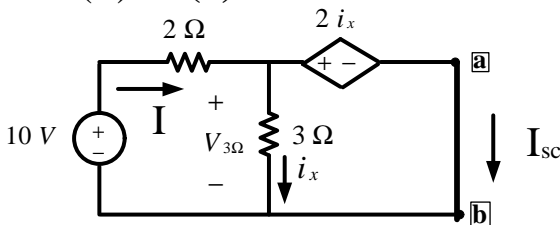

$V_{3\Omega} = 3i_x = 2i_x \Rightarrow i_x = 0$

$I_{sc} = I = \frac{10}{2} = 5A$

(c)

$$R_{\text{TH}} = \frac{V_{\text{oc}}}{I_{\text{sc}}} = \frac{2}{5} \Omega$$

(d)


$$R_{\text{L}} = R_{\text{TH}} = \frac{2}{5} \Omega$$

(d)

$$P_{\text{max}} = \frac{V_{\text{oc}}^2}{4R_{\text{TH}}} = \frac{4}{4(2/5)} = \frac{5}{2} = 2.5 \text{ W}$$

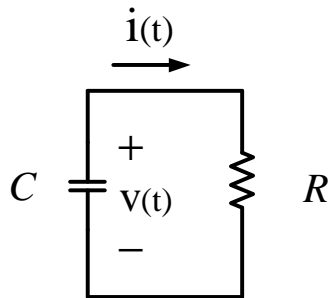Q3 (25)

Part I For the RC circuit shown below , the voltage across the capacitor and the current through the capacitor are



$$v(t) = 35e^{-10t} \text{ V for } t > 0$$

$$i(t) = 7e^{-10t} \text{ mA for } t > 0$$

Circle the correct answer :


(a) **The value of the resistor R is**

- (i) 7 k Ω (ii) 200 k Ω (iii) 35 k Ω **(iv) 5 k Ω** (v) $\frac{1}{5}$ k Ω (vi) $\frac{1}{200}$ k Ω

(a) **The value of the capacitor C is**

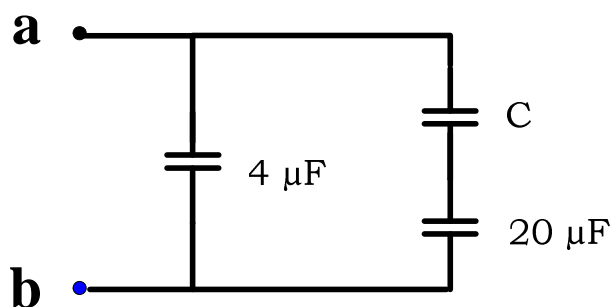- (i) 2000 μF (ii) 250 μF (iii) 200 μF **(iv) 20 μF** (v) 10 μF (vi) 5 μF


Part II The equivalent capacitance between terminals **a** and **b** in the circuit shown below is 8 μF .




(c) The value of the capacitor C is (**Circle the correct answer**)

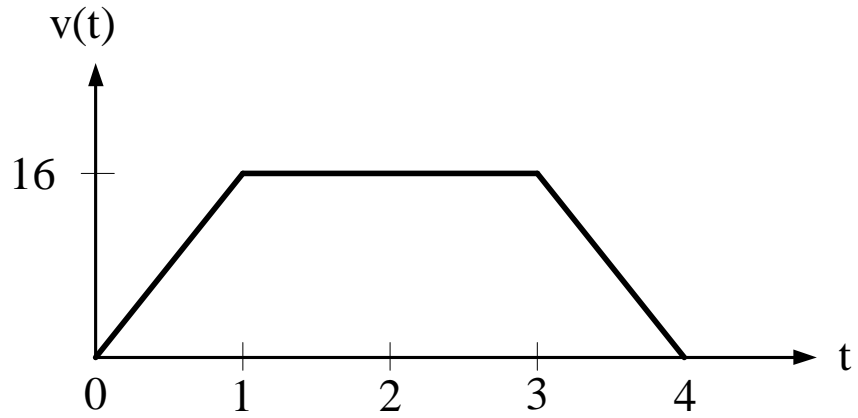- (i) 6 μF **(ii) 5 μF** (iii) 8 μF (iv) 2 μF (v) 10 μF (vi) 4 μF


Part III The voltage $v(t)$ across a 2 mF capacitor is shown below



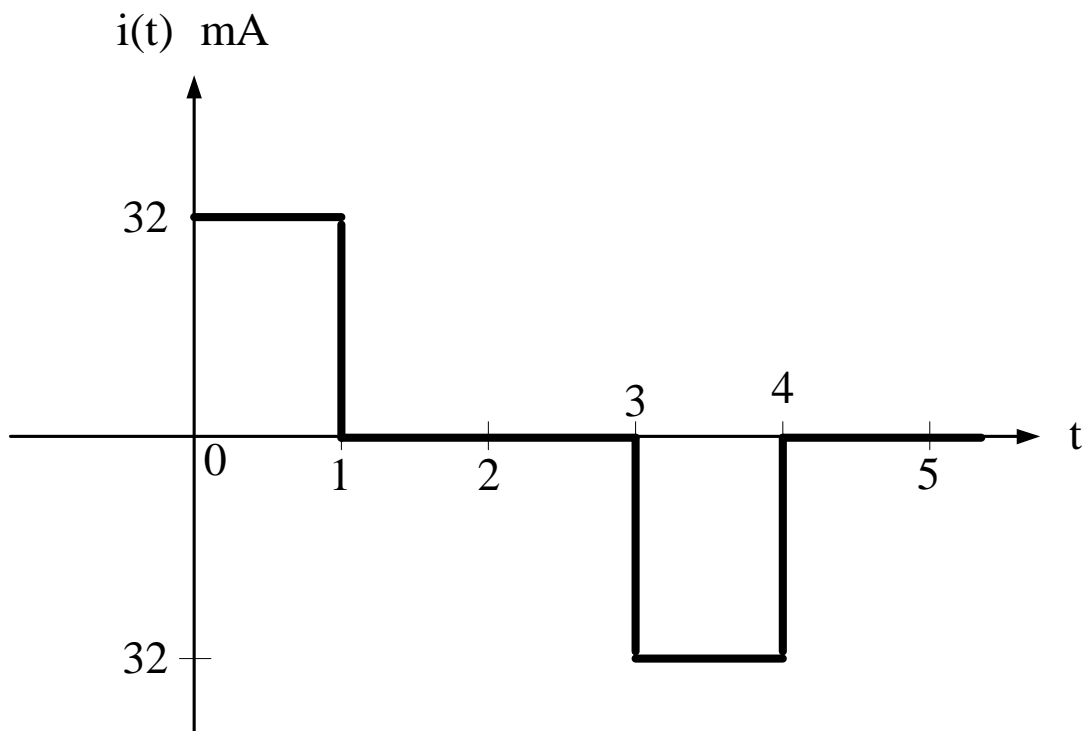(d) Plot current $i(t)$ through the capacitor showing all **significant values** ?




① After switching the circuit becomes ^①

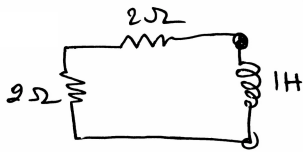

$$R_{eq} = 2 + 2 = 4\Omega$$

$$\therefore \tau = \frac{L}{R} = \frac{1}{4} \text{ sec.}$$

② Circuit before switching $t < 0$ is

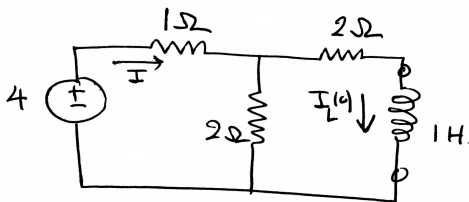

This circuit is equivalent to




$$\therefore I = \frac{4}{1 + 2 \parallel 2} = \frac{4}{1+1} = 2 \text{ A}$$

Using current division

$$I_L(0) = 1 \text{ A} = I_L(0^+)$$

(2)

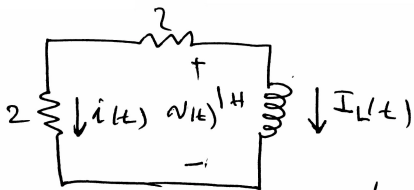

$$i(t) = -I_L(t) = -I_L(0^+) e^{-\frac{t}{\tau}}$$

$$= -e^{-4t} \quad t > 0$$

$$\textcircled{3} \quad v(t) = L \frac{dI_L(t)}{dt} = 1 \cdot \frac{d}{dt} (e^{-4t})$$

$$= -4e^{-4t}$$

(4) Energy in Inductor =

$$\frac{1}{2} L I_L(0)^2 = \frac{1}{2} \times 1 \times 1^2 = \frac{1}{2} \text{ Joule}$$