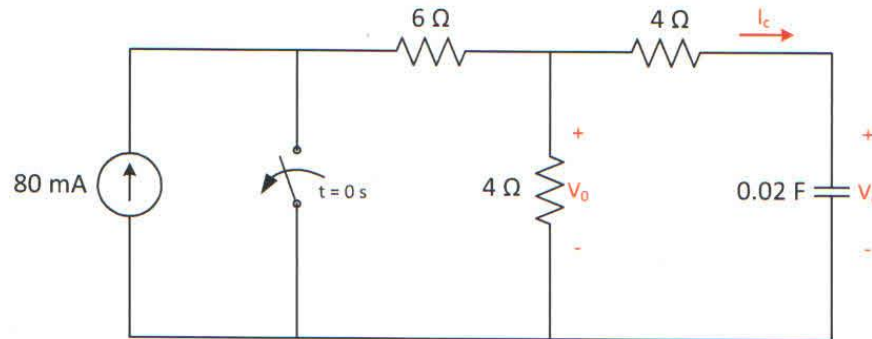


Q-1:

The switch in the circuit shown above has been closed for a long time before opening at $t=0$ s. for $t \geq 0$, find:


- $V_c(t)$
- $I_c(t)$
- $V_0(t)$

$$\begin{aligned} \textcircled{a} \quad V_c(0^-) &= 0 \\ V_c(\infty) &= 80 \times 10^{-3} (4) = 0.32 \text{ V} \\ \tau &= RC = 8(0.02) = 0.16 \\ \rightarrow V_c(t) &= 0.32 + (0 - 0.32) e^{-\frac{1}{0.16}t} \\ &= 0.32 - 0.32 e^{-\frac{1}{0.16}t} \quad t \geq 0 \end{aligned}$$

$$\textcircled{b} \quad I_c(t) = C \frac{dV_c(t)}{dt} = 0.02 \left(\frac{0.32}{0.16} e^{-\frac{1}{0.16}t} \right) = 0.04 e^{-\frac{1}{0.16}t} \quad t \geq 0$$

$$\begin{aligned} \textcircled{c} \quad V_0(t) &= 4 I_c(t) + V_c \\ &= 0.16 e^{-\frac{1}{0.16}t} + (0.32 - 0.32 e^{-\frac{1}{0.16}t}) \\ &= 0.32 - 0.16 e^{-\frac{1}{0.16}t} \quad t \geq 0 \end{aligned}$$

Q-2:

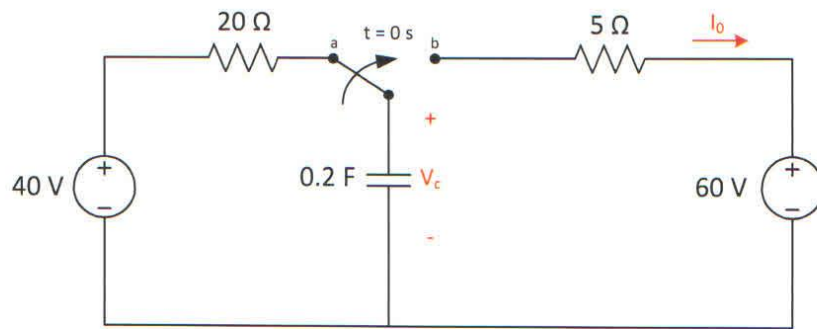

The switch in the circuit shown above has been in position *a* for a long time before switching to position *b* at $t=0$ s. Find:

- a) $V_c(0^+)$
- b) $V_c(t)$ for $t \geq 0$
- c) $V_c(\infty)$
- d) Time constant for $t \geq 0$
- e) $I_0(t)$ for $t \geq 0$

a) $V_c(0^+) = V_c(0^-) = 40 \text{ V}$

b) $V_c(\infty) = 60 \text{ V}$

$$V_c(t) = 60 + (40 - 60)e^{-t} = 60 - 20e^{-t} \quad t \geq 0$$


c) $V_c(\infty) = 60 \text{ V}$

d) $\tau = RC = 0.2 \times 5 = 1$

e) $I_0(t) = \frac{V_c(t) - 60}{5}$

$$= \frac{(60 - 20e^{-t}) - 60}{5} = -4e^{-t} \quad t \geq 0$$

Q-3:

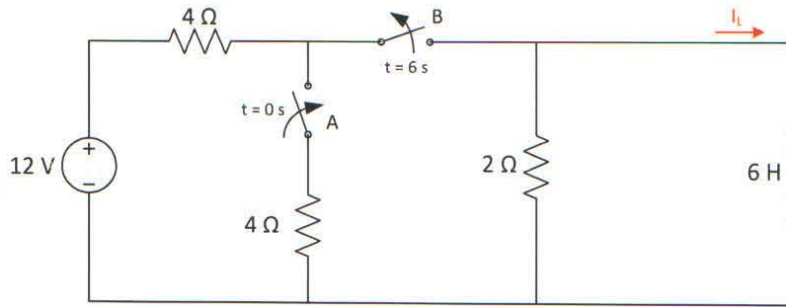

The switch A in the circuit shown above has been open and switch B has been closed for a long time. At $t=0$, switch A closes. After 6 seconds, switch B opens. Find $i_L(t)$ for $t \geq 0$.

⊗ for $0 \leq t \leq 6$

$$i_L(0^-) = 3 \text{ A}$$

$$i_L(0) = 3 \text{ A}$$

$$i_L(t) = 3 + (3-3)e^{-\frac{1}{6}t} = 3 \text{ A} \quad 0 \leq t \leq 6$$


⊗ for $t \geq 6$

$$i_L(6^-) = 3 \text{ A}$$

$$i_L(6) = 0$$

$$\begin{aligned} i_L(t) &= 0 + (3-0)e^{-\frac{1}{3}(t-6)} \\ &= 3e^{-\frac{1}{3}(t-6)} \quad t \geq 6 \end{aligned}$$

Q-4:

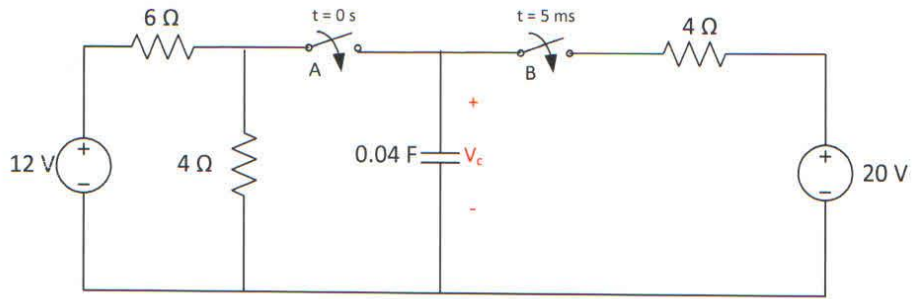

The switch A in the circuit shown above has been open and switch B has been closed for a long time. At $t=0$, switch A closes. At $t=5$ milliseconds, switch B then closes. Find $V_c(t)$ for $t \geq 0$.

⊗ for $0 \leq t \leq 0.005$

$$V_c(0^-) = 0$$

$$V_c(\infty) = 12 \frac{4}{10} = 4.8 \text{ V}$$


$$\tau = RC = \frac{4 \times 6}{10} (0.04) = 0.096$$

$$V_c(t) = 4.8 - 4.8 e^{-\frac{1}{0.096}t} \quad 0 \leq t \leq 0.005 \text{ s}$$

⊗ for $t \geq 0.005$

$$V_c(0.005^-) = 4.8 - 4.8 e^{-\frac{1}{0.096}(0.005)} = 0.243 \text{ V}$$

$$V_c(\infty) = 10.5 \text{ V}$$

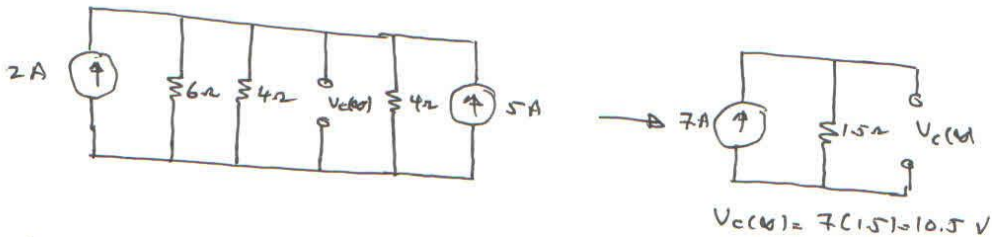

$$V_c(t) = 10.5 + (0.243 - 10.5) e^{-\frac{1}{(1.5)(0.04)}(t - 0.005)}$$

$$= 10.5 - 10.257 e^{-\frac{1}{0.06}(t - 0.005)} \quad t \geq 0.005 \text{ s}$$