

EE 202 (122) – HW4
Due Saturday April 6, 2013
Dr. Abdallah Al-Ahmari

Question 1:

For the circuit shown in Figure 1, find the following:

- a) What is the value of R_L that will maximize the power transfer to the load (R_L).
- b) With this value of R_L (part a), what the maximum power in R_L .

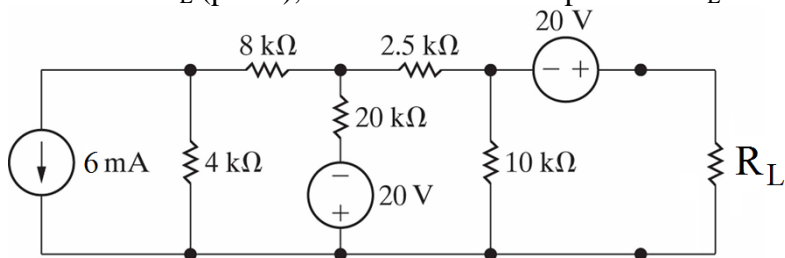


Figure 1

Question 2:

For the circuit shown in Figure 2, find the following:

- a) What is the value of R_L that will maximize the power transfer to the load (R_L).
- b) With this value of R_L (part a), what the maximum power in R_L .

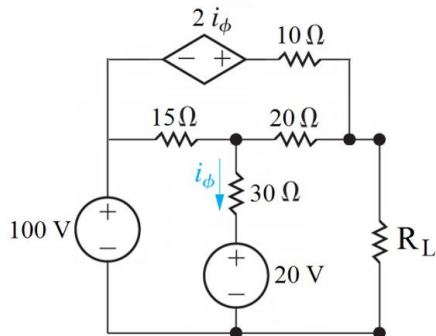


Figure 2

Question 3:

For the circuit shown in Figure 3, use the superposition principle to find the current i_o .

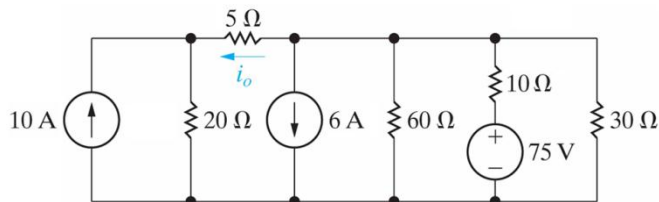


Figure 3

Question 4:

For the circuit shown in Figure 4, find the following:

- Find and sketch the current $i(t)$.
- Find and sketch the power $p(t)$ in the inductor.
- Find and sketch the energy $w(t)$ stored in the inductor.

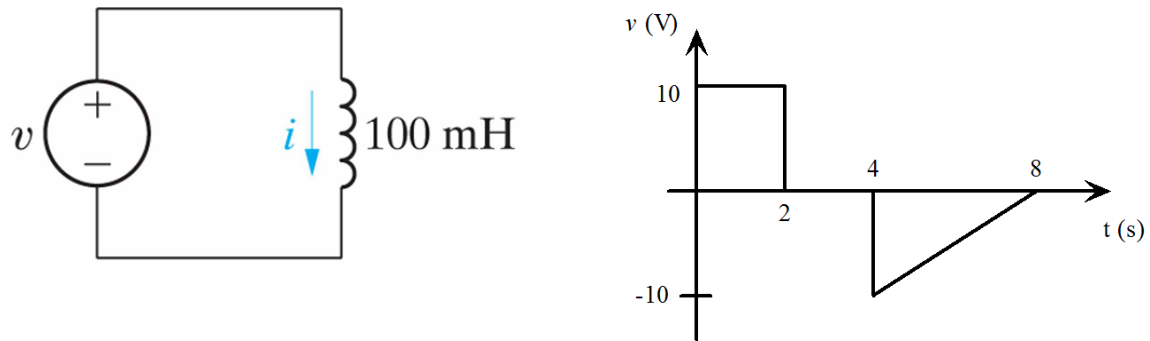


Figure 4


Question 5:

The four capacitors in the circuit below are connected across the terminals of a black box at $t = 0$. The resulting current i_b for $t > 0$ is known to be

$$i_b = 500e^{-40t} \mu\text{A}.$$

If $v_a(0) = 25 \text{ V}$, $v_c(0) = -20 \text{ V}$, $v_d(0) = 45 \text{ V}$, find the following for $t \geq 0$.

- $v_b(t)$,
- $v_a(t)$,
- $v_c(t)$,
- $v_d(t)$,
- $i_1(t)$, and
- $i_2(t)$.

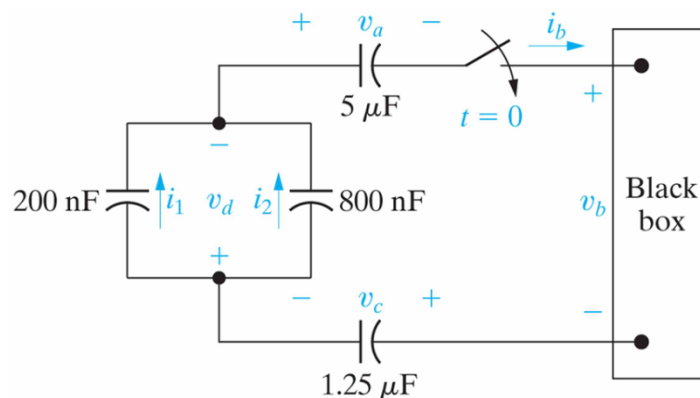

Question 6:

In the circuit shown in Figure 6, the switch has been closed for a long time. At $t = 0$ it is opened. Find the current $i_o(t)$ for $t \geq 0$.

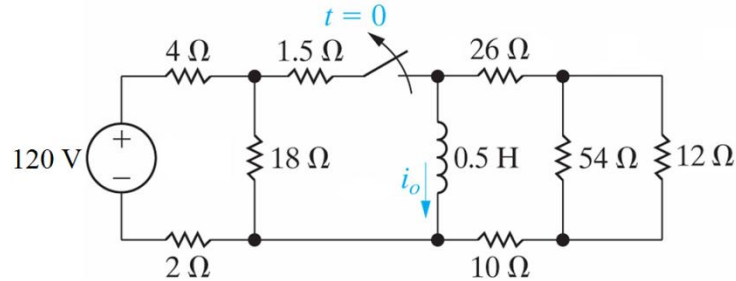


Figure 6

Question 7:

In the circuit shown in Figure 7, the two switches operate together; that is, they either open or close at the same time. The switches have been closed for a long time before opening at $t = 0$.

- a) How many microjoules of energy have been dissipated in the $68\text{ k}\Omega$ resistor 10 ms after the switches open.
- b) How long does it take to dissipate 90% of the initially stored energy?

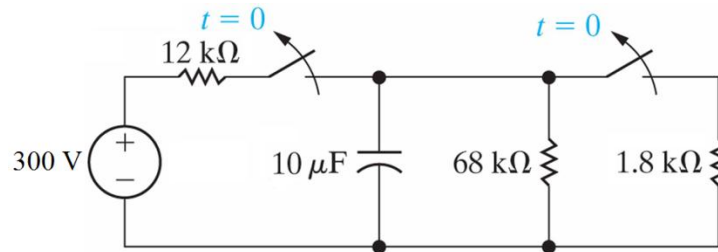


Figure 7