


EE 202 (122)

HW1 KEY

Due Monday 11/2/2013

Dr. Adil S. Balghonaim

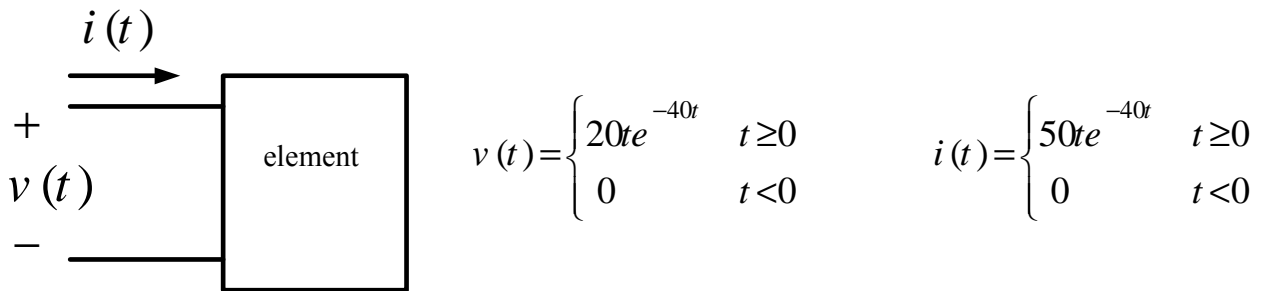Q1 The current entering the terminal of an element and the voltage across it are



$$v(t) = \begin{cases} 20te^{-40t} & t \geq 0 \\ 0 & t < 0 \end{cases}$$

$$i(t) = \begin{cases} 50te^{-40t} & t \geq 0 \\ 0 & t < 0 \end{cases}$$

Find the followings:

- The total charges entering the element (in milli coulombs) ?
- Find the time when the power delivered to the element is maximum ?
- Find the maximum power delivered to the element ?
- Find the total energy delivered to the element ?

(a) Since $q(t) = \int_{-\infty}^t i(\tau) d\tau \Rightarrow$ then $q_{\text{Total}} = \int_{-\infty}^{\infty} 50\tau e^{-40\tau} d\tau$

using intrgration by parts or intrgration table $q_{\text{Total}} = 31.2500 \text{ mC}$

(b) $p(t) = v(t)i(t) = \begin{cases} 1000t^2 e^{-80t} & t \geq 0 \\ 0 & t < 0 \end{cases} \Rightarrow \frac{dp(t)}{d(t)} = 1000te^{-80t} - 80,000t^2 e^{-80t} = 0$


$\Rightarrow 1 - 40t = 0 \Rightarrow t = \frac{1}{40} \text{ s} = 25 \text{ ms}$

(c) $P_{\text{max}} = p(25 \text{ ms}) = 84.5846 \text{ mW}$

(d) $W(t) = \int_{-\infty}^t p(\tau) d\tau \Rightarrow$ then $W_{\text{Total}} = \int_{-\infty}^{\infty} 1000\tau^2 e^{-80\tau} d\tau$

using intrgration by parts or intrgration table $W_{\text{Total}} = 3.9063 \text{ mJ}$

Q2

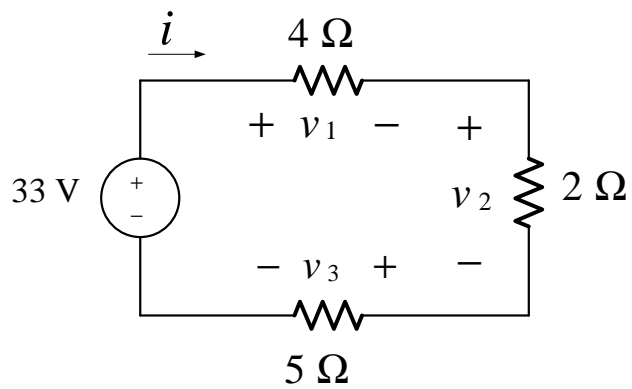

For the circuit shown above , find i , v_1 , v_2 , v_3 ?

KVL $-33+v_1+v_2+v_3=0$


ohms $\Rightarrow -33+4i+2i+5i=0 \Rightarrow -33+11i=0 \Rightarrow i=3A$

$$v_1 = 4i = 4(3) = 12 \text{ V}$$


$$v_2 = 2i = 2(3) = 6 \text{ V}$$

$$v_3 = 5i = 5(3) = 15 \text{ V}$$

Q3

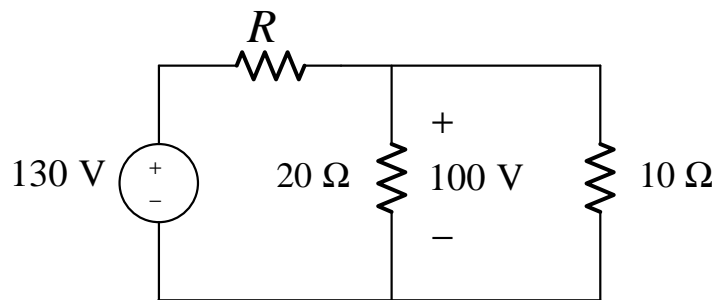

For the circuit shown above , find R ?

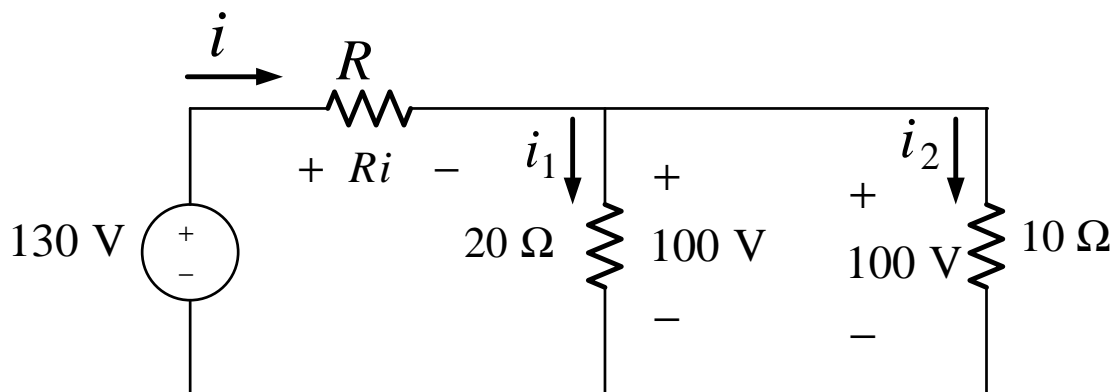


ohms $i_1 = \frac{100V}{20\Omega} = 5A$ $i_2 = \frac{100V}{10\Omega} = 10A$

KCL $i = i_1 + i_2 = 5 + 10 = 15A$

KVL $-130 + Ri + 100 = 0 \Rightarrow -30 + R(15) = 0 \Rightarrow R = 2\Omega$

Q4

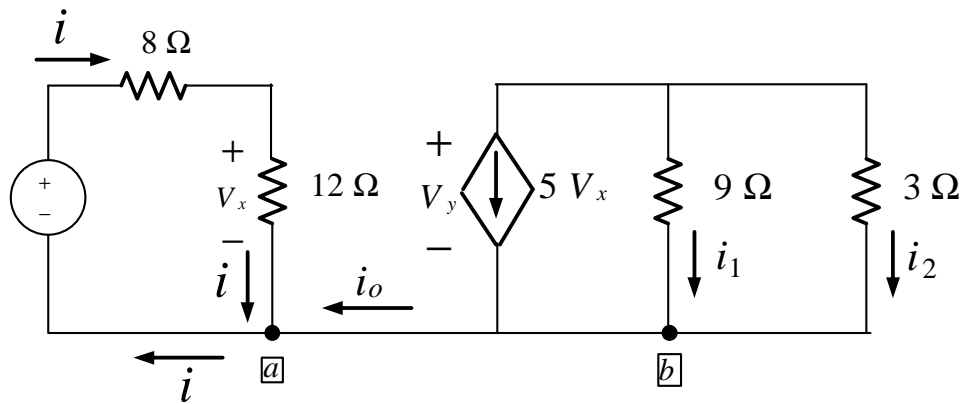

For the circuit shown above , find the followings:

- i_o ?
- i_1 ?
- i_2 ?
- The power deliver by the independent source ?
- The power absorb by the dependent source ?

(a) KCL at node **a** $\Rightarrow i + i_o - i = 0 \Rightarrow i_o = 0$

(b) KVL $-20 + 8i + 12i = 0 \Rightarrow i = 1\text{A} \Rightarrow V_x = 12(1) = 12\text{ V}$

KCL at node **b** $\Rightarrow 5V_x + i_1 + i_2 = 0 \Rightarrow 5(12) + i_1 + i_2 = 0 \Rightarrow i_1 + i_2 = -60$ (1)

however since $9i_1 = 3i_2 \Rightarrow i_2 = 3i_1$ (2)


(2) \Rightarrow (1) $i_1 + 3i_1 = -60 \Rightarrow i_1 = -15\text{A}$

(c) $i_2 = 3i_1 = 3(-15) = -45\text{A}$

(d) $P_{20\text{V}}^{\text{absorbed}} = -(20)i = -(20)(1) = -20\text{ W} \Rightarrow P_{20\text{V}}^{\text{deliver}} = 20\text{ W}$

(e) $P_{5V_x}^{\text{absorbed}} = (V_y)i = (9i_1)(5V_x) = [9(-15)][5(12)] = -8100\text{ W}$

Q5

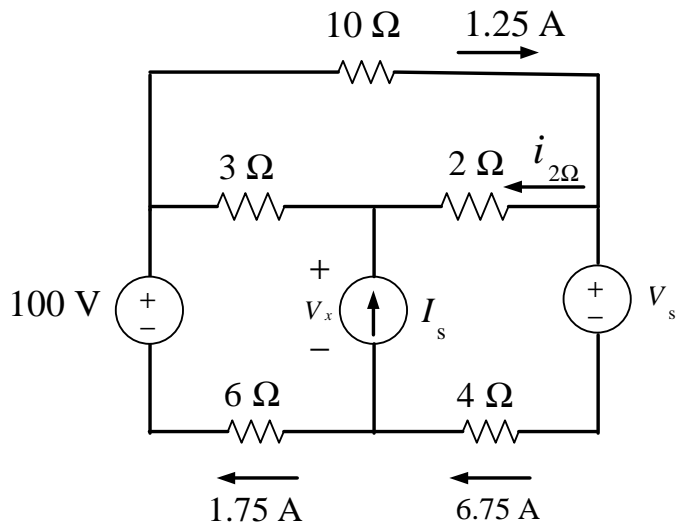

For the circuit shown above , find the followings:

- (a) I_s ?
- (b) V_s ?
- (c) The power absorb by the $2\ \Omega$ resistor ?
- (d) power deliver by the independent current source ?

(a) KCL $6.75 = I_s + 1.75 \Rightarrow I_s = 5\ A$

(b) KVL $-100 + 10(1.25) + V_s + 4(6.75) + 6(1.75) = 0 \Rightarrow V_s = 50\ V$

(c) KCL $1.25 = \dot{i}_{2\Omega} + 6.75 \Rightarrow \dot{i}_{2\Omega} = -5.5\ A$
 $\Rightarrow P_{2\Omega} = 2(\dot{i}_{2\Omega})^2 = 2(-5.5)^2 = 60.5\ W$

(d) KVL $-V_x - 2\dot{i}_{2\Omega} + 50 + 4(6.75) = 0 \Rightarrow V_x = 88\ V$

$\Rightarrow P_{I_s}^{\text{absorbed}} = -V_x I_s = -(88)(5) = -440\ W \Rightarrow P_{I_s}^{\text{deliver}} = 440\ W$