

EE 202 (122) – HW3 – Solution
Due Monday March 11, 2013
Dr. Abdallah Al-Ahmari

Question 1:

For the circuit shown in Figure 1, use source transformation to find the current i_o .


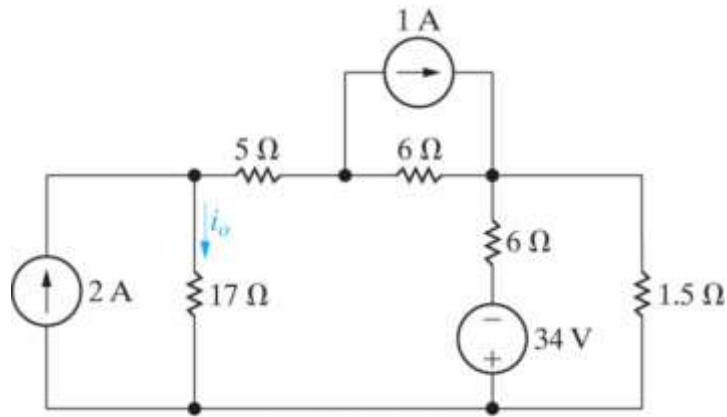



Figure 1

Solution:


a) Two source transformations to get:

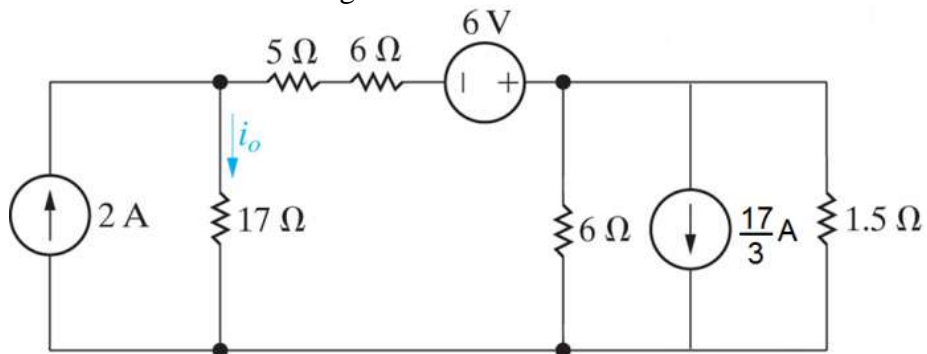

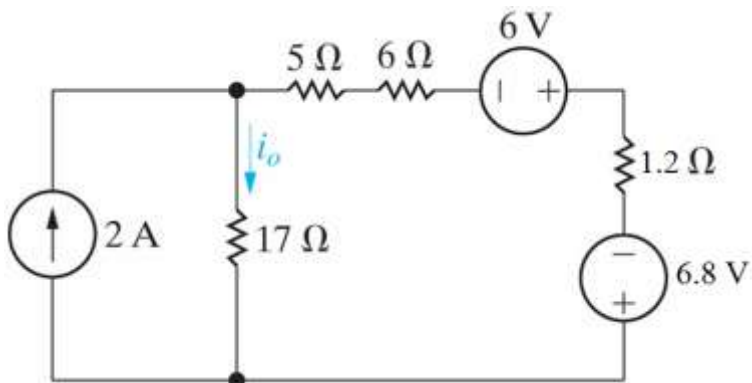
b) Combine two parallel resistors and one source transformation to get:



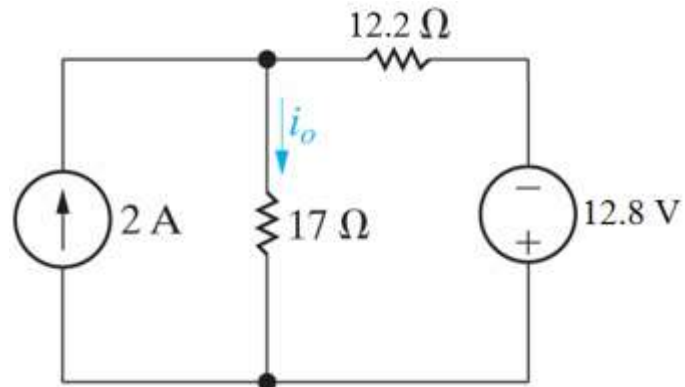
c) Combine three resistors and two voltage sources to get:



d) Once source transformation to get:

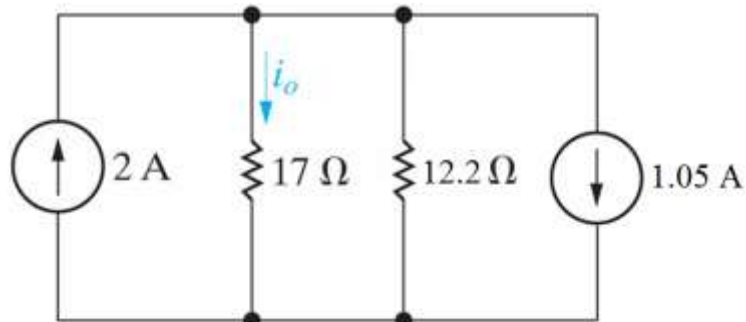

e) Assign a voltage v as follows:

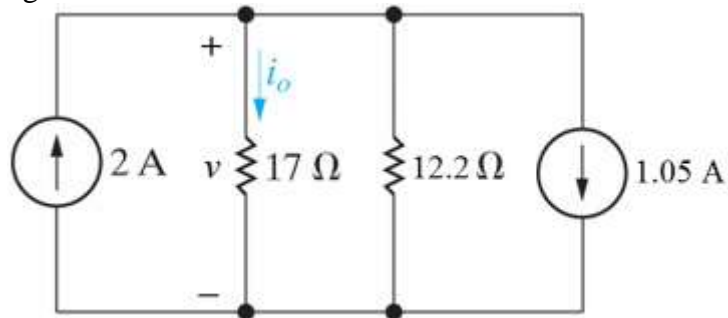

Apply KCL to get
 $-2 + v/17 + v/12.2 + 1.05 = 0$
 $v = 6.75 \text{ V}$


$i_o = 6.75 / 17 = 0.397 \text{ A}$

Question 2:


For the circuit shown in Figure 1, use source transformation to find the power dissipated by the 5 Ω resistor.

Solution:

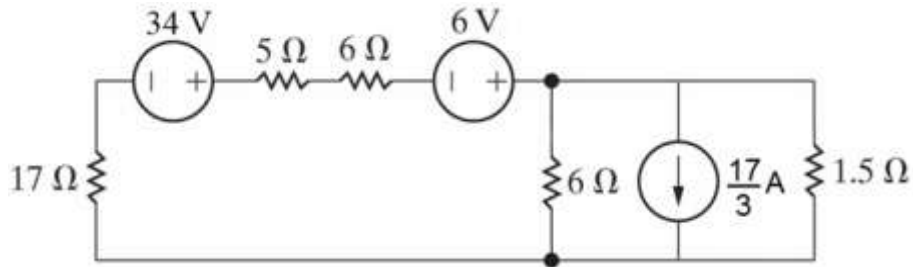
a) Three source transformations (right, left, and middle) to get:



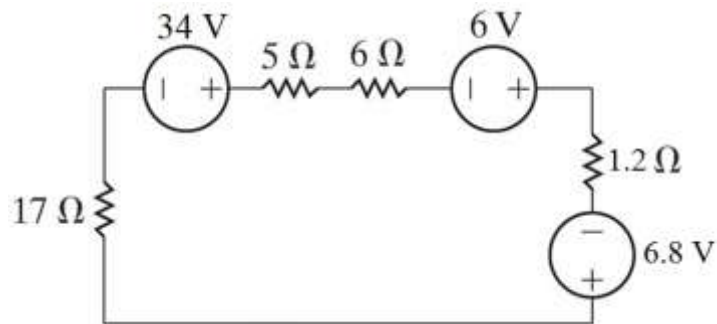b) Combine two resistors and one source transformation to get:



c) Mesh analysis

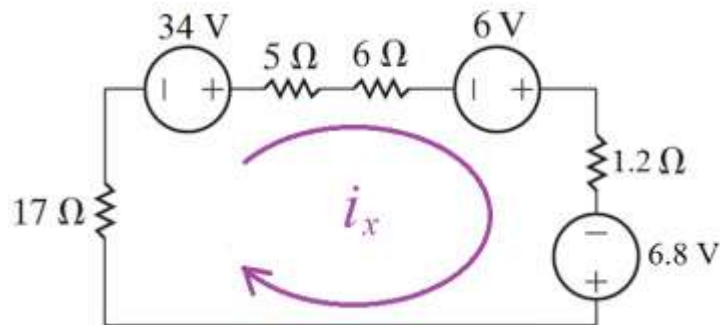

$$i_x = (34+6+6.8)/(17+5+6+1.2) = 1.603 \text{ A}$$

$$P_{5\text{-Ohms}} = 5 (1.603)^2 = 12.848 \text{ W absorbed.}$$

Question 3:

For the circuit shown in Figure 2, use source transformation to find the following:

- The voltage v_o .
- The power dissipated by the 10 Ω resistor.


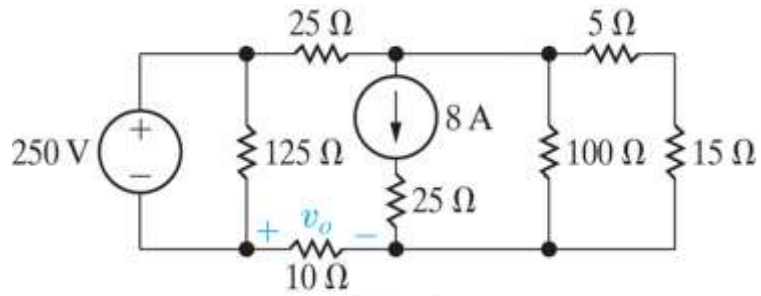



Figure 2

Solution:

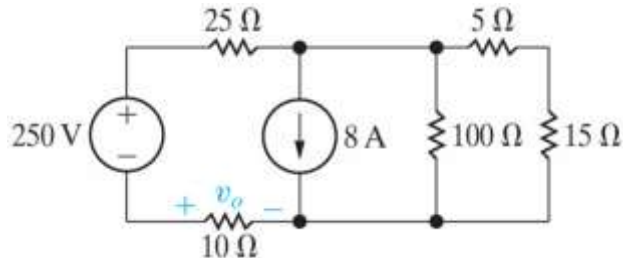
a) Remove 125 Ω and 25 Ω resistors as follows:




b) Combine two series resistors to get:

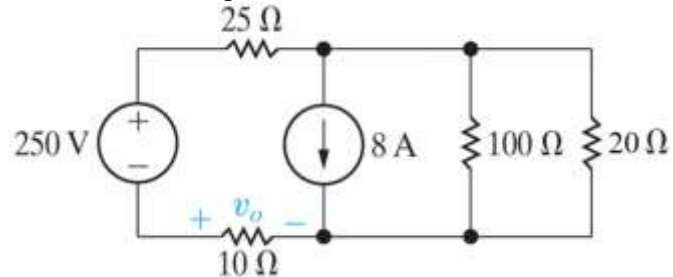

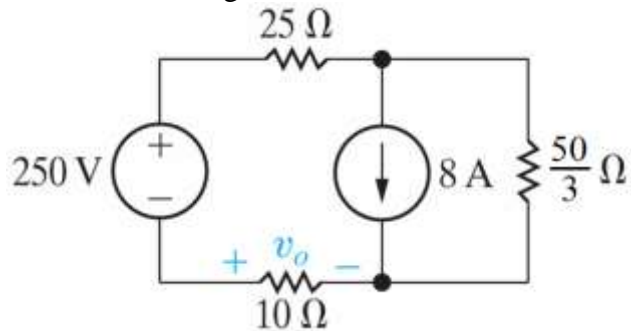
c) Combine two parallel resistors to get:



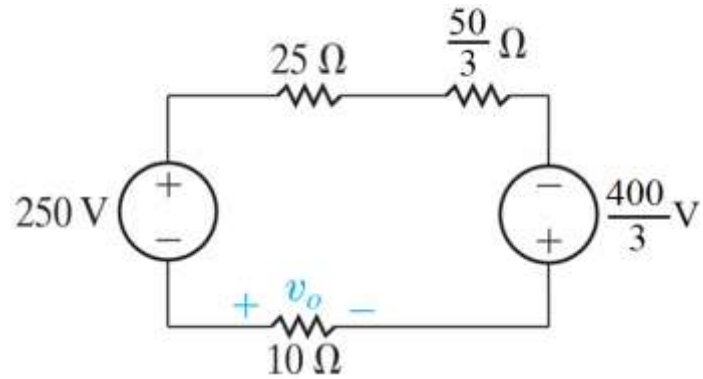d) One source transformation from the right to get:



e) Mesh analysis:

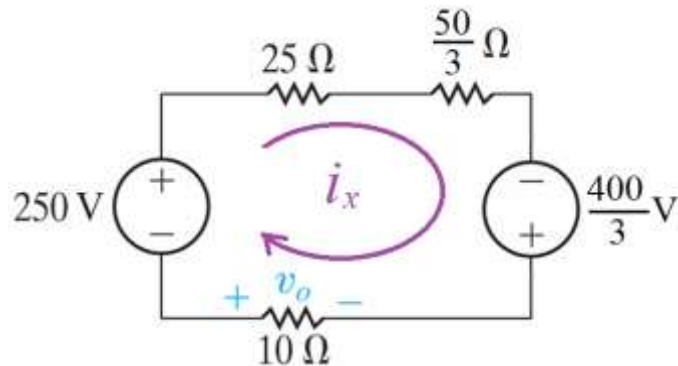

$$i_x = (250 + 400/3) / (25 + 50/3 + 10) = 7.42 \text{ A}$$

$$v_o = -10 i_x = -74.2 \text{ V}$$

$$P_{10\text{-Ohms}} = 10 (7.42)^2 = 550.564 \text{ W}$$

Question 4:

For the circuit shown in Figure 3, find the Thevenin equivalent circuit with respect to the terminals a,b.


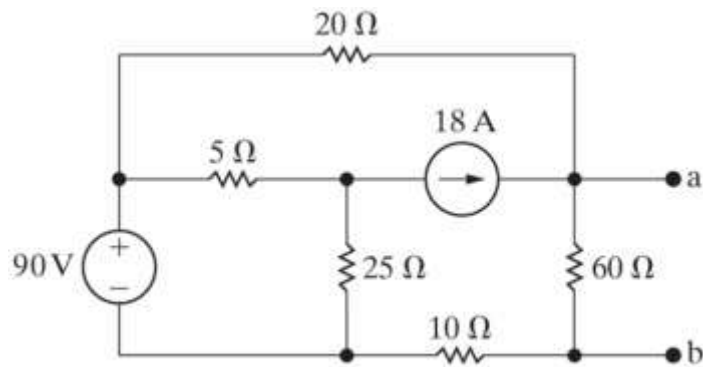


Figure 3

Solution:

Start with finding V_{oc} :

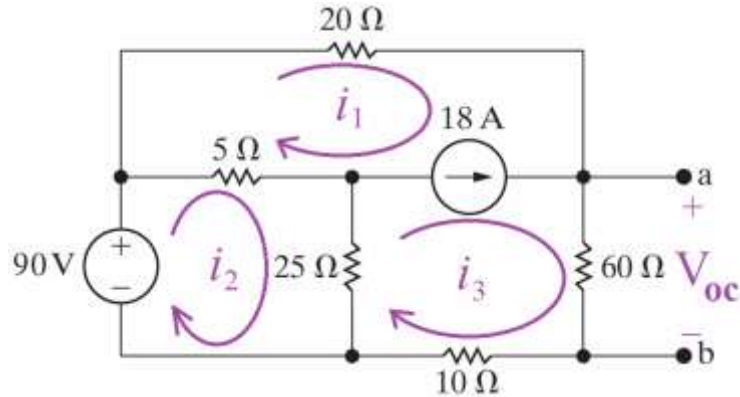

The mesh current equations are

$$-90 + 5(i_2 - i_1) + 25(i_2 - i_3) = 0$$


$$i_3 - i_1 = 18$$

Supermesh around M1 & M3:

$$20 i_1 + 60 i_3 + 10 i_3 + 25(i_3 - i_2) + 5(i_1 - i_2) = 0$$

$$V_{oc} = 60 i_3 = 60(5) = 300 \text{ V}$$

Then find R_{Th} as follows

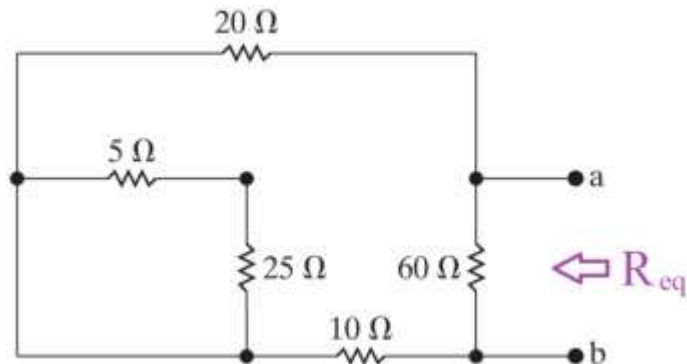

$$R_{Th} = R_{eq} = 60 // (20+10) = 20 \Omega$$

Question 5:

For the circuit shown in Figure 4,

- Find the open circuit voltage V_{oc} with respect to the terminals a, b. Use the mesh-current method.
- Find the short circuit current I_{sc} with respect to the terminals a, b. Use the mesh-current method.
- Use an external current source (1.0 A) to find the Thevenin resistor R_{th} . Use the mesh-current method.
- Find the Thevenin equivalent circuit with respect to the terminals a, b.
- Find the Norton equivalent circuit with respect to the terminals a, b.


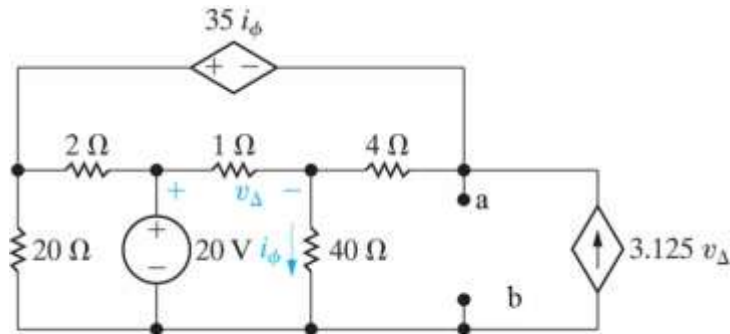


Figure 4

Solution:

a) Start with finding V_{oc} as follows:

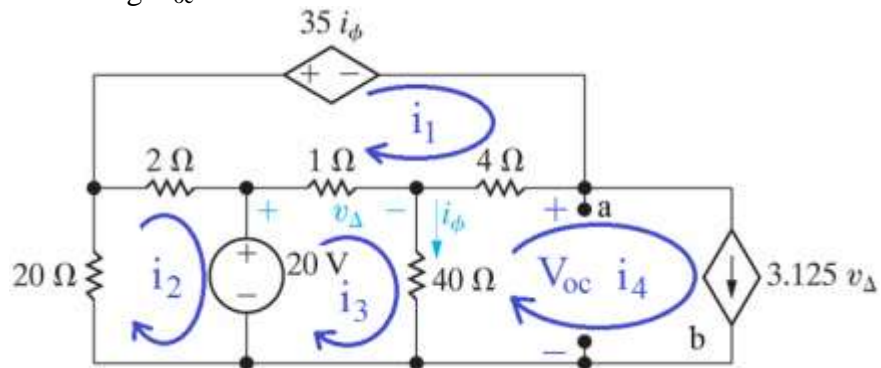

The mesh equations are:

$$35 i_{phi} + 4(i_1 - i_4) + (i_1 - i_3) + 2(i_1 - i_2) = 0$$

$$20 i_2 + 2(i_2 - i_1) + 20 = 0$$

$$-20 + (i_3 - i_1) + 40(i_3 - i_4) = 0$$

$$i_4 = 3.125 v_{delta}$$


Help equations:

$$i_{phi} = i_3 - i_4$$

$$v_{delta} = i_3 - i_1$$

$$V_{oc} = 4(i_1 - i_4) + 40(i_3 - i_4) = 21.08 \text{ V}$$

b) Finding I_{sc} as follows:

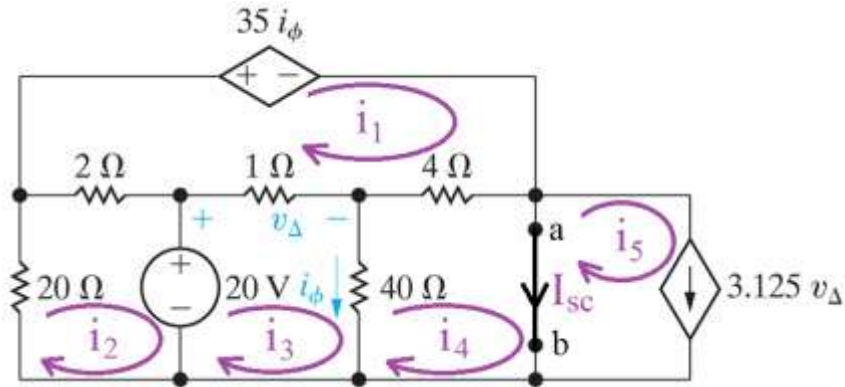

The mesh equations are:

$$35 i_{\text{phi}} + 4(i_1 - i_4) + (i_1 - i_3) + 2(i_1 - i_2) = 0$$

$$20 i_2 + 2(i_2 - i_1) + 20 = 0$$

$$-20 + (i_3 - i_1) + 40(i_3 - i_4) = 0$$

$$40(i_4 - i_3) + 4(i_4 - i_1) = 0$$

$$i_5 = 3.125 v_{\Delta}$$


Help equations:

$$i_{\text{phi}} = i_3 - i_4$$

$$v_{\Delta} = i_3 - i_1$$

$$I_{\text{sc}} = i_4 - i_5 = 13.8 \text{ A}$$

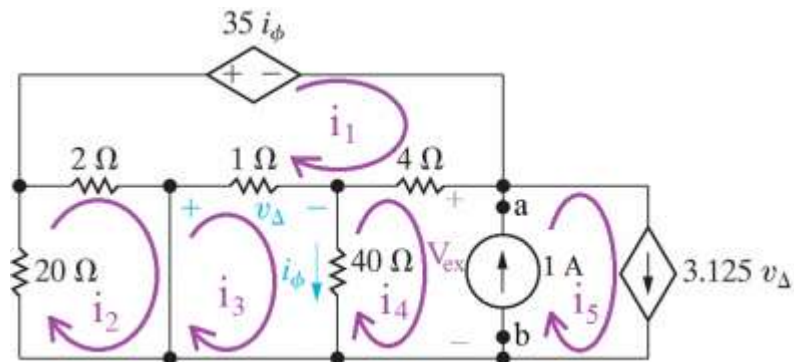c) Finding R_{Th} using an external current source



The mesh equations are:

$$35 i_{\text{phi}} + 4(i_1 - i_4) + (i_1 - i_3) + 2(i_1 - i_2) = 0$$

$$20 i_2 + 2(i_2 - i_1) = 0$$

$$(i_3 - i_1) + 40(i_3 - i_4) = 0$$

$$i_5 - i_4 = 1$$

$$i_5 = 3.125 v_{\Delta}$$

Help equations:


$$i_{\text{phi}} = i_3 - i_4$$

$$v_{\Delta} = i_3 - i_1$$

$$V_{ex} = 4(i_1 - i_4) + 40(i_3 - i_4) = 1.528 \text{ V}$$

$$R_{Th} = V_{ex}/1.0 = 1.528 \text{ } \Omega$$

d) Thevenin Equivalent Circuit

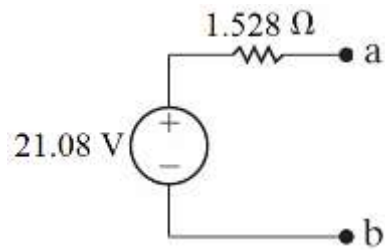

e) Norton Equivalent Circuit

