

Problem No 1 (40)

Q1 The total charge $q(t)$ entering the element **A** shown below (**Figure 1**)

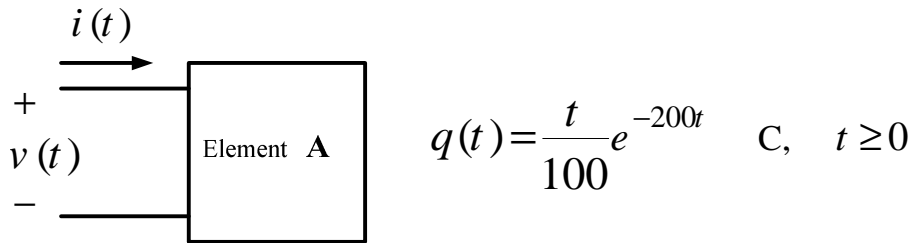


Figure 1

The current induced by the charge is equal to

(a) $i(t) = \frac{1}{100}e^{-200t} - 2te^{-200t}$ A, $t \geq 0$

(b) $i(t) = \frac{t}{2}e^{-200t}$ A, $t \geq 0$

(c) $i(t) = \frac{t}{100}e^{-200t}$ A, $t \geq 0$

(d) $i(t) = e^{-200t} + e^{200t}$ A, $t \geq 0$

Q2 For the circuit shown below (**Figure 2**)

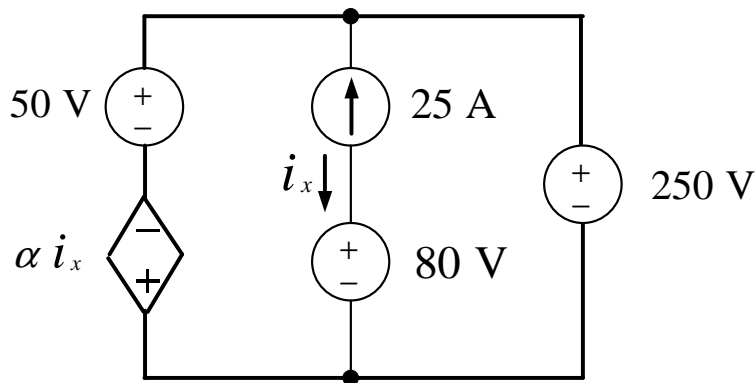


Figure 2

The value of α that will make the connection a valid connection

(a) $\alpha = 8$

(b) $\alpha = 12$

(c) $\alpha = -8$

(d) $\alpha = -12$

Q3 For the circuit shown below (**Figure 3**), if the voltage v across the resistor R is

$$\frac{V_s}{3} \leq v \leq \frac{V_s}{2}$$

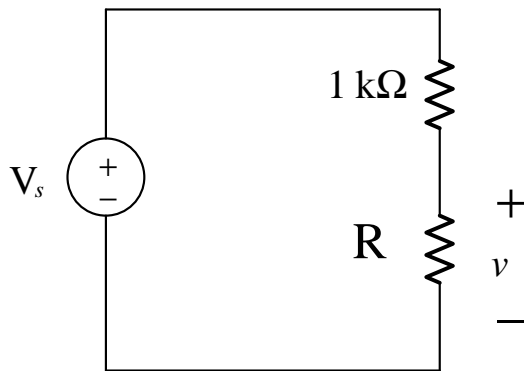


Figure 3

Then the choice of the resistor R is

- (a) $R = 500\Omega$ **(b)** $500\Omega \leq R \leq 1000\Omega$
(c) $100\Omega \leq R \leq 200\Omega$ (d) $R \geq 1000\Omega$

Q4 Two resistances R_1 and R_2 give combined resistance of 4.5Ω when in series and 1Ω when in parallel. The resistances are

- (a) $R_1=3\Omega$ and $R_2=6\Omega$ (b) $R_1=3\Omega$ and $R_2=9\Omega$
(c) $R_1=1.5\Omega$ and $R_2=3\Omega$ (d) $R_1=1.5\Omega$ and $R_2=0.5\Omega$

Q5 For the circuit shown below (Figure 4),

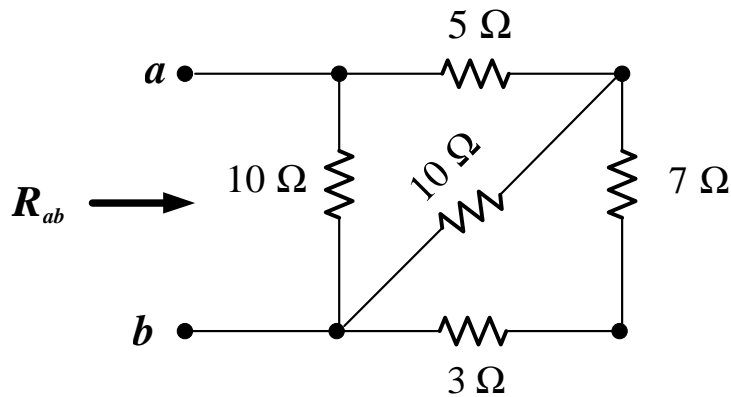


Figure 4

The equivalent resistant R_{ab} between a and b is

- (a) $R_{ab} = 35\ \Omega$ (b) $R_{ab} = 25\ \Omega$ (c) $R_{ab} = 15\ \Omega$ (d) $R_{ab} = 5\ \Omega$

Q6 For the circuit shown below (Figure 5),

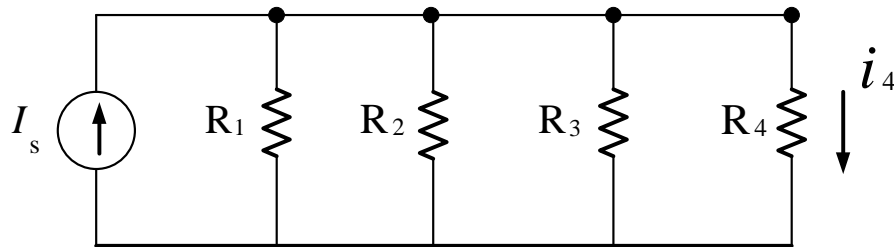


Figure 5

The current i_4 is

- (a) $i_4 = \frac{R_4}{R_1 + R_2 + R_3 + R_4} I_s$ (b) $i_4 = \frac{R_1 R_2 + R_1 R_3 + R_1 R_4}{R_1 + R_2 + R_3 + R_4} I_s$
 (c) $i_4 = \frac{R_1 R_2 R_3}{R_2 R_3 R_4 + R_1 R_3 R_4 + R_1 R_2 R_4 + R_1 R_2 R_3} I_s$ (d) $i_4 = \frac{R_1 R_2 R_3}{R_1 + R_2 + R_3 + R_4} I_s$

Q7

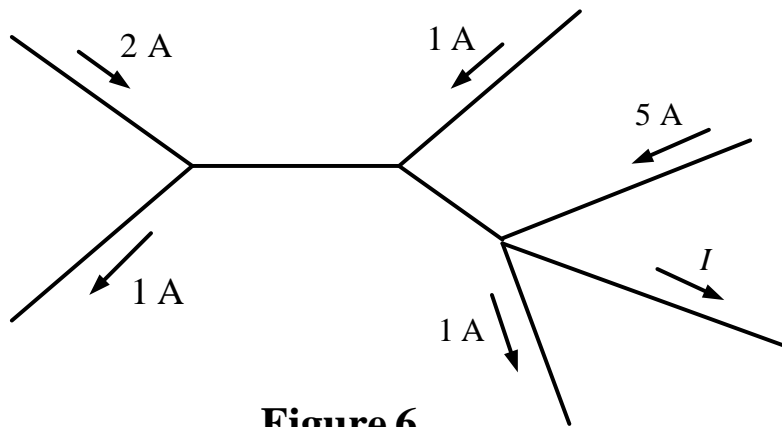


Figure 6

The current I in **Figure 6** is

- (a) $I=8\text{ A}$ (b) $I=7\text{ A}$ (c) $I=6\text{ A}$ (d) $I=5\text{ A}$

Q8 For the circuit shown below (**Figure 7**),

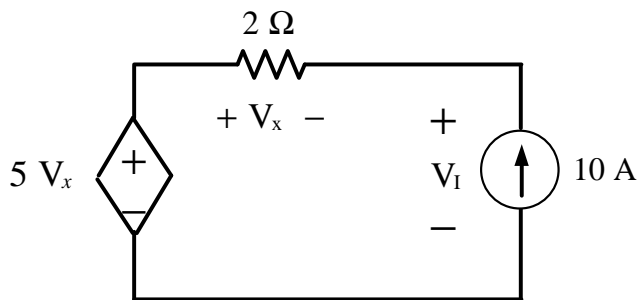


Figure 7

The voltage across the independent current source V_I is

- (a) $V_I = -80\text{ V}$ (b) $V_I = +80\text{ V}$ (c) $V_I = 120\text{ V}$ (d) $V_I = -120\text{ V}$

Q9 For the circuit shown below (**Figure 8**),

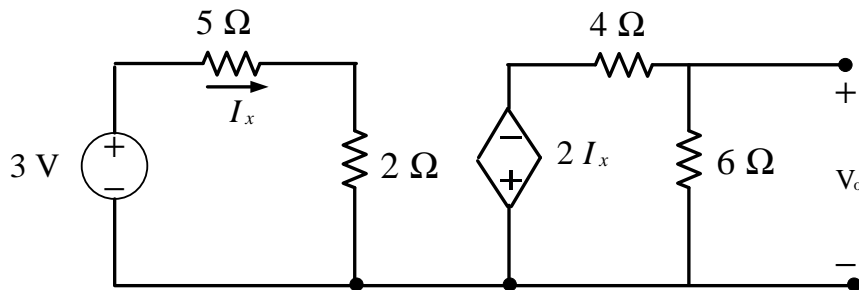


Figure 8

The voltage V_o is

- (a) $V_o = \frac{35}{18}$ V (b) $V_o = -\frac{35}{18}$ V (c) $V_o = \frac{36}{70}$ V (d) $V_o = -\frac{36}{70}$ V

Q10 For the circuit shown below (**Figure 9**),

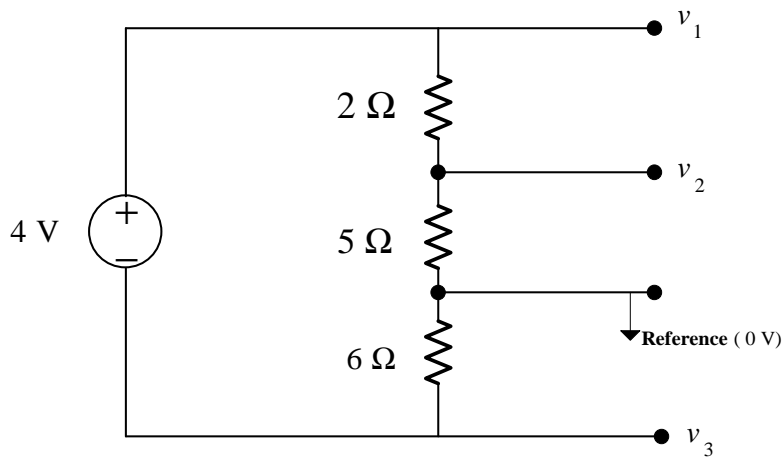


Figure 9

The nodes voltages v_1 , v_2 , v_3 with respect to the reference voltage are


$$(a) \quad v_1 = \frac{8}{13} \quad v_2 = \frac{20}{13} \quad v_3 = \frac{24}{13}$$

$$(b) \quad v_1 = \frac{8}{13} \quad v_2 = \frac{20}{13} \quad v_3 = -\frac{24}{13}$$

$$(c) \quad v_1 = \frac{28}{13} \quad v_2 = \frac{20}{13} \quad v_3 = \frac{24}{13}$$

$$(d) \quad v_1 = \frac{28}{13} \quad v_2 = \frac{20}{13} \quad v_3 = -\frac{24}{13}$$

Problem No 2 (20)

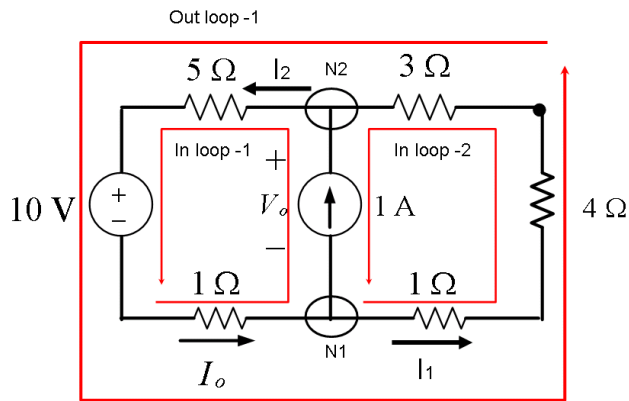

Let the circuit as shown above. Using directly KVL, KCL and ohm's law

find V_o and I_o ? (**Do Not Use Node Voltage Method or Mesh Method**)

KCL at Node-1: $-I_1 + I_o - 1 = 0 \Rightarrow I_1 = I_o - 1$

KCL at Node-2: $-I_2 + 1 + I_1 = -I_2 + 1 + (I_o - 1) = 0 \Rightarrow I_2 = I_o$

KVL Out loop -1: $10 + I_o + 8 \cdot I_1 + 5 \cdot I_2 = 0$
 $+10 + I_o + 8 \cdot (I_o - 1) + 5 \cdot I_o = 14 \cdot I_o + 2 = 0$
 $\Rightarrow I_o = -1/7$


KVL in Loop-1: $+10 + I_o - V_o + 5 \cdot I_2 = 0 \Rightarrow +10 + I_o - V_o + 5 \cdot I_o = 0$

$$V_o = 64/7$$

Or

KVL in Loop-2: $V_o + 8 \cdot I_1 = 0 \Rightarrow V_o + 8 \cdot (I_o - 1) = 0$

Problem No 3 (25)

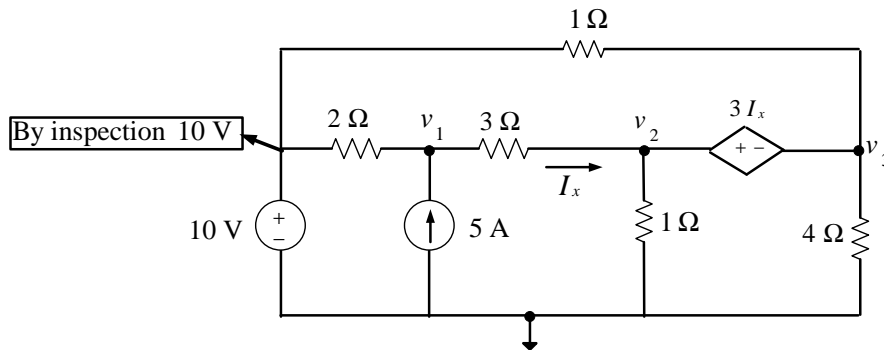

For the circuit shown above find the nodal equations necessary to solve for the node voltages v_1 , v_2 , v_3 and put your results in the matrix form as

$$\begin{bmatrix} \\ \\ \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} \\ \\ \end{bmatrix}$$

(DO NOT SOLVE THE SYTEM OF EQUATIONS)

Solution

$$\text{KCL at } v_1 \Rightarrow \frac{v_1 - 10}{2} - 5 + \frac{v_1 - v_2}{3} = 0$$

$$\Rightarrow 5v_1 - 2v_2 = 60 \quad \text{-----(1)}$$

$$\text{KCL at Supernode} \Rightarrow \frac{v_2 - v_1}{3} + \frac{v_2}{1} + \frac{v_3}{4} + \frac{v_3 - 10}{1} = 0$$


$$\Rightarrow -4v_1 + 16v_2 + 15v_3 = 120 \quad \text{-----(2)}$$

$$\text{Voltage Restriction} \Rightarrow v_2 - v_3 = 3I_x = 3 \frac{v_1 - v_2}{3} = v_1 - v_2$$

$$\Rightarrow -v_1 + 2v_2 - v_3 = 0 \quad \text{-----(3)}$$

$$\Rightarrow \begin{bmatrix} 5 & -2 & 0 \\ -4 & 16 & 15 \\ -1 & 2 & -1 \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \\ v_3 \end{bmatrix} = \begin{bmatrix} 60 \\ 120 \\ 0 \end{bmatrix}$$

Problem No 4 (15)

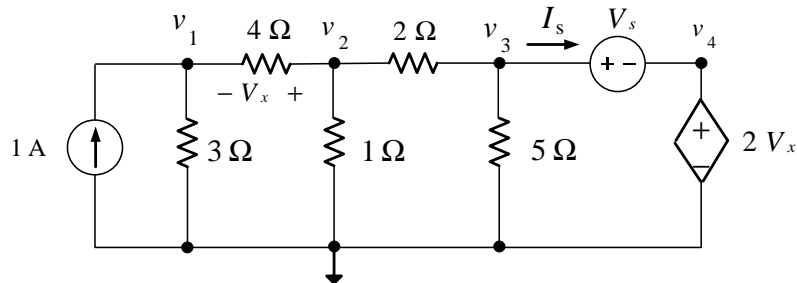

For the circuit shown above the nod voltages are given as :

$$v_1 = 1.5 \text{ V} \quad v_2 = -0.5 \text{ V} \quad v_3 = -2.5 \text{ V}$$

- (a) Find the node voltage v_4 ?
- (b) The power delivered by the independent current source ?
- (c) The power delivered by the independent voltage source ?

Solution

(a) $V_4 = 2V_x = 2(v_2 - v_1) = 2(-0.5 - 1.5) = -4 \text{ V}$

(b) $P_{1A}^{\text{absorbed}} = -V_I(1)$

$\Rightarrow P_{1A}^{\text{delivered}} = V_I(1) = v_1(1) = (1.5)(1) = 1.5 \text{ W}$

(c) $P_{V_s}^{\text{absorbed}} = V_s I_s$

$\Rightarrow P_{1A}^{\text{delivered}} = -V_s I_s$

$$V_s = v_3 - v_4 = -2.5 - (-4) = 1.5 \text{ V}$$

$$I_s = \frac{v_2 - v_3}{2} + \frac{0 - v_3}{5} = \frac{-0.5 + 2.5}{2} + \frac{2.5}{5} = 1.5 \text{ A}$$

$\Rightarrow P_{1A}^{\text{delivered}} = -(1.5)(1.5) = -2.25 \text{ W}$