

EE 202-131

HW3

Adil S. Balghonaim

Due Tuesday Oct 22

Problem 1 4.34

Note Find the total power developed mean find the total (sum) power delivered (generated)

Problem 2 4.37

Problem 3 4.50

Note The branch currents $i_a - i_e$ mean find the currents i_a, i_b, i_c, i_d, i_e

Problem 4 4.59

Problem 5 4.60