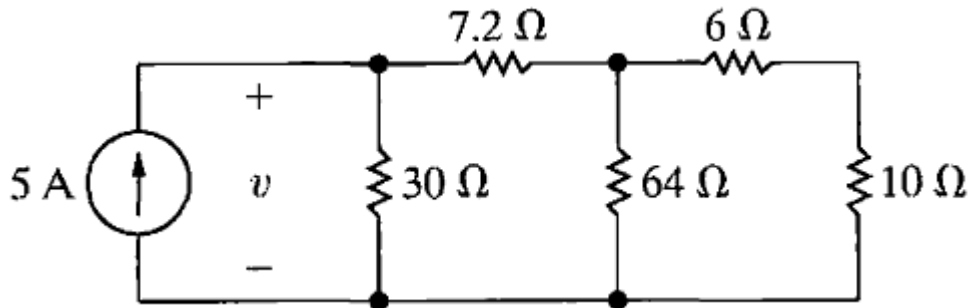


EE 202-132

HW2 (due Sunday 23/2/ 2014)


P1



for the circuit shown:


- (a) Use the combining resistor techniques to find the voltage v
- (b) the power delivered to the circuit by the current source
- (c) the power dissipated in the $10\ \Omega$

P2

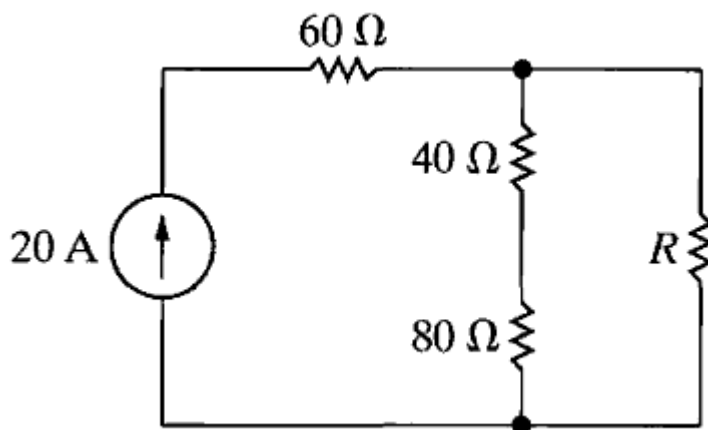


for the circuit shown:

- (a) Use the current division techniques to find the resistor R that will cause a 4 A to flow through the $80\ \Omega$ resistor
- (b) the power dissipated in the resistor R of part (a)
- (c) the power generated by the current source for the value of R part (a)

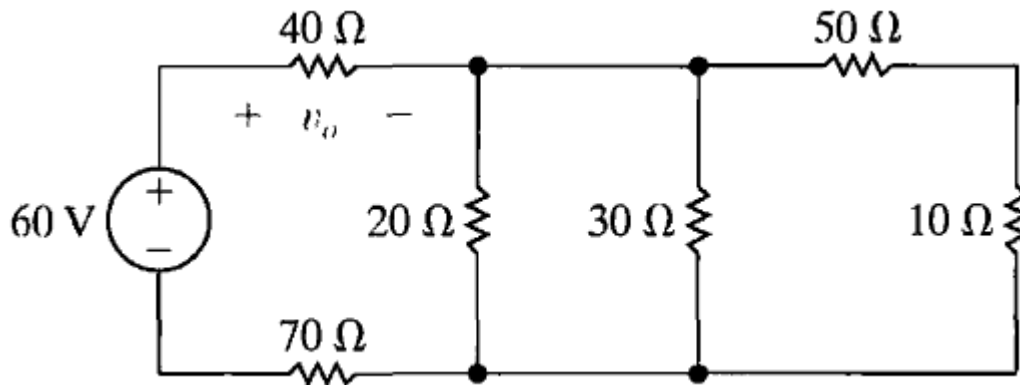P3

for the circuit shown to find the followings:

- (a) Use the **voltage division techniques** to find the voltage v_o
- (b) Use the **current division techniques** to find the current through the $30\ \Omega$
- (c) How much power is absorbed by the $50\ \Omega$

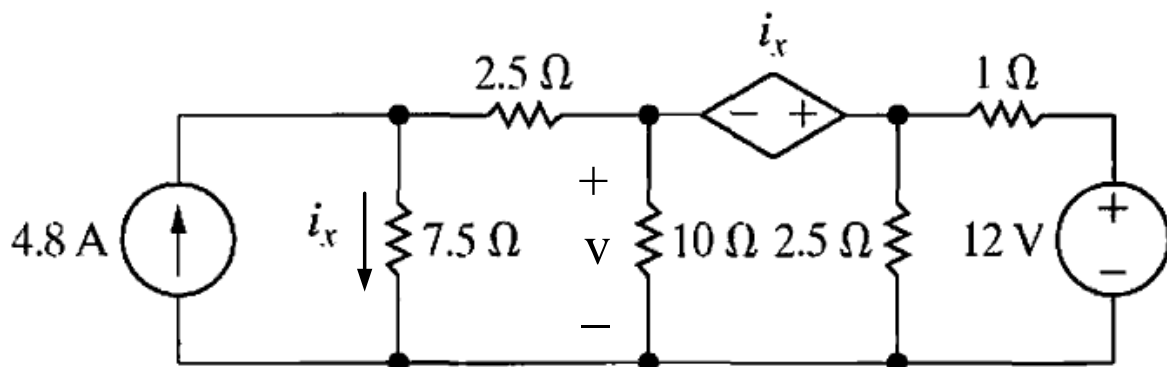P4

for the circuit shown, use the **node-voltage method** to find the voltage V