

EE 202-Winter 2013-2014 (132)

HW5 Solution

Prepared By: Dr. Mohammad S. Sharawi

Due 13/4/2014

Q1 A voltage of $60 \cos 4\pi t$ V appears across the terminals of a 3-mF capacitor. Calculate the current through the capacitor and the energy stored in it from $t = 0$ to $t = 0.125$ s.

$$i = C \frac{dv}{dt} = 3 \times 10^{-3} \times 60(4\pi)(-\sin 4\pi t)$$

$$= \underline{-0.72 \pi \sin(4\pi t) \text{ A}}$$

$$P = vi = 60(-0.72)\pi \cos 4\pi t \sin(4\pi t) = -21.6\pi \sin(8\pi t) \text{ W}$$

$$W = \int_0^t p dt = -\int_0^{\frac{1}{8}} 21.6\pi \sin(8\pi t) dt$$

$$= \frac{21.6\pi}{8\pi} \cos 8\pi \Big|_0^{\frac{1}{8}} = \underline{-5.4 \text{ J}}$$

Q2 Find the equivalent capacitance between terminals a and b in the circuit of Fig. 1. All capacitances are in μF .


We combine 10-, 20-, and 30- μF capacitors in parallel to get 60 μF . The 60- μF capacitor in series with another 60- μF capacitor gives 30 μF .

$$30 + 50 = 80 \mu\text{F}, \quad 80 + 40 = 120 \mu\text{F}$$

120- μF capacitor in series with 80 μF gives $(80 \times 120) / 200 = 48$

$$48 + 12 = 60$$

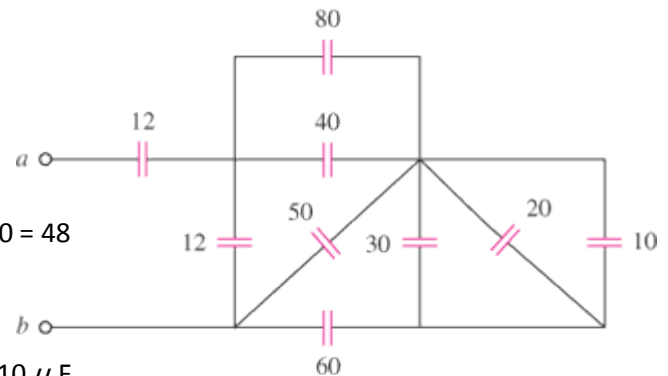60- μF capacitor in series with 12 μF gives $(60 \times 12) / 72 = \underline{10 \mu\text{F}}$



Q3 In the circuit in Fig. 2, let $i_s = 30e^{-2t}$ mA and $v_1(0) = 50$ V, $v_2(0) = 20$ V. Determine:
 (a) $v_1(t)$ and $v_2(t)$, (b) the energy in each capacitor at $t = 0.5$ s.

(a) $C_{eq} = (12 \times 60) / 72 = 10 \mu F$

$$v_1 = \frac{10^{-3}}{12 \times 10^{-6}} \int_0^t 30e^{-2t} dt + v_1(0) = \frac{-1250e^{-2t}}{12} \Big|_0^t + 50 = \frac{-1250e^{-2t}}{12} + 1300V$$

$$v_2 = \frac{10^{-3}}{60 \times 10^{-6}} \int_0^t 30e^{-2t} dt + v_2(0) = \frac{250e^{-2t}}{60} \Big|_0^t + 20 = \frac{-250e^{-2t}}{60} + 270V$$


(b) At $t=0.5s$,

$$v_1 = -1250e^{-1} + 1300 = 840.2, \quad v_2 = -250e^{-1} + 270 = 178.03$$

$$w_{12\mu F} = \frac{1}{2} \times 12 \times 10^{-6} \times (840.15)^2 = \underline{4.235 J}$$

$$w_{20\mu F} = \frac{1}{2} \times 20 \times 10^{-6} \times (178.03)^2 = \underline{0.3169 J}$$
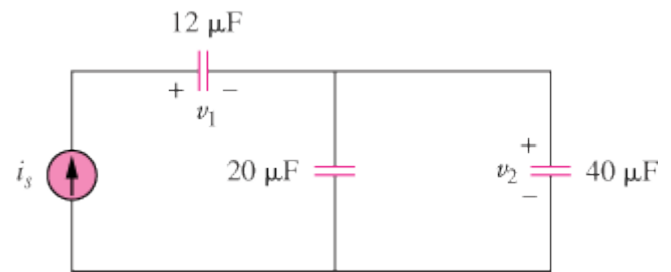
$$w_{40\mu F} = \frac{1}{2} \times 40 \times 10^{-6} \times (178.03)^2 = \underline{0.6339 J}$$




Q4 Determine L_{eq} at terminals $a-b$ of the circuit in Fig. 3.

$$\frac{1}{L} = \frac{1}{60} + \frac{1}{20} + \frac{1}{30} = \frac{1}{10} \quad L = 10 \text{ mH}$$

$$L_{eq} = 10 \parallel (25 + 10) = \frac{10 \times 35}{45}$$

$$= \underline{7.778 \text{ mH}}$$

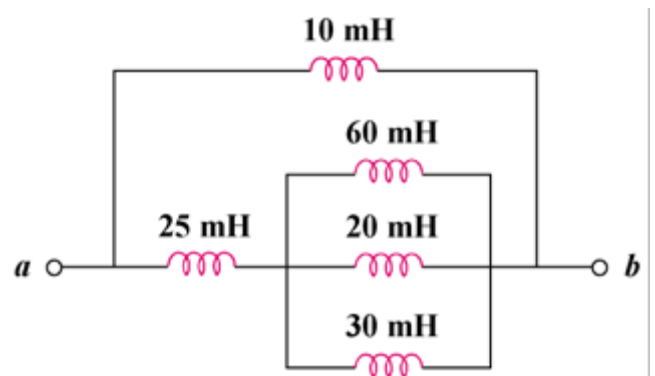

Q5 Determine L_{eq} that may be used to represent the inductive network of Fig. 4 at the terminals.

$$\text{Let } v = L_{eq} \frac{di}{dt} \quad (1)$$

$$v = v_1 + v_2 = 4 \frac{di}{dt} + v_2$$

(2)

$$i = i_1 + i_2 \longrightarrow i_2 = i - i_1 \quad (3)$$

$$v_2 = 3 \frac{di_1}{dt} \text{ or } \frac{di_1}{dt} = \frac{v_2}{3} \quad (4)$$

and

$$-v_2 + 2 \frac{di}{dt} + 5 \frac{di_2}{dt} = 0$$

$$v_2 = 2 \frac{di}{dt} + 5 \frac{di_2}{dt} \quad (5)$$

Incorporating (3) and (4) into (5),

$$v_2 = 2 \frac{di}{dt} + 5 \frac{di}{dt} - 5 \frac{di_1}{dt} = 7 \frac{di}{dt} - 5 \frac{v_2}{3}$$

$$v_2 \left(1 + \frac{5}{3} \right) = 7 \frac{di}{dt}$$


$$v_2 = \frac{21}{8} \frac{di}{dt}$$

Substituting this into (2) gives


$$v = 4 \frac{di}{dt} + \frac{21}{8} \frac{di}{dt} = \frac{53}{8} \frac{di}{dt}$$

Comparing this with (1),
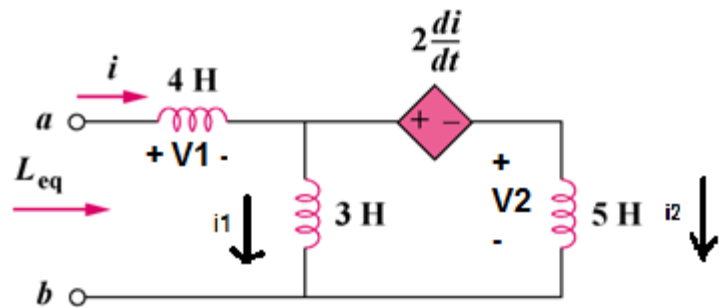
$$L_{eq} = \frac{53}{8} = \underline{\underline{6.625 \text{ H}}}$$



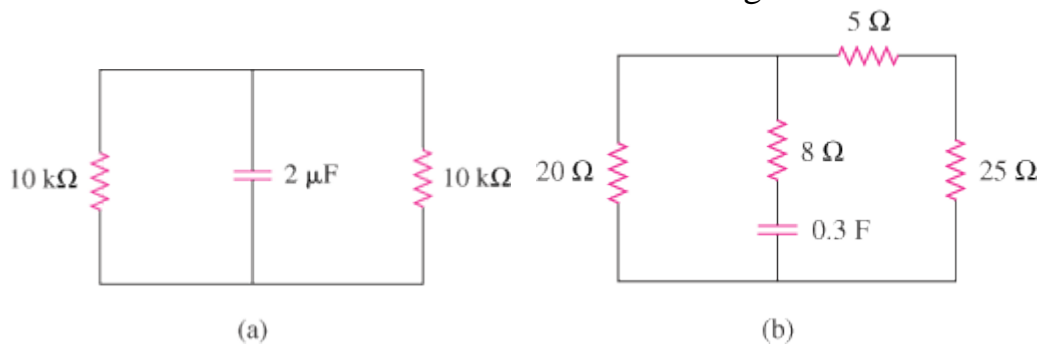Q6 Find the time constant of each of the circuits in Fig. 5.



(a) $R_{Th} = 10 // 10 = 5k\Omega$, $\tau = R_{Th}C = 5 \times 10^3 \times 2 \times 10^{-6} = \underline{10 \text{ ms}}$

(b) $R_{Th} = 20 // (5 + 25) + 8 = 20\Omega$, $\tau = R_{Th}C = 20 \times 0.3 = \underline{6 \text{ s}}$


Q7 In the circuit of Fig. 6, $v(0) = 20 \text{ V}$. Find $v(t)$ for $t > 0$.

$$v(t) = v(0)e^{-t/\tau}, \quad \tau = R_{eq}C$$

$$R_{eq} = 2 + (8 // 8) + (6 // 3) = 2 + 4 + 2 = 8 \Omega$$

$$\tau = R_{eq}C = (0.25)(8) = 2$$
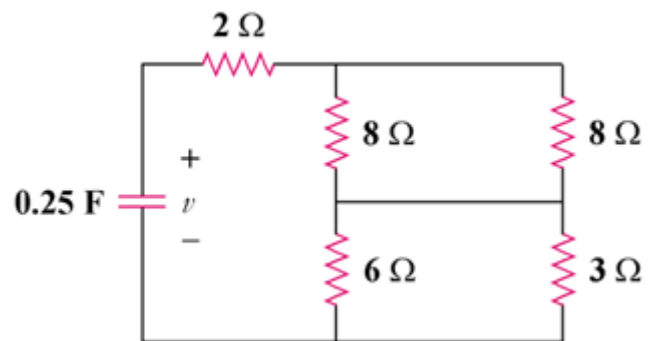
$$v(t) = \underline{20e^{-t/2} \text{ V}}$$



Q8 Consider the circuit of Fig. 7. Find $v_o(t)$ if $i(0) = 2$ A and $v(t) = 0$.

$$i(t) = i(0)e^{-t/\tau}, \quad \tau = \frac{L}{R_{eq}} = \frac{1/4}{4} = \frac{1}{16}$$

$$i(t) = 2e^{-16t}$$

$$v_o(t) = 3i + L \frac{di}{dt} = 6e^{-16t} + (1/4)(-16)2e^{-16t}$$

$$v_o(t) = \underline{-2e^{-16t} \text{ V}}$$

