

EE 202-132
HW3 (Due Sunday, March 09 - 2014)
Prepared by: Dr. Kamal Harb

P1.

For the circuit shown in Figure 1, use the mesh-current method to calculate:

- a)- The current in all the circuit.
- b)- The power of each element in the circuit.

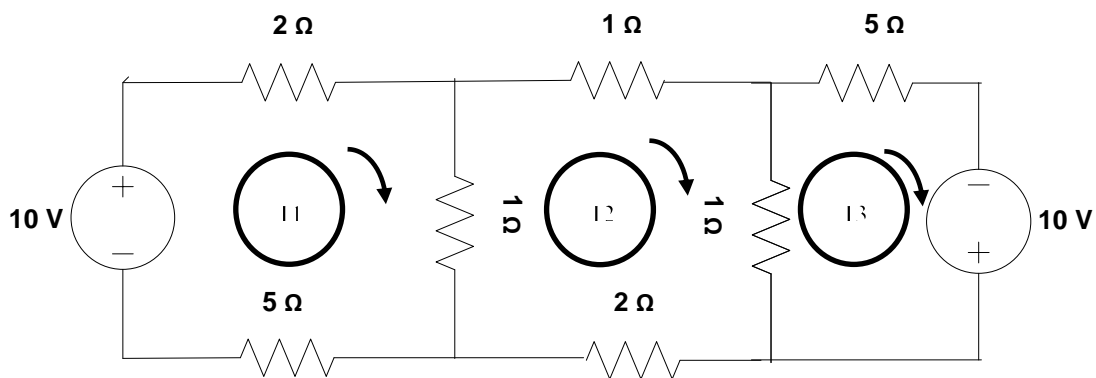


Figure 1.

Solution:

$$10 = 8 I_1 - I_2 - 0$$

$$0 = -I_1 + 5I_2 - I_3$$

$$10 = 0 - I_2 + 6I_3$$

$$I_1 = 1.32 \text{ A}; \quad I_2 = 0.619 \text{ A}; \quad I_3 = 1.77 \text{ A};$$

$$P(10V) = I_1 \cdot V = 1500/113;$$

$$P'(10V) = I_3 \cdot V = 2000/113;$$

$$P(R_x) = (I_x)^2 \cdot R_x \text{ (For each individual resistance)}$$

$$P(R = 1) = (I_1 - I_2)^2 \cdot (1)$$

$$P(R = 1) = (I_2 - I_3)^2 \cdot (1)$$

P2.

For the circuit shown in Figure 2, use the node-voltage method to calculate the power in the voltage sources.

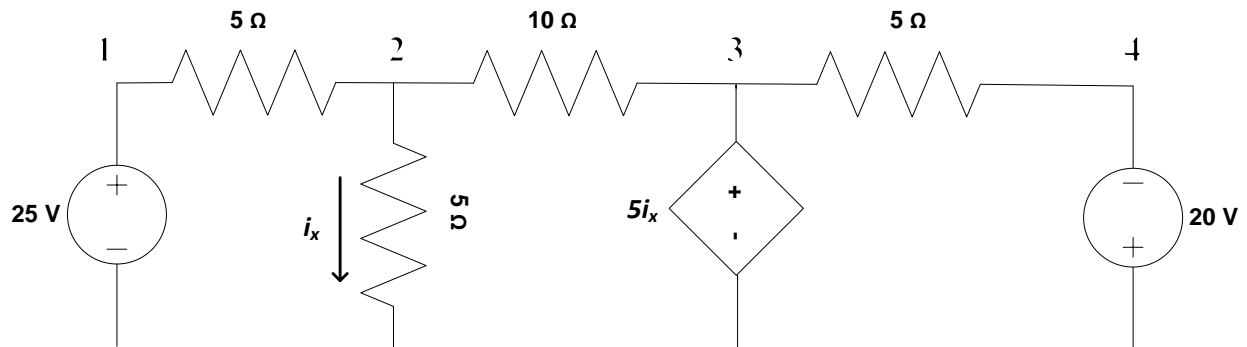


Figure 2.

$$V_1 = 25; V_4 = -20V; V_3 = 5 i_x = 5 (V_2/5) = V_2;$$

KCL at node 2:

$$- V_1(1/5) + V_2 (1/5 + 1/5 + 1/10) - V_3 (1/10) = 0; \quad \textcircled{1}$$

$$\text{Sub. } V_1 \text{ and } V_3 \Rightarrow V_2 = 12.5 \text{ v.}$$

$$I_{25} = (V_1 - V_2)/5 = 2.5 \text{ v.} \Rightarrow P_{25} = I.V = 2.5 \cdot 25 = 62.5 \text{ w;}$$

$$I_{20} = (V_3 - V_4)/5 = 6.5 \text{ v.} \Rightarrow P_{20} = I.V = 6.5 \cdot 20 = 130 \text{ w;}$$

P3.

For the circuit shown in Figure 3, use the mesh-current method to calculate:

a)- The current i_z

b)- The power in the circuit.

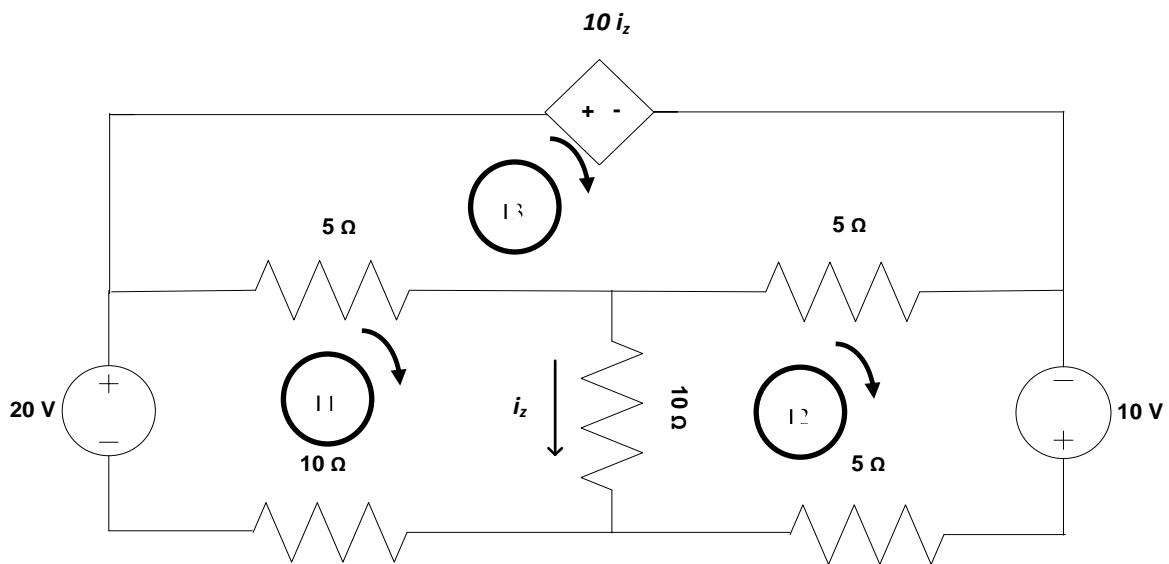


Figure 4.

Solution:

$$I_z = (I_1 - I_2);$$

$$20 = I_1 (25) - I_2 (10) - I_3 (5)$$

$$10 = -I_1 (10) + I_2 (20) - I_3 (5)$$





$$-10 (I_1 - I_2) = -I_1 (5) - I_2 (5) + I_3 (10)$$



$$I_1 = 2 \text{ A}; I_2 = 2 \text{ A}; I_3 = 2 \text{ A};$$

$$P_{20} = I_1 (20) = 40 \text{ W}, P_{10} = I_2 (10) = 20 \text{ W} \text{ and } P_{10ix} = 0 \text{ W}.$$

P4.

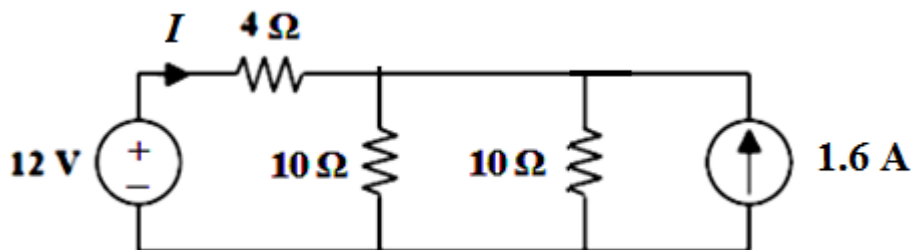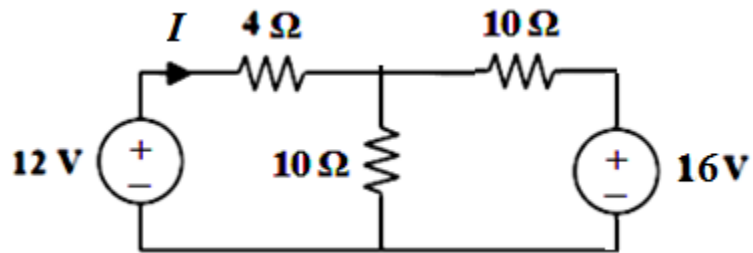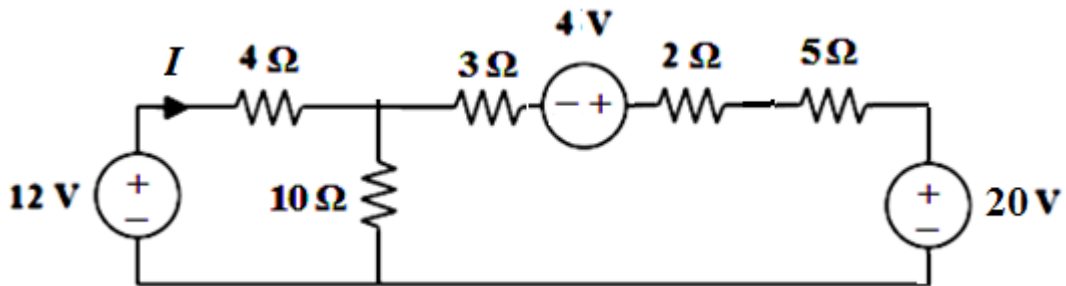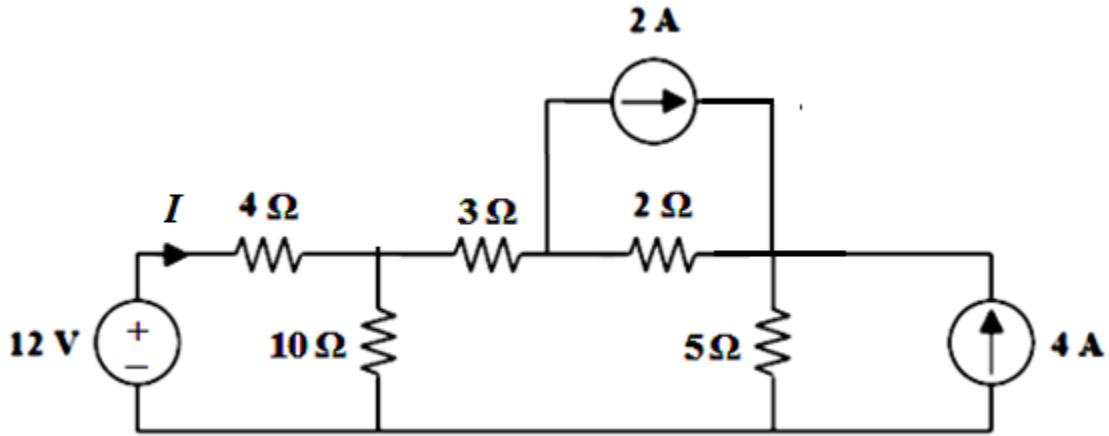Use source transformations to reduce the circuit shown to a single loop, and then find the current I . Draw a circuit for each step you take.



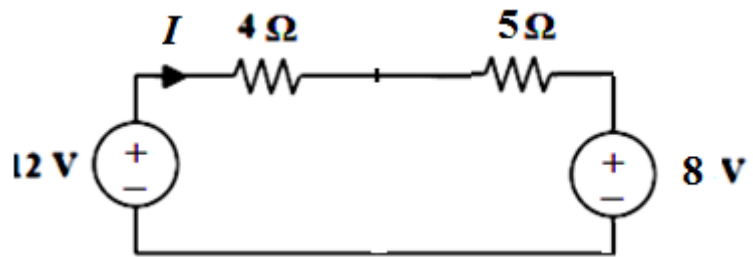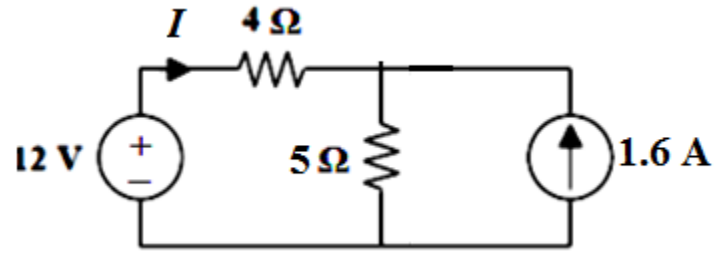

$$I = (12 - 8)/9 = 4/9 \text{ A.}$$