

$$\text{P 9.8} \quad V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^{T/2} V_m^2 \sin^2 \frac{2\pi}{T} t \, dt}$$

$$\int_0^{T/2} V_m^2 \sin^2 \left(\frac{2\pi}{T} t \right) \, dt = \frac{V_m^2}{2} \int_0^{T/2} \left(1 - \cos \frac{4\pi}{T} t \right) \, dt = \frac{V_m^2 T}{4}$$

$$\text{Therefore} \quad V_{\text{rms}} = \sqrt{\frac{1}{T} \frac{V_m^2 T}{4}} = \frac{V_m}{2}$$

$$\text{P 9.12 [a]} \quad V_g = 300/\underline{78^\circ}; \quad I_g = 6/\underline{33^\circ}$$

$$\therefore Z = \frac{V_g}{I_g} = \frac{300/\underline{78^\circ}}{6/\underline{33^\circ}} = 50/\underline{45^\circ} \, \Omega$$

[b] i_g lags v_g by 45° :

$$2\pi f = 5000\pi; \quad f = 2500 \text{ Hz}; \quad T = 1/f = 400 \, \mu\text{s}$$

$$\therefore i_g \text{ lags } v_g \text{ by } \frac{45^\circ}{360^\circ} (400 \, \mu\text{s}) = 50 \, \mu\text{s}$$

P 9.13 [a] $\omega = 2\pi f = 160\pi \times 10^3 = 502.65 \text{ krad/s} = 502,654.82 \text{ rad/s}$

[b] $\mathbf{I} = \frac{25 \times 10^{-3} \angle 0^\circ}{1/j\omega C} = j\omega C(25 \times 10^{-3}) \angle 0^\circ = 25 \times 10^{-3} \omega C \angle 90^\circ$

$$\therefore \theta_i = 90^\circ$$

[c] $628.32 \times 10^{-6} = 25 \times 10^{-3} \omega C$

$$\frac{1}{\omega C} = \frac{25 \times 10^{-3}}{628.32 \times 10^{-6}} = 39.79 \Omega, \quad \therefore X_C = -39.79 \Omega$$

[d] $C = \frac{1}{39.79(\omega)} = \frac{1}{(39.79)(160\pi \times 10^3)}$

$$C = 0.05 \times 10^{-6} = 0.05 \mu\text{F}$$

[e] $Z_c = j \left(\frac{-1}{\omega C} \right) = -j39.79 \Omega$

P 9.18 [a] $Y_2 = \frac{1}{R_2} - \frac{j}{\omega L_2}$

$$Y_1 = \frac{1}{R_1 + j\omega L_1} = \frac{R_1 - j\omega L_1}{R_1^2 + \omega^2 L_1^2}$$


Therefore $Y_2 = Y_1$ when

$$R_2 = \frac{R_1^2 + \omega^2 L_1^2}{R_1} \quad \text{and} \quad L_2 = \frac{R_1^2 + \omega^2 L_1^2}{\omega^2 L_1}$$

[b] $R_2 = \frac{8000^2 + 1000^2(4)^2}{8000} = 10 \text{ k}\Omega$

$$L_2 = \frac{8000^2 + 1000^2(4)^2}{1000^2(4)} = 20 \text{ H}$$

P 9.33 [a]

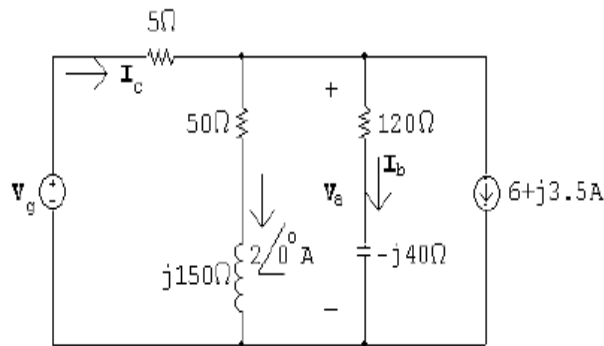

$$V_a = (50 + j150)(2/0^\circ) = 100 + j300 \text{ V}$$

$$I_b = \frac{100 + j300}{120 - j40} = j2.5 \text{ A}$$

$$I_c = 2/0^\circ + j2.5 + 6 + j3.5 = 8 + j6 \text{ A}$$

$$V_g = 5I_c + V_a = 5(8 + j6) + 100 + j300 = 140 + j330 \text{ V}$$

[b] $i_b = 2.5 \cos(800t + 90^\circ) \text{ A}$

$$i_c = 10 \cos(800t + 36.87^\circ) \text{ A}$$


$$v_g = 358.47 \cos(800t + 67.01^\circ) \text{ V}$$

$$I_b = I_1 - j5 = (2.4 + j1.8) - j5 = 2.4 - j3.2 \text{ A}$$

$$V_Z = -j5I_2 + (4 - j3)I_1 = -j5(2.4 - j3.2) + (4 - j3)(2.4 + j1.8) = -1 - j12 \text{ V}$$

$$-25 + (1 + j3)I_3 + (-1 - j12) = 0 \quad \therefore \quad I_3 = 6.2 - j6.6 \text{ A}$$

P 9.36

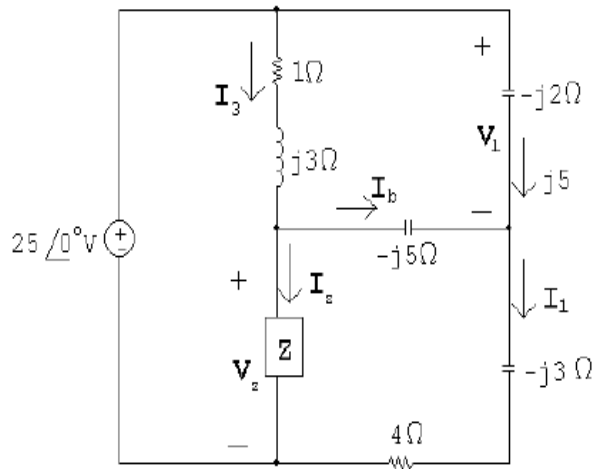

$$V_1 = j5(-j2) = 10 \text{ V}$$

$$-25 + 10 + (4 - j3)I_1 = 0 \quad \therefore \quad I_1 = \frac{15}{4 - j3} = 2.4 + j1.8 \text{ A}$$

$$I_b = I_1 - j5 = (2.4 + j1.8) - j5 = 2.4 - j3.2 \text{ A}$$

$$V_Z = -j5I_2 + (4 - j3)I_1 = -j5(2.4 - j3.2) + (4 - j3)(2.4 + j1.8) = -1 - j12 \text{ V}$$


$$-25 + (1 + j3)I_3 + (-1 - j12) = 0 \quad \therefore \quad I_3 = 6.2 - j6.6 \text{ A}$$

$$I_Z = I_3 - I_2 = (6.2 - j6.6) - (2.4 - j3.2) = 3.8 - j3.4 \text{ A}$$

$$Z = \frac{V_Z}{I_Z} = \frac{-1 - j12}{3.8 - j3.4} = 1.42 - j1.88 \Omega$$

P 9.44 [a] $j\omega L = j(1000)(100) \times 10^{-3} = j100 \Omega$
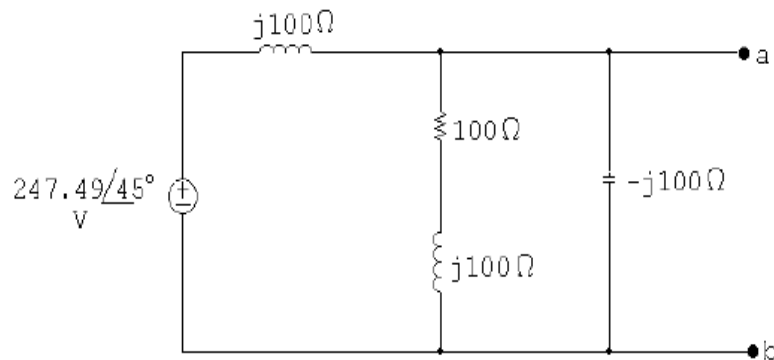
$$\frac{1}{j\omega C} = -j \frac{10^6}{(1000)(10)} = -j100 \Omega$$



Using voltage division,

$$V_{ab} = \frac{(100 + j100) \parallel (-j100)}{j100 + (100 + j100) \parallel (-j100)} (247.49 \angle 45^\circ) = 350 \angle 0^\circ$$

$$V_{Th} = V_{ab} = 350 \angle 0^\circ \text{ V}$$


[b] Remove the voltage source and combine impedances in parallel to find

$$Z_{Th} = Z_{ab}:$$


$$Y_{ab} = \frac{1}{j100} + \frac{1}{100 + j100} + \frac{1}{-j100} = 5 - j5 \text{ mS}$$

$$Z_{Th} = Z_{ab} = \frac{1}{Y_{ab}} = 100 + j100 \Omega$$

[c]

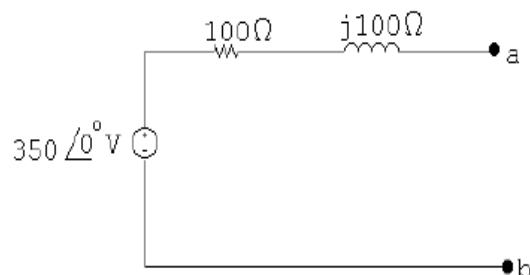

P 9.48 Open circuit voltage:

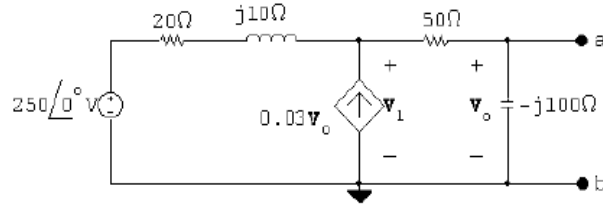


$$\frac{V_1 - 250}{20 + j10} - 0.03V_o + \frac{V_1}{50 - j100} = 0$$

$$\therefore V_o = \frac{-j100}{50 - j100} V_1$$

$$\frac{V_1}{20 + j10} + \frac{j3V_1}{50 - j100} + \frac{V_1}{50 - j100} = \frac{250}{20 + j10}$$

$$V_1 = 500 - j250 \text{ V}; \quad V_o = 300 - j400 \text{ V} = V_{\text{Th}}$$


Short circuit current:

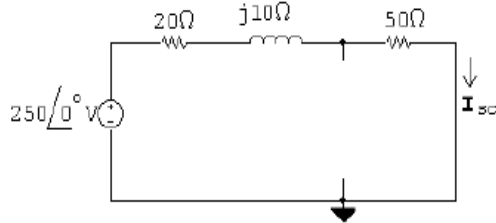


$$I_{\text{sc}} = \frac{250\angle 0^\circ}{70 + j10} = 3.5 - j0.5 \text{ A}$$

$$Z_{\text{Th}} = \frac{V_{\text{Th}}}{I_{\text{sc}}} = \frac{300 - j400}{3.5 - j0.5} = 100 - j100 \Omega$$

The Thévenin equivalent circuit:

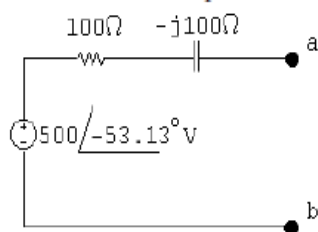

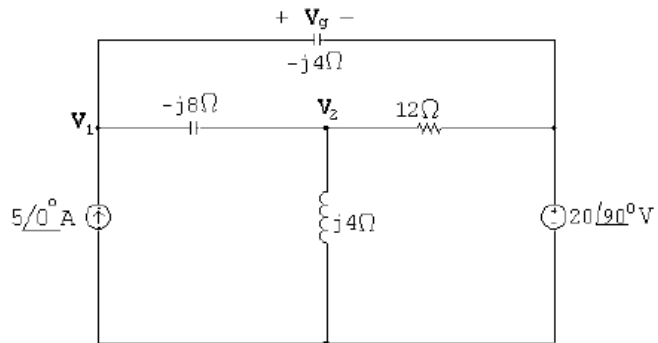P 9.56 Set up the frequency domain circuit to use the node voltage method:



$$\text{At } V_1: \quad -5\angle 0^\circ + \frac{V_1 - V_2}{-j8} + \frac{V_1 - 20\angle 90^\circ}{-j4} = 0$$

$$\text{At } V_2: \quad \frac{V_2 - V_1}{-j8} + \frac{V_2}{j4} + \frac{V_2 - 20\angle 90^\circ}{12} = 0$$

In standard form:

$$V_1 \left(\frac{1}{-j8} + \frac{1}{-j4} \right) + V_2 \left(-\frac{1}{-j8} \right) = 5\angle 0^\circ + \frac{20\angle 90^\circ}{-j4}$$

$$V_1 \left(-\frac{1}{-j8} \right) + V_2 \left(\frac{1}{-j8} + \frac{1}{j4} + \frac{1}{12} \right) = \frac{20\angle 90^\circ}{12}$$

Solving on a calculator:

$$V_1 = -\frac{8}{3} + j\frac{4}{3} \quad V_2 = -8 + j4$$

Thus

$$V_g = V_1 - 20\angle 90^\circ = -\frac{8}{3} - j\frac{56}{3} \text{ V}$$

P 9.59 Write a KCL equation at the top node:

$$\frac{V_o}{-j8} + \frac{V_o - 2.4I_{\Delta}}{j4} + \frac{V_o}{5} - (10 + j10) = 0$$


The constraint equation is:

$$I_{\Delta} = \frac{V_o}{-j8}$$

Solving,

$$V_o = j80 = 80\angle 90^\circ \text{ V}$$

P 9.63

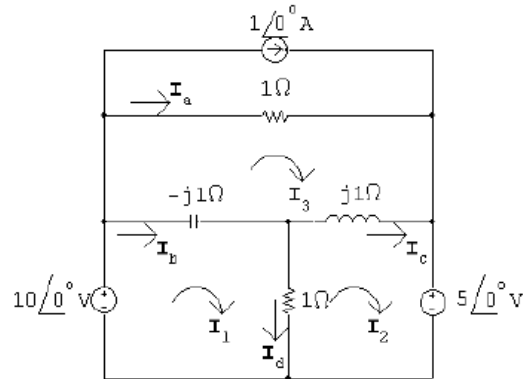

$$10\angle 0^\circ = (1 - j1)I_1 - 1I_2 + j1I_3$$

$$-5\angle 0^\circ = -1I_1 + (1 + j1)I_2 - j1I_3$$

$$1 = j1I_1 - j1I_2 + I_3$$

Solving,

$$I_1 = 11 + j10 \text{ A}; \quad I_2 = 11 + j5 \text{ A}; \quad I_3 = 6 \text{ A}$$

$$I_a = I_3 - 1 = 5 \text{ A}$$


$$I_b = I_1 - I_3 = 5 + j10 \text{ A}$$

$$I_c = I_2 - I_3 = 5 + j5 \text{ A}$$

$$I_d = I_1 - I_2 = j5 \text{ A}$$

P 9.64 $j\omega L = j10,000(5 \times 10^{-3}) = j50 \Omega$
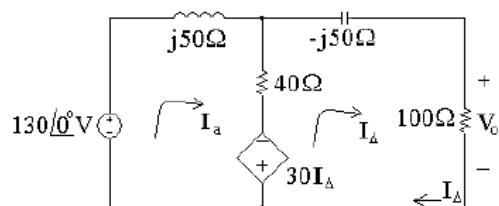
$$\frac{1}{j\omega C} = \frac{-j}{(10,000)(2 \times 10^{-6})} = -j50 \Omega$$



$$130\angle 0^\circ = (40 + j50)I_a - 40I_\Delta + 30I_\Delta$$

$$0 = -40I_a + 30I_\Delta + (140 - j50)I_\Delta$$

Solving,

$$I_\Delta = (400 - j400) \text{ mA}$$

$$V_o = 100I_\Delta = 40 - j40 = 56.57\angle -45^\circ$$

$$v_o = 56.57 \cos(10,000t - 45^\circ) \text{ V}$$