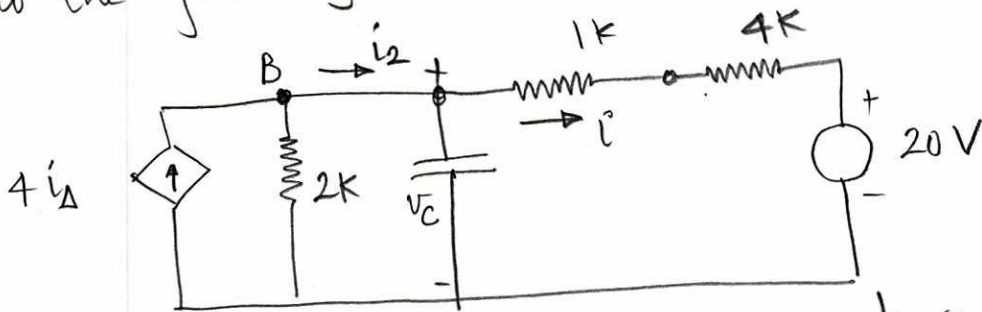


Solution Problem 1.

Using source transformation, the circuit is equivalent to the following circuit:



Using (KVL) to the left loop, we have

$$-v_C + 5 \times 10^3 i + 20 = 0$$

$$i = \frac{-1}{250} + \frac{1}{5000} v_C \quad (1)$$

At node A (KCL) $i_2 = C \frac{dv_C}{dt} + i \quad (2)$

KCL at node B gives $4i_A = \frac{v_C}{2 \times 10^3} + i_2 \quad (3)$

KCL at node C gives $i_A = i + 5 \times 10^{-3} \quad (4)$

From Eqs. (1), (2), (3) and (4), we write the differential equation:

$$1.6 \times 10^{-6} \frac{dv_c}{dt} - \frac{1}{10^4} v_c - \frac{1}{125} = 0 \quad (5)$$

$$\tau = -62.5$$

Then,

$$v_c(t) = v_c(0) e^{-\frac{t}{\tau}} + v_f(\infty) \left(1 - e^{-\frac{t}{\tau}}\right)$$

$v_c(\infty)$ is the solution of $-\frac{1}{10^4} v_c - \frac{1}{125} = 0$

Before the switch is opened $i_A = 0 \Rightarrow v_c(0) = 0$

$$v_c(t) = -80 + 80 e^{-\frac{125}{2} t}$$

$$v_f(t^*) = 14.4 \times 10^3 \Rightarrow$$

$$t^* = 0.08317 \text{ (s)}$$

See the figure in the next page.

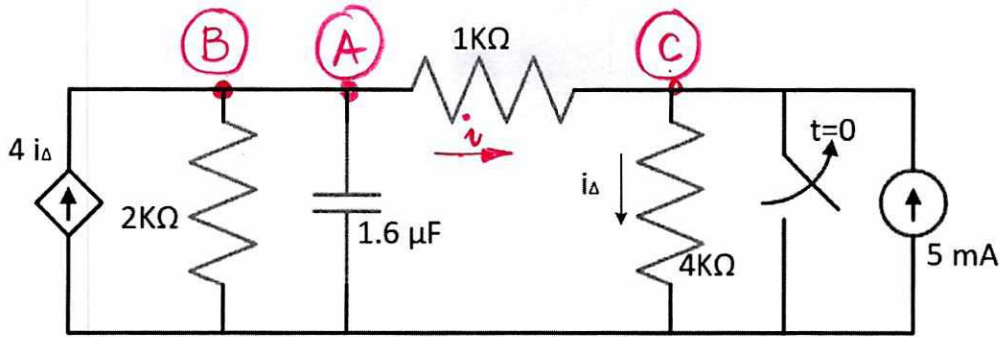


Figure 1: Circuit of Problem 1.

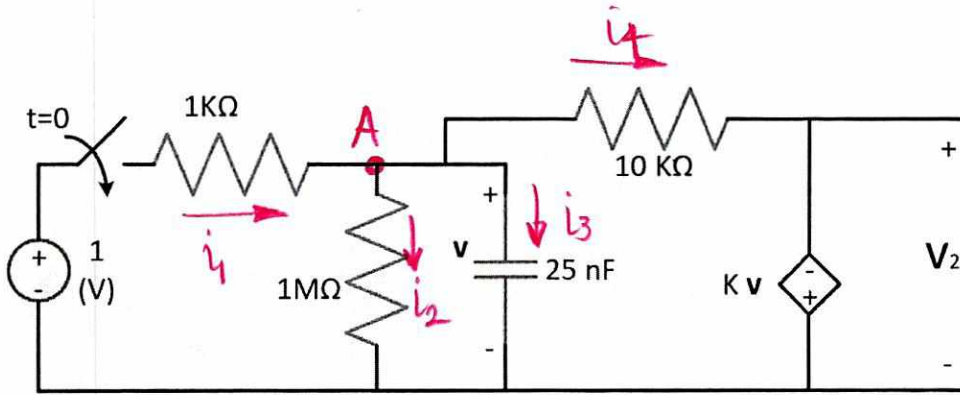


Figure 2: Circuit of Problem 2.

Solution of Problem 2.

At node A, we write

$$\frac{1-v}{10^3} = \frac{v}{10^6} + C \frac{dv}{dt} + \frac{v-v_2}{10^4} ; \begin{cases} C = 25 \text{ nF} \\ v_2 = -Kv \end{cases}$$

This gives $25 \times 10^{-6} \frac{dv}{dt} + \left(10^2 + 1 + \frac{1}{10} + \frac{1}{10^3}\right)v = 1$

Where the solution is given by:

$$v(t) = \frac{1000}{101101} - \frac{1000}{101101} e^{-4044040t}$$

$$v_2(t) = -\frac{1}{10} v(t) = -9.89 + 9.89 e^{-4.044 \times 10^6 t}$$

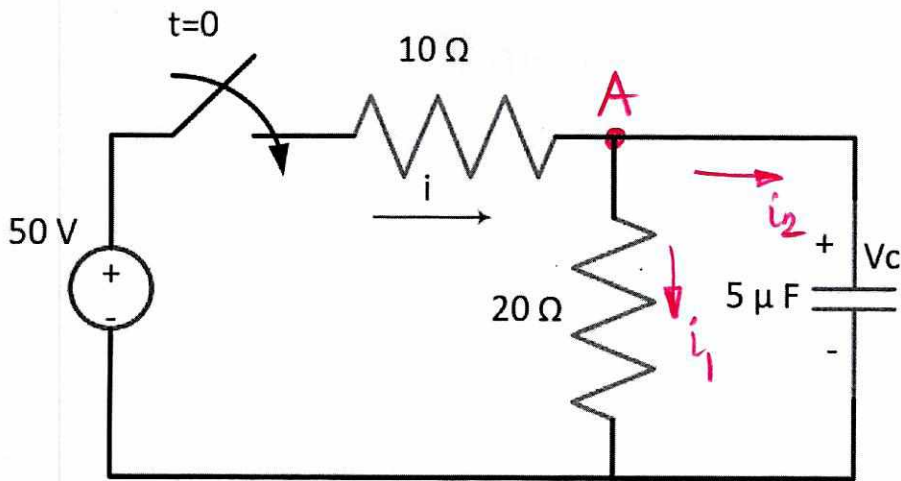


Figure 3: Circuit of Problem 3.

Solution of Problem 3.

At node A; $i = i_1 + i_2$, or

$$\frac{50 - v_c}{10} = \frac{v_c}{20} + C \frac{dv_c}{dt}$$

$$5 \times 10^{-6} \frac{dv_c}{dt} + \left(\frac{1}{20} + \frac{1}{10} \right) v_c = 5$$

$$v_c(t) = \frac{100}{3} \left(1 - e^{-3 \times 10^4 t} \right) \text{ (V)} \quad \text{with } v_c(0) = 0$$

The current $i(t)$ is then deduced

$$i(t) = \frac{5}{3} + \frac{10}{3} e^{-3 \times 10^4 t}$$


Solution of Problem 4.

Solve problem referenced (8.32, page 322) in your text book.

$$\text{At } t < 0 \quad i_L(0^-) = \frac{-15}{3000} = -5 \text{ mA}$$

$$v_C(0^-) = 0 \text{ V}$$

The circuit is reduced to

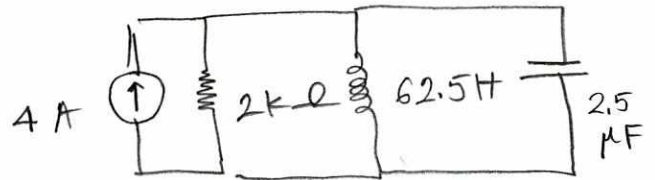

$$i_L(\infty) = 4 \text{ mA}$$

$$\omega_0^2 = \frac{1}{LC} = 6400, \quad \omega_0 = 80 \text{ rad/s}$$

$$\alpha = \frac{1}{2RC} = 100$$

$$s_1 = -40 \text{ rad/s}, \quad s_2 = -160 \text{ rad/s}$$

$$i_L = I_f + A_1' e^{-40t} + A_2' e^{-160t}; \quad i_L(\infty) = \frac{I_f}{1} = 4 \text{ mA}$$

$$i_L(0) = A_1' + A_2' + I_f = -5 \text{ mA} \rightarrow \underline{A_1' + A_2' = -9 \text{ mA}}$$

$$\frac{di_L}{dt}(0) = 0 = \underline{-40 A_1' - 160 A_2'}$$

By solving with respect to $A_1', A_2' \Rightarrow$

$$i_L(t) = 4 - 12e^{-40t} + 3e^{-160t} \text{ mA}$$

Solution of Problem 5.

Solve problem referenced (8.33, page 322) in your text book.

$$\underline{v_c(0^+) = 120 \text{ V}} \quad ; \quad \underline{i_L(0^+) = 60 \text{ mA}} \quad ; \quad \underline{i_L(\infty) = 48 \text{ mA}}$$

$$\alpha = \frac{1}{2RC} = 40, \quad \omega_0^2 = \frac{1}{LC} = 2500$$

$$\alpha^2 = 1600; \quad \alpha^2 < \omega_0^2 \quad \underline{\text{solution under damped}}$$

$$\underline{s_{1,2} = -40 \pm j30 \text{ rad/s}}$$

$$i_L = I_f + B_1 e^{-\alpha t} \cos(\omega_d t) + B_2 e^{-\alpha t} \sin(\omega_d t)$$

$$i_L(t) = 48 + B_1 e^{-40t} \cos(30t) + B_2 e^{-40t} \sin(30t)$$

The constants B_1 and B_2 are determined by:

$$i_L(0) = 60 \text{ mA} \quad \text{and} \quad \frac{di_L}{dt}(0) = 1.5$$

$$i_L(t) = 48 + 12 e^{-40t} \cos(30t) + 66 e^{-40t} \sin(30t)$$