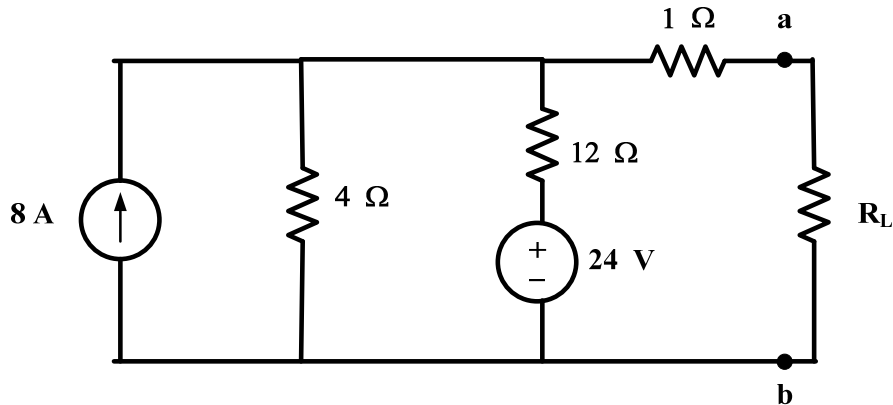


EE 202-05-Winter 2014(141)  
QZ2

Sec	Ser	ID	Name
-----	-----	----	------




For the circuit shown, the load resistant is  $R_L$ .

Find the **maximum power** absorb by load resistant is  $R_L$ ?

method ①

Finding  $V_{oc}$

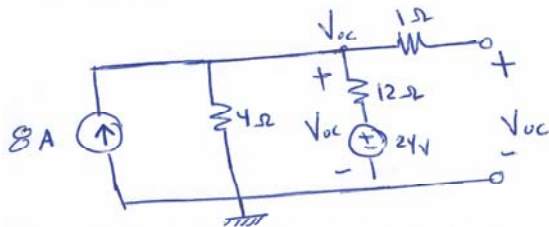


Kcl at node  $V_{oc}$





$$-8 + \frac{V_{oc}}{4} + \frac{V_{oc} - 24}{12} = 0$$

$$V_{oc} = 30 \text{ V}$$

Finding  $R_{th}$

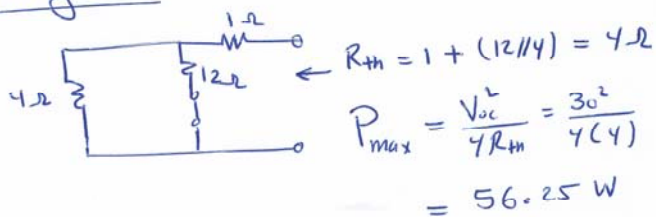

method (2)

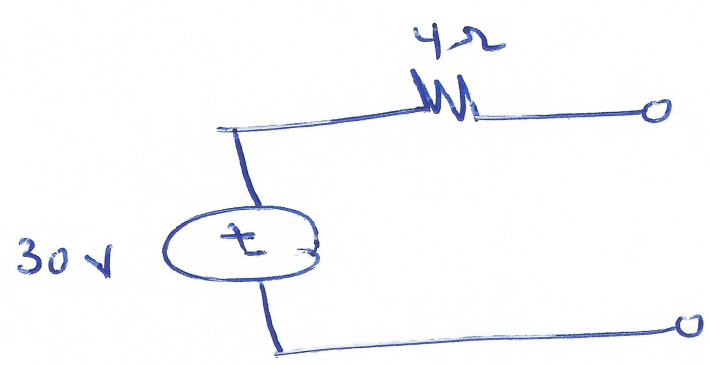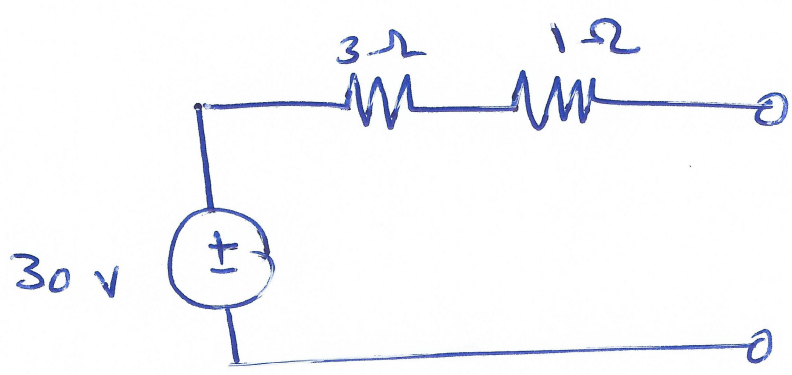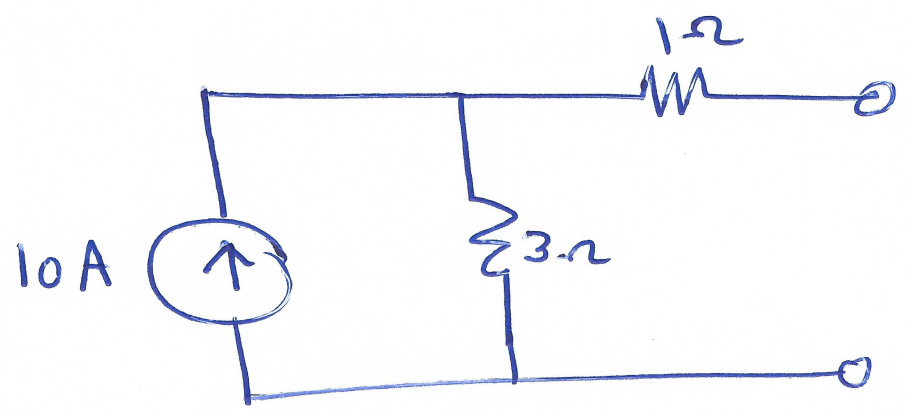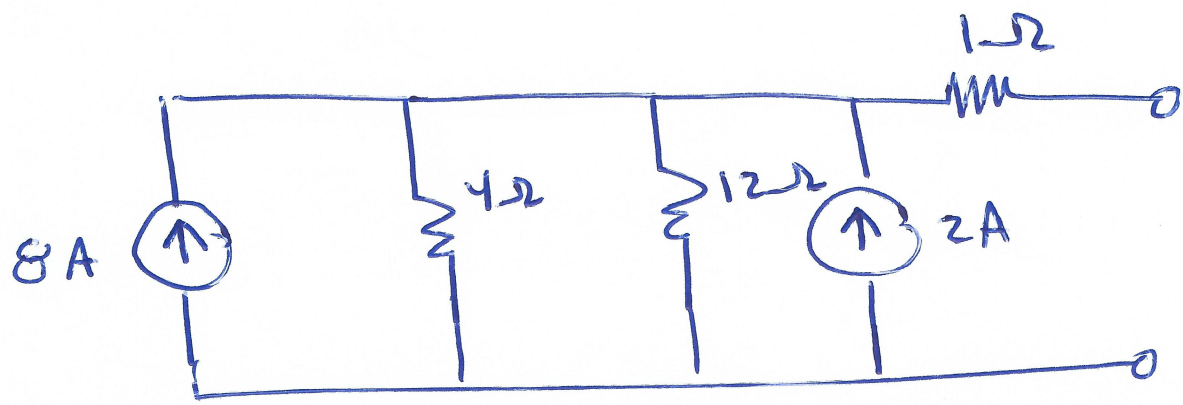


$$R_L = R_{th} = 4\Omega$$

$$P_{max} = \frac{V_{oc}^2}{4R_{th}}$$

$$= \frac{30^2}{4(4)} = 56.25W$$

EE 202-02-Winter 2014(141)  
QZ5


Sec	Ser	ID	Name
-----	-----	----	------

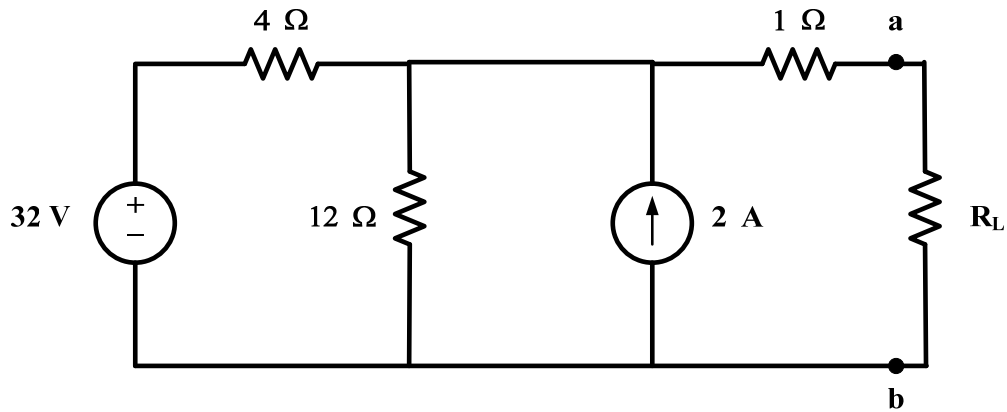

For the circuit shown, the load resistant is  $R_L$ .

Find the **maximum power** absorb by load resistant is  $R_L$ ?

Method (V)

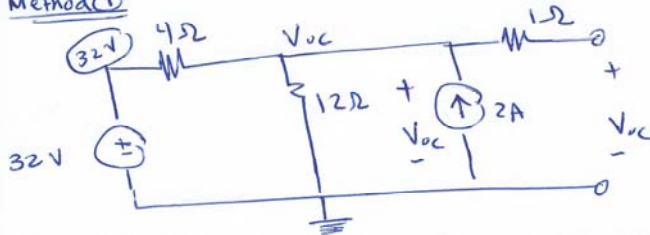


Finding  $V_{oc}$

KCL at node  $V_{oc}$   $\frac{V_{oc} - 32}{4} + \frac{V_{oc}}{12} - 2 = 0$

$\Rightarrow V_{oc} = 30$

Finding  $R_{th}$





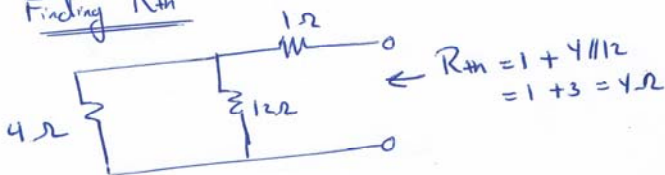


$R_{th} = 1 + 4 \parallel 12$   
 $= 1 + 3 = 4\Omega$

$\Rightarrow R_L = R_{th} = 4\Omega$

$P_{max} = \frac{V_{oc}^2}{4R_{th}} = \frac{30^2}{4(4)} = 56.25W$

method (2)

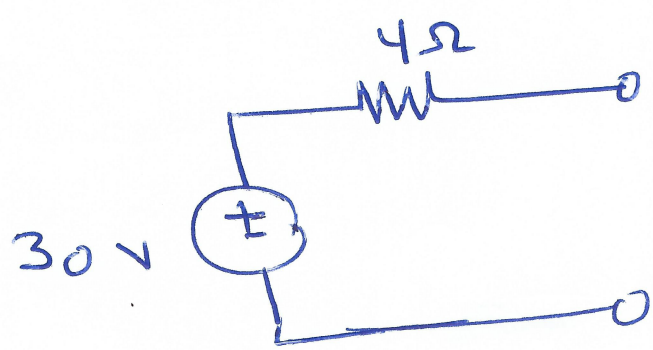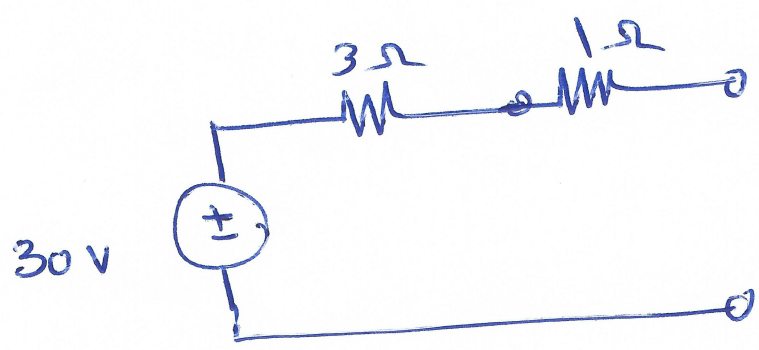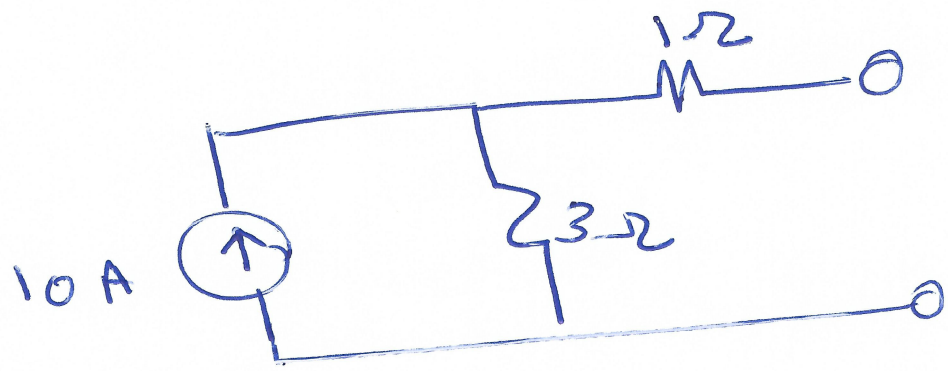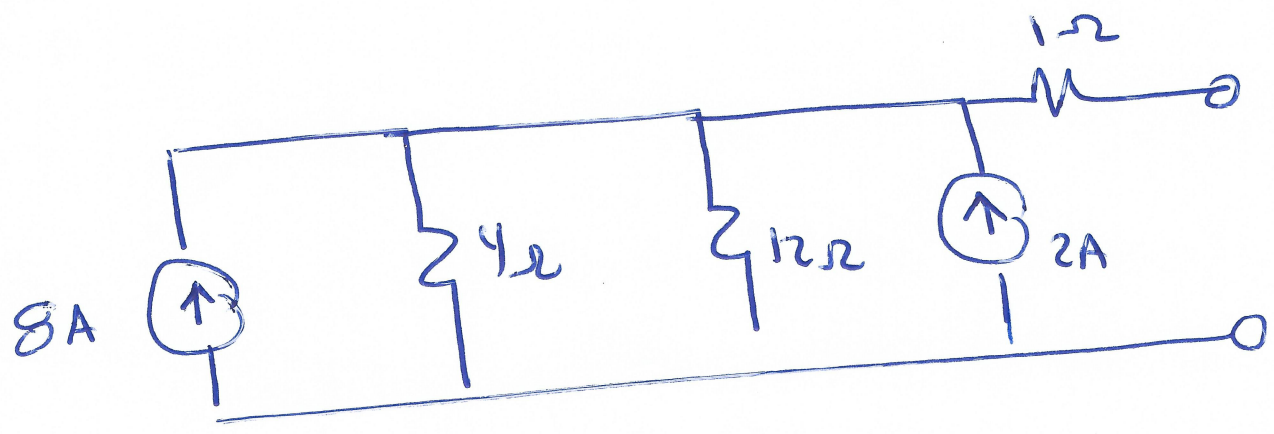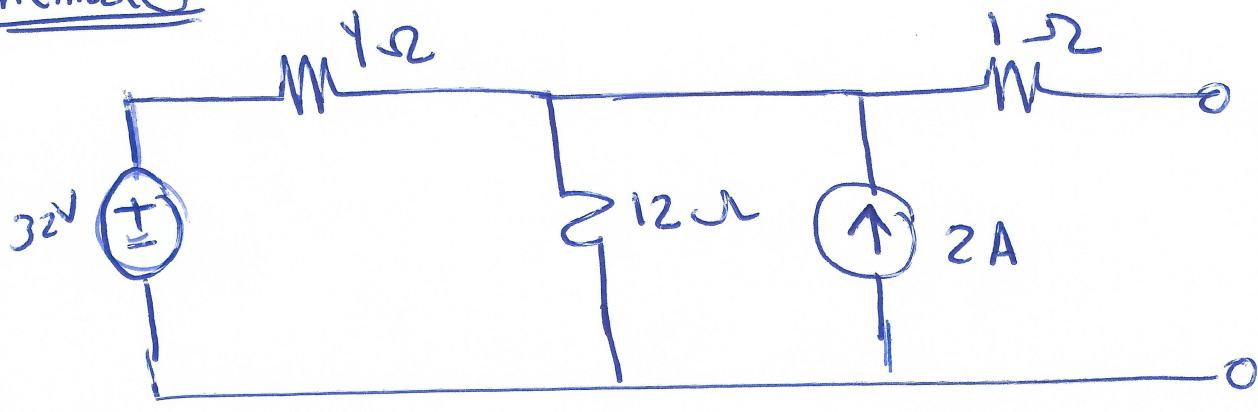

$$R_L = R_{th} = 4\Omega$$
$$P_{max} = \frac{V_{oc}^2}{4R_{th}}$$
$$= \frac{30^2}{4(4)} = 56.25W$$