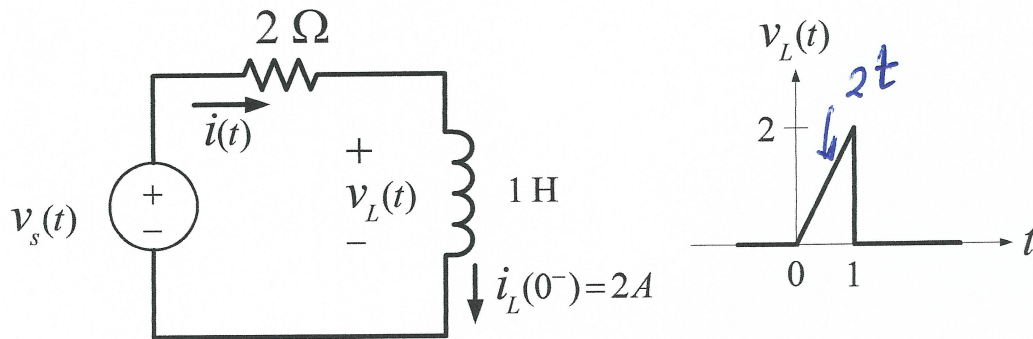


Sec	Ser	ID	Name
			KEY



For the circuit shown above, the inductor voltage $v_L(t)$ is as shown:

(a) Find $i(t)$ if the current through the inductor is 2 A ?

(b) Find the energy stored at the inductor at $t = 0, 0.5$ and 1.5 seconds?

$$(a) \quad i'(t) = i_L'(t) = \frac{1}{L} \int_{t_0}^t v_L(\tau) d\tau + i_L(t_0)$$

$$= \frac{1}{1} \int_0^t (2\tau) d\tau + 2 = t^2 + 2 \text{ A} \quad 0 \leq t \leq 1$$

$$i'(t) = \frac{1}{1} \int_1^t (0) d\tau + i_L(1) = 0 + (1^2 + 2)$$

$$= 3 \text{ A} \quad t \geq 1$$


$$i_L'(t) = \begin{cases} t^2 + 2 & 0 \leq t \leq 1 \\ 3 & t \geq 1 \end{cases}$$

$$(b) \quad W_L(t) = \frac{1}{2} L i_L^2(t) \Rightarrow W_L(0) = \frac{1}{2} (1) (2)^2 = 2 \text{ J}$$

$$W_L(0.5) = \frac{1}{2} (1) (0.5^2 + 2) = 1.125 \text{ J}$$


$$W_L(1.5) = \frac{1}{2} (1) (1.5^2 + 2) = 2.125 \text{ J}$$

Sec	Ser	ID	Name
			KEY

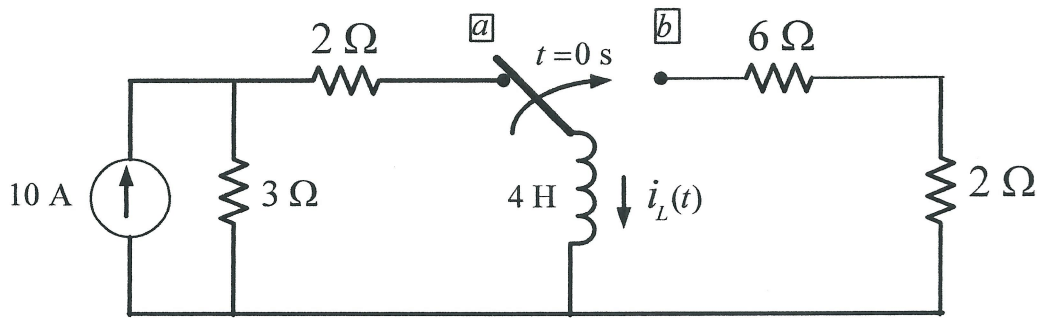


For the circuit shown above, the switch was in position **a** for long time and at $t=0$ the switch move to position **b** find $i_L(t)$ $t > 0$?

$t < 0$

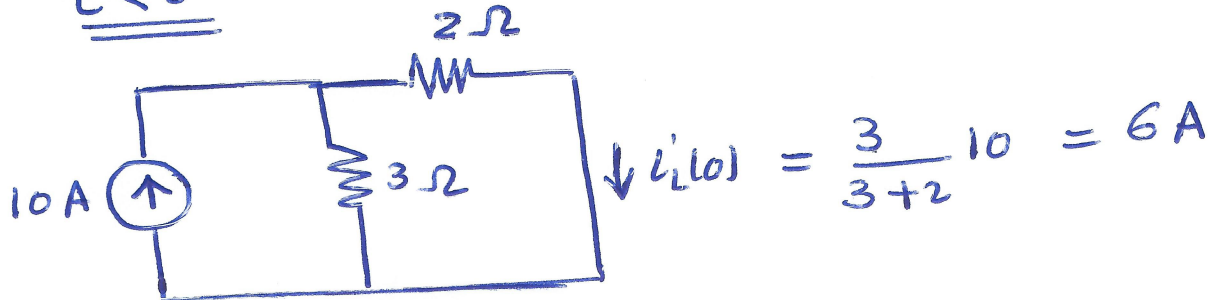

$t > 0$

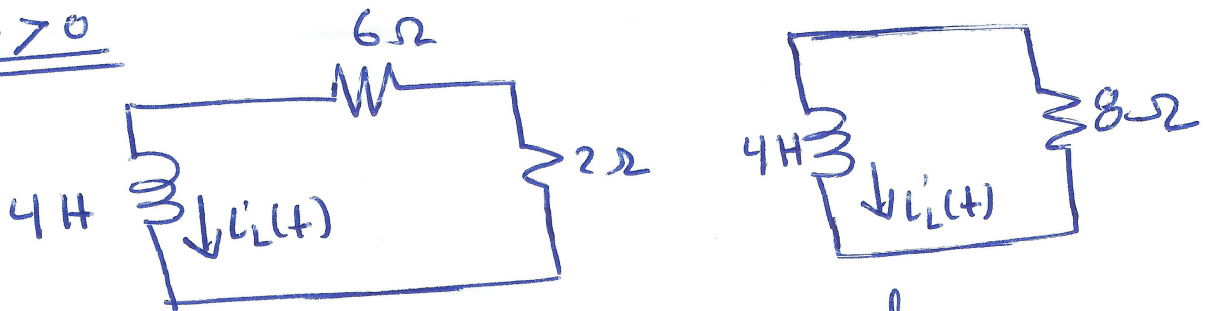

$$\tau = \frac{L}{R} = \frac{4}{8} = \frac{1}{2} \text{ second}$$

$$\begin{aligned} i_L(t) &= i_L(0) e^{-t/\tau} \\ &= 6 e^{-t/1/2} \\ &= 6 e^{-2t} \end{aligned}$$