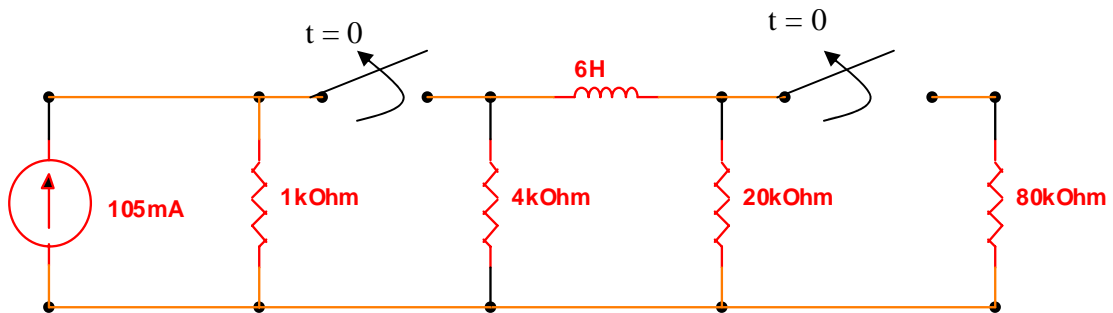


KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
ELECTRICAL ENGINEERING DEPARTMENT
EE-201 ELECTRIC CIRCUITS
Dr. Ibrahim O. Habiballah


Solution

Sec: 8 Quiz # 6 Ser. # Name: I.D.#

The two switches in the circuit below are opened at $t = 0$. How much time does it take for the energy dissipated in the 4 K-Ohm resistor to 10% of the initial energy stored in the 6 H inductor.




For $t < 0$

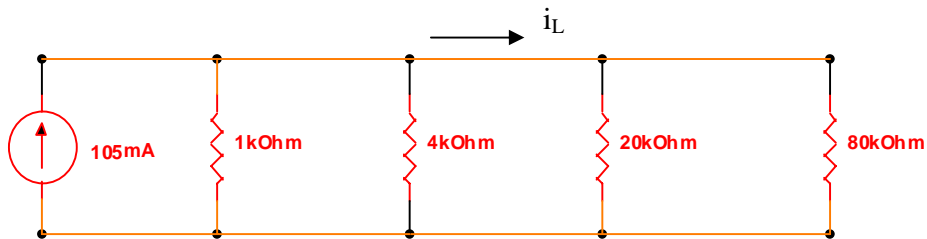

$$1 \parallel 4 = 0.8 \text{ K-Ohm} \quad \& \quad 20 \parallel 80 = 16 \text{ K-Ohm}$$

$$i_L(t) = \frac{0.8}{0.8 + 16} (105) = 5 \text{ mA}$$

For $t \geq 0$

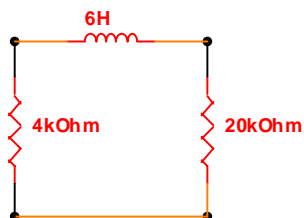

$$i_L(t) = 5e^{-4000t} \text{ mA}$$

The energy stored in the inductor at $t = 0$

$$w(0) = \frac{1}{2}(6)(5 \times 10^{-3})^2 = 75 \mu \text{ J}$$

The power dissipated across the 4 K-Ohm resistor at time t

$$p(t) = (4000)(5e^{-4000t})^2 = 0.1e^{-8000t} \text{ W}$$

The energy dissipated across the 4 K-Ohm resistor at time t

$$w(t) = \int_0^t 0.1e^{-8000t} dt = 12.5(1 - e^{-8000t}) \mu \text{ J}$$

10% of the initial energy stored in the 6 H inductor = $7.5 \mu \text{ J}$

Therefore, at this time

$$12.5(1 - e^{-8000t}) = 7.5$$

$$t = 114.5 \mu \text{ s}$$