

Student Name :

Student ID:

A 10-kVA, 450 / 120-V, 60-Hz, transformer gives the following test results:

Open circuit test (HV side open): 120 V, 4.2 A, 80 W

Short circuit test (LV side short): 9.65 V, 22.2 A, 120 W

- (a) Derive the approximate equivalent circuit referred to the high-voltage side.  
 (b) Determine the voltage regulation at full load and 0.8 PF leading.  
 (c) Determine the efficiency at 50% of full load and 0.8 PF lagging.

$$\text{O.C.} \quad R'_C = \frac{(120)^2}{80} = 180 \Omega, \quad a = \frac{450}{120} = 3.75$$

$$R_C = a^2 R'_C = \underline{\underline{2530 \Omega}}$$

$$I'_C = \frac{120}{R'_C} = 0.667 \text{ A} \quad I_m = \sqrt{I_0^2 - I'_C} = 4.15 \text{ A}$$

$$X'_m = \frac{120}{I'_m} = 28.94 \Omega$$

$$X_m = a^2 X'_m = \underline{\underline{407 \Omega}}$$

$$\text{S.C.} \quad Z_{e1} = \frac{9.65}{22.2} = 0.435 \Omega$$

$$R_{e1} = \frac{120}{(22.2)^2} = \underline{\underline{0.243 \Omega}}$$

$$X_{e1} = \sqrt{Z_{e1}^2 - R_{e1}^2} = \underline{\underline{0.361 \Omega}}$$

$$I_{1FL} = \frac{10000}{450} = 22.2 \text{ A}$$

$$\text{Voltage Drop} \approx I_1 (R_{e1} \cos \phi + X_{e1} \sin \phi) \approx 9.2 \text{ V}$$

$$\text{VR} = \frac{9.2}{450} \times 100 = 2.04 \%$$

$$\eta_{FL} = \frac{10000 \times 0.8}{10000 \times 0.8 + 80 + 120} \times 100 = 97.57 \%$$

at half load

$$\eta = \frac{\frac{1}{2} \times 10000 \times 0.8}{\frac{1}{2} \times 10000 \times 0.8 + 80 + \left(\frac{1}{2}\right)^2 \times 120} \times 100 = 97.34 \%$$