

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

ELECTRICAL ENGINEERING DEPARTMENT

EE 306

Solved-HW # 3: Transformers

4-14

$$\textcircled{a} \quad a = \frac{4800}{240} = 20$$

$$Z_{E2} = \frac{1}{a^2} Z_{E1} = \frac{1}{(20)^2} (120 + j300) = 0,3 + j0,75 \, \Omega$$

$$\textcircled{b} \quad V_2 = 230 \angle 0^\circ \, \text{V}$$

$$I_{2, \text{ref}} = \frac{10,000}{240} \angle -\cos^{-1} 1 = 41,67 \angle 0^\circ \, \text{A}$$

$$\begin{aligned} V_1 &= aV_2 + \frac{I_2}{a} Z_{E1} \\ &= 20(230 \angle 0^\circ) + \left(\frac{41,67}{20} \angle 0^\circ\right)(120 + j300) \\ &= 4600 \angle 0^\circ + 2,083 \angle 0^\circ (120 + j300) \\ &= 4890 \angle 7,3^\circ \, \text{V} \end{aligned}$$

## 4-15

$$V_2 = 230 \angle 0^\circ \text{ V}$$

$$I_2 = \frac{75,000}{(230)(0,85)} \angle -\cos^{-1} 0,85 = 383,63 \angle -31,8^\circ \text{ A}$$

$$a = \frac{2300}{230} = 10$$

$$\begin{aligned} \textcircled{a} \quad E_1 &= aV_2 + \frac{I_2}{a} (a^2 R_2 + ja^2 X_2) \\ &= 10(230 \angle 0) + \left( \frac{383,63 \angle -31,8^\circ}{10} \right) (10)^2 (0,003 + j0,0065) \\ &= 2322,9 + j15,1 = 2322,97 \angle 0,37^\circ \text{ V} \end{aligned}$$

---

$$\begin{aligned} I_1 &= \frac{I_2}{a} + E_1 \left( \frac{1}{R_c} + \frac{1}{jX_m} \right) = \frac{383,63 \angle -31,8^\circ}{10} + E_1 \left( \frac{10^{-3}}{45} + \frac{10^{-3}}{j1} \right) \\ &= 33,14 - j22,54 = 40,08 \angle -34,2^\circ \text{ A} \end{aligned}$$

$$\begin{aligned} \textcircled{b} \quad V_1 &= E_1 + I_1 (R_1 + jX_1) = 2322,97 \angle 0,37^\circ + (40,08 \angle -34,2^\circ) (0,3 + j0,65) \\ &= 2347,5 + j29,78 = 2347,7 \angle 0,73^\circ \text{ V} \end{aligned}$$

$$\begin{aligned} \textcircled{c} \quad P_1 &= V_1 I_1 \cos \theta_{V_1, I_1} = (2347,7)(40,08) \cos (0,73 + 34,2) \\ &= 77,15 \text{ kW} \end{aligned}$$

$$\text{PF} = \cos (0,73 + 34,2) = 0,82 \text{ lagging}$$

## 4-21

$$\textcircled{a} \quad P_{\text{out}} = (10)(0.8) = 8 \text{ kW} = 8000 \text{ W}$$

$$\begin{aligned} P_{\text{in}} &= P_{\text{out}} + P_{\text{core}} + P_{\text{cu}} \\ &= 8000 + 150 + 250 = 8400 \text{ W} \end{aligned}$$

$$\eta = \frac{P_{\text{out}}}{P_{\text{in}}} = \frac{8000}{8400} 100\% = 95.2\%$$

$$\textcircled{b} \quad P_{\text{out}} = \left(\frac{3}{4}\right)(10,000)(1.0) = 7500 \text{ W}$$

$$P_{\text{in}} = 7500 + 150 + \left(\frac{3}{4}\right)^2(250) = 7790.6 \text{ W}$$

$$\eta = \frac{7500}{7790.6} 100\% = 96.3\%$$

$$\textcircled{c} \quad P_{\text{out}} = \left(\frac{1}{2}\right)(10,000)(0.6) = 3000 \text{ W}$$

$$P_{\text{in}} = 3000 + 150 + \left(\frac{1}{2}\right)^2(250) = 3212.5 \text{ W}$$

$$\eta = \frac{3000}{3212.5} 100\% = 93.4\%$$



# 4-24

$$a = \frac{2400}{240} = 10$$

$$I_{1, \text{rated}} = \frac{50,000}{2400} = 20.8 \text{ A}$$

$$R_{C2} = \frac{V_{OC}^2}{P_{OC}} = \frac{(240)^2}{450} = 128 \Omega$$

$$G_{C2} = \frac{1}{R_{C2}} = 0.0078 \text{ S}$$

$$Y_{O2} = \frac{I_{OC}}{V_{OC}} = \frac{5}{240} = 0.02083 \text{ S}$$

$$B_{M2} = \sqrt{Y_{O2}^2 - G_{C2}^2} = \sqrt{(0.02083)^2 - (0.0078)^2} = 0.0193 \text{ S}$$

---

$$X_{M2} = \frac{1}{B_{M2}} = 51.8 \Omega$$

$$R_{E1} = \frac{P_{SC}}{I_{SC}^2} = \frac{600}{(20.8)^2} = 1.39 \Omega$$

$$Z_{E1} = \frac{V_{SC}}{I_{SC}} = \frac{55}{20.8} = 2.64 \Omega$$

$$X_{E1} = \sqrt{Z_{E1}^2 - R_{E1}^2} = \sqrt{(2.64)^2 - (1.39)^2} = 2.24 \Omega$$

(a)  $V_2 = 220 \angle 0^\circ$

$$I_2 = 156 \angle -\cos^{-1} 0.8 = 156 \angle -36.9^\circ$$

$$\begin{aligned} V_1 &= aV_2 + \frac{I_2}{a} (R_{E1} + jX_{E1}) = 10(220 \angle 0^\circ) + \left(\frac{156}{10} \angle -36.9^\circ\right)(1.39 + j2.24) \\ &= 2238.4 \angle 0.4^\circ \end{aligned}$$

$$\text{V.R.} = \frac{V_1 - aV_2}{aV_2} = \frac{2238.4 - 2200}{2200} \cdot 100\% = 1.7\%$$