

**KING FAHD UNIVERSITY OF PETROLEUM & MINERALS**  
**ELECTRICAL ENGINEERING DEPARTMENT**

**Dr. Ibrahim O. Habiballah**


**EE-306**

**Key Solution**

Quiz # 4      Sec.: 3      I.D.#      Name:

Circle the correct answer.

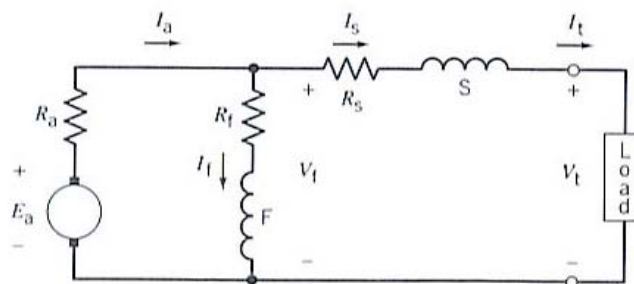The equivalent circuit shown below is for a



- a- long-shunt compound DC generator.
- b- short-shunt compound DC generator.**
- c- long-shunt compound DC motor.
- d- short-shunt compound DC motor.