

**King Fahd University of Petroleum & Minerals**  
**Electrical Engineering Department**

**EE 360: Home Work #1**

**Due Dates (Sep 10<sup>th</sup> for SMW Classes & Sep 11<sup>th</sup> for UT Classes)**

1. Problem A-2 from text
2. Problem A-3 from text
3. A balanced 3-phase, 173-V, 60-Hz source supplies the two following loads:
  - A  $\Delta$ -connected load with a phase impedance of  $(18+j24) \Omega$ ,
  - A Y-connected load with a phase impedance of  $10\angle 53.13^\circ \Omega$ .

Find:

- a) The power factor of the entire load.
- b) The total line current supplied.
- c) The total real, reactive, and apparent powers.

If two watt-meters are connected to measure the total power supplied. Find the reading on each instrument.

4. The 2 wattmeter method used to measure the power of a  $\Delta$ -connected load gave the wattmeter readings as 1560W and 2100W. If the line voltage is 220-V, calculate
  - a. Power per phase
  - b. Reactive power per phase
  - c. The power factor
  - d. The impedance of each phase