

EE 360 HW#6 solution

Q₁) @ A 40 km line is a short one. Hence


$$A = \underline{1} = D$$

$$B = Z$$

$$C = 0$$

$$A = (0.2 + j0.5)40 = \underline{8 + j20 \Omega}$$

(b)

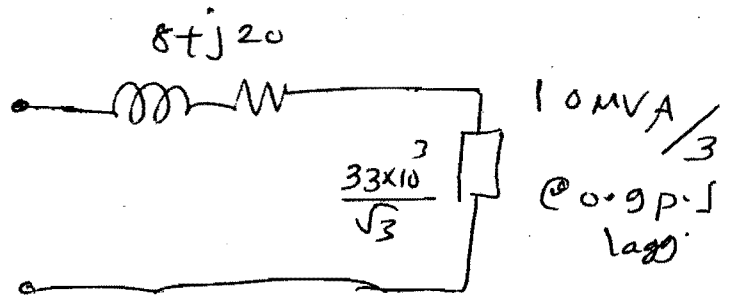

$$\begin{bmatrix} \vec{V}_s \\ \vec{I}_s \end{bmatrix} = \begin{bmatrix} 1 & 8 + j20 \\ 0 & 1 \end{bmatrix} \begin{bmatrix} \vec{V}_R \\ \vec{I}_R \end{bmatrix}$$

$$\vec{V}_R = \frac{33 \times 10^3}{\sqrt{3}} \quad \text{For lagging P.f.}$$

$$\vec{I}_R = \frac{10 \times 10^6 / 3}{\frac{33 \times 10^3}{\sqrt{3}}} \angle -\cos^{-1} 0.9$$

$$\vec{I}_R = 174.95 \angle -25.8^\circ \text{ A}$$

$$\Rightarrow \vec{V}_s = \frac{33 \times 10^3}{\sqrt{3}} \angle 0^\circ + (8 + j20)(174.95 \angle -25.8^\circ) + (21.54 \angle 68.2^\circ)(174.95 \angle -25.8^\circ)$$

$$= 19052.5 + 3768.4 \angle 42.4^\circ$$

$$= 19052.5 + 2782.8 + j2541$$

$$= 21835.3 + j2541$$

$$\vec{V}_s = 21.98 \angle 6.63^\circ \text{ kV}$$

For leading P.f.

$$\vec{I}_R = 174.95 \angle +25.8^\circ$$

$$\vec{V}_s = 19052.5 + 3768.4 \angle 94^\circ$$

$$= (19052.5 - 262.8) + j3759.2$$

$$= 18789.6 + j3759.2$$

$$\vec{V}_s = 19.16 \angle 11.3^\circ \text{ kV}$$

Q2)

Solution For a load of 40 MW, at 220 kV and 0.9 power factor lagging, the receiving-end current is given by

$$I_R = \frac{40,000}{\sqrt{3}(220)(0.9)} \angle -\cos^{-1} 0.9 = 116.6 \angle -25.8^\circ$$

The sending-end voltage is found as follows:

$$\begin{aligned} V_S &= V_R + ZI_R \\ &= (220/\sqrt{3}) \times 10^3 \angle 0^\circ + (35 + j140)(116.6 \angle -25.8^\circ) \\ &= 127,000 \angle 0^\circ + (144.3 \angle 76^\circ)(116.6 \angle -25.8^\circ) \\ &= 138.4 \angle 5.4^\circ \text{ kV (line-to-neutral)} \\ &= 239.7 \angle 35.4^\circ \text{ kV (line-to-line)} \end{aligned}$$

Since there is no shunt branch, the sending-end current is the same as the receiving-end current. Thus,

$$I_S = I_R = 116.6 \angle -25.8^\circ$$

The sending-end power factor is

$$PF_S = \cos[5.4^\circ - (-25.8^\circ)] = 0.86 \text{ lagging}$$

The percent voltage regulation is computed as

$$\begin{aligned} \text{Voltage regulation} &= \frac{V_{R,nl} - V_{R,fl}}{V_{R,fl}} 100\% \\ &= \frac{239.7 - 220}{220} 100\% = 8.95\% \end{aligned}$$

The sending-end real power is

$$\begin{aligned} P_S &= 3V_S I_S PF_S = 3(138.4 \times 10^3)(116.6)(0.86) \\ &= 41.6 \times 10^6 \text{ W} = 41.6 \text{ MW} \end{aligned}$$

Therefore, the efficiency of the line is found as follows:

$$\text{Efficiency} = (P_R/P_S)100\% = (40/41.6)100\% = 96.2\%$$

Q3)

Solution For a load of 40 MW, at 220 kV and 0.9 power factor lagging, the receiving-end current is given by

$$I_R = \frac{40,000}{\sqrt{3}(220)(0.9)} \angle -\cos^{-1} 0.9 = 116.6 \angle -25.8^\circ \text{ A}$$

For the nominal π equivalent circuit, the ABCD parameters are computed as follows:

$$\begin{aligned} A &= D = ZY/2 + 1 \\ &= (35 + j140)(930 \times 10^{-6} \angle 90^\circ)/2 + 1 \\ &= 0.935 + j0.0163 = 0.935 \angle 1^\circ \\ B &= Z = 35 + j140 = 144.3 \angle 76^\circ \Omega \\ C &= Y(ZY/4 + 1) \\ &= (930 \times 10^{-6} \angle 90^\circ)[(35 + j140)(930 \times 10^{-6} \angle 90^\circ)/4 + 1] \\ &= (-7.57 + j899.7) \times 10^{-6} = 900 \times 10^{-6} \angle 90.5^\circ \text{ S} \end{aligned}$$

Thus, the sending-end voltage and current are given by

$$\begin{aligned} V_S &= AV_R + BI_R \\ &= (0.935 \angle 1^\circ)(127,000 \angle 0^\circ) + (144.3 \angle 76^\circ)(116.6 \angle -25.8^\circ) \\ &= 130.4 \angle 6.6^\circ \text{ kV (line-to-neutral)} \\ &= 225.8 \angle 36.6^\circ \text{ kV (line-to-line)} \end{aligned}$$

$$\begin{aligned} I_S &= CV_R + DI_R \\ &= (900 \times 10^{-6} \angle 90.5^\circ)(127,000 \angle 0^\circ) + (0.935 \angle 1^\circ)(116.6 \angle -25.8^\circ) \\ &= 97.97 + j68.57 = 119.6 \angle 35^\circ \text{ A} \end{aligned}$$

The sending-end power factor is

$$PF_S = \cos(6.6^\circ - 35.0^\circ) = 0.88 \text{ leading}$$

At no load, the receiving-end voltage is $1/A$ times the sending-end voltage; thus, the voltage regulation is computed as follows:

$$\begin{aligned} \text{Voltage regulation} &= \frac{V_S/A - V_{R,nl}}{V_{R,nl}} 100\% \\ &= \frac{225.8/0.935 - 220}{220} 100\% = 9.77\% \end{aligned}$$

The sending-end real power is

$$\begin{aligned} P_S &= 3V_S I_S PF_S = 3(130.4 \times 10^3)(119.6)(0.88) \\ &= 41.17 \times 10^6 \text{ W} = 41.17 \text{ MW} \end{aligned}$$

Therefore, the efficiency of the line is found as follows:

$$\text{Efficiency} = (P_R/P_S)100\% = (40/41.17)100\% = 97.2\%$$