

P1)

$$I_2 = \frac{150 \times 10^3}{240} = 625 \text{ A}$$

$$\frac{I_2}{a} = 62.5 \angle -36.8^\circ = 50 - j37.5 \text{ A}$$

$$aV_2 = 2400 \angle 0^\circ = 2400 + j0 \text{ V}$$

$$a^2R_2 = 0.2 \Omega \quad \text{and} \quad a^2X_2 = 0.45 \Omega$$

Hence

$$\begin{aligned} E_1 &= (2400 + j0) + (50 - j37.5)(0.2 + j0.45) \\ &= 2427 + j15 = 2427 \angle 0.35^\circ \text{ V} \end{aligned}$$

$$I_m = \frac{2427 \angle 0.35^\circ}{1550 \angle 90^\circ} = 1.56 \angle -89.65^\circ = 0.0095 - j1.56 \text{ A}$$

$$I_c = \frac{2427 + j15}{10,000} \approx 0.2427 + j0 \text{ A}$$

$$I_0 = I_c + I_m = 0.25 - j1.56 \text{ A}$$

$$I_1 = I_0 + \frac{I_2}{a} = 50.25 - j39.06 = 63.65 \angle -37.85^\circ \text{ A}$$

Thus, the primary voltage is

$$\begin{aligned} V_1 &= (2427 + j15) + (50.25 - j39.06)(0.2 + j0.45) \\ &= 2455 + j30 = 2455 \angle 0.7^\circ \text{ V} \end{aligned}$$

$$VR = \frac{2455 - 2400}{2400} * 100 = 2.3\%$$

$$P_c = I_c^2 R_c, \quad P_{cu} = I_1^2 R_1 + I_2^2 R_2$$

$$P_c + P_{cu} = 2.18 \text{ kW}, \quad P_{o/p} = 150 * 0.8 = 120 \text{ kW}$$

$$\eta = \frac{120}{120 + 2.18} * 100 = 98.2\%$$

P2

$$aV_2 = 2400 \angle 0^\circ \text{ V}$$

$$\frac{I_2}{a} = 50 - j37.5 \text{ A}$$

$$R_1 + a^2R_2 = 0.4 \ \Omega$$

$$X_1 + a^2X_2 = 0.9 \ \Omega$$

$$\begin{aligned} V_1 &= (2400 + j0) + (50 - j37.5)(0.4 + j0.9) \\ &= 2453 + j30 = 2453 \angle 0.7^\circ \text{ A} \end{aligned}$$

$$I_c = \frac{2453 \angle 0.7^\circ}{10 \times 10^3} = 0.2453 \angle 0.7^\circ \text{ A}$$

$$I_m = \frac{2453 \angle 0.7^\circ}{1550 \angle 90^\circ} = 1.58 \angle -89.3^\circ \text{ A}$$

$$I_0 = 0.2453 - j1.58 \text{ A}$$

$$I_1 = 50.25 - j39.08 = 63.66 \angle -37.9^\circ \text{ A}$$

$$\text{percent regulation} = \frac{2453 - 2400}{2400} \times 100 = 2.2\%$$

$$\begin{aligned} \text{efficiency} &= \frac{120 \times 10^3}{120 \times 10^3 + (63.66)^2(0.4) + (0.2453)^2(10 \times 10^3)} \\ &= 0.982 = 98.2\% \end{aligned}$$

Notice that the approximate circuit yields results that are sufficiently accurate.

P3

$$\frac{O.C}{R'_C} = \frac{(120)^2}{80} = 180 \Omega, \quad a = \frac{450}{120} = 3.75$$

$$R_C = a^2 R'_C = \underline{\underline{2530 \Omega}}$$

$$I'_C = \frac{120}{R'_C} = 0.667 \text{ A} \quad I_m = \sqrt{I_0^2 - I'_C} = 4.15 \text{ A}$$

$$X'_m = \frac{120}{I'_m} = 28.94 \Omega$$

$$X_m = a^2 X'_m = \underline{\underline{407 \Omega}}$$

$$\frac{S.C}{Z_{e1}} = \frac{9.65}{22.2} = 0.435 \Omega$$

$$R_{e1} = \frac{120}{(22.2)^2} = \underline{\underline{0.243 \Omega}}$$

$$X_{e1} = \sqrt{Z_{e1}^2 - R_{e1}^2} = \underline{\underline{0.361 \Omega}}$$

$$I_{IFL} = \frac{10000}{450} = 22.2 \text{ A}$$

$$\text{Voltage Drop} \approx I_1 (R_{e1} \cos \phi + X_{e1} \sin \phi) \approx 9.2 \text{ V}$$

$$VR = \frac{9.2}{450} \times 100 = 2.04 \%$$

$$\eta_{FL} = \frac{10000 \times 0.8}{10000 \times 0.8 + 80 + 120} \times 100 = 97.57 \%$$

at half load

$$\eta = \frac{\frac{1}{2} \times 10000 \times 0.8}{\frac{1}{2} \times 10000 \times 0.8 + 80 + (\frac{1}{2})^2 \times 120} \times 100 = 97.34 \%$$

P3

P4

$$\textcircled{a} \quad I_t = \frac{P_{\text{net}}}{V_t} = \frac{10,000}{250} = 40 \text{ A}$$

$$I_f = \frac{V_t}{R_f} = \frac{250}{125} = 2 \text{ A}$$

$$I_a = I_t + I_f = 40 + 2 = 42 \text{ A}$$

$$E_a = V_t + R_a I_a = 250 + (0.2)(42) = 258.4 \text{ V}$$

$$\textcircled{b} \quad \omega_m = \frac{2\pi n}{60} = \frac{2\pi(1750)}{60} = 183.26 \text{ rad/sec}$$

$$P_{\text{dev}} = E_a I_a = (258.4)(42) = 10,852.8 \text{ W}$$

$$T_e = \frac{P_{\text{dev}}}{\omega_m} = \frac{10,852.8}{183.26} = 59.2 \text{ N-m}$$

$$\textcircled{c} \quad VR = \frac{E_a - V_t}{V_t} \times 100 = \frac{258.4 - 250}{250} \times 100 = 3.36\%$$


$$\textcircled{d} \quad P_{\text{cu}} = I_a^2 R_a + I_f^2 R_f = (42)^2(0.2) + (2)^2(125) = 852.8 \text{ W}$$

$$P_{\text{out}} = 10,000 \text{ W}$$

$$P_{\text{in}} = P_{\text{out}} + P_{\text{cu}} + P_{\text{rotational}} = 10,000 + 852.8 + 450 = 11,302.8 \text{ W}$$

$$\eta = \frac{P_{\text{out}}}{P_{\text{in}}} = \frac{10,000}{11,302.8} \times 100\% = 88.5\%$$

P5


 The no Load Saturation curve for a speed of 1500 rpm
 a)
$$\frac{E_1}{E} = \frac{K_a \phi_p \omega_{m1}}{K_a \phi_p \omega_m} \Rightarrow E = E_1 \frac{\omega_m}{\omega_{m1}}$$

$$E = E_1 \frac{1500}{1800}$$

(for a given field current the speed affects E proportionally $E \propto \text{speed}$)

(V) E	6.67	33.33	61.67	94.17	126.7	177.5	195	206.7	221.7	231.7
(A) I_f	0	0.5	1.0	1.5	2.0	3.0	3.5	4.0	5.0	6.0

Both Plots are attached

b) when $I_f = 4.6 \text{ A}$, $E = 215 \text{ V}$ at 1500 rpm.
 taken from the graph

$$E \text{ at } 1000 \text{ rpm is } 215 \times \frac{1000 \text{ rpm}}{1500} = 143.33 \text{ V}$$

c) For a given field current, $E = 120 \text{ V}$ at 900 rpm.
 This is equivalent to $E = 120 \times \frac{1500}{900} = 200 \text{ V}$ at 1500 rpm.
 From the graph the corresponding field current is 3.75 Amp.

OCC

