

**King Fahd University of Petroleum & Minerals**  
Electrical Engineering Department


**EE-360 Problem session #2, 2014, 132**

**Problem 1:**

A 24-kVA, 60-Hz, 2400/240-V distribution transformer is to be reconnected for use as an autotransformer. Determine the following for step-up and step-down connections:

- The primary winding voltage
- The secondary winding voltage
- The ratio of transformation
- The nominal rating of the autotransformer

\* Step-up autotransformer

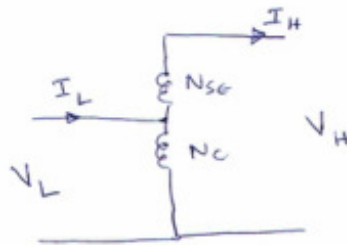


(a)  $V_p = V_L = 2400\text{V}$

(b)  $V_s = V_H = 2400 + 240 = 2640\text{V}$

(c)  $a = \frac{2400}{2640} = 0.91$

(d)  $S_{10} = V_H I_H = 2640 \times \frac{24\text{ kVA}}{240} = 2640 \times 100 = 264\text{ kVA}$

\* Step-down autotransformer

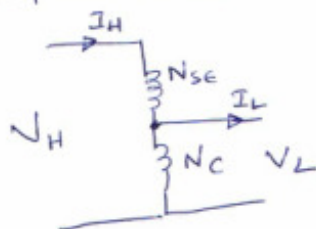

(a)  $V_p = V_H = 240 + 2400 = 2640\text{V}$

(b)  $V_s = V_L = 2400\text{V}$

(c)  $a = \frac{2640}{2400} = 1.1$

(d)  $S_{10} = V_L I_L = 2400 \left( \frac{I_{sc}}{240} + \frac{I_c}{2400} \right) = 2400 \times 110 = 264\text{ kVA}$

**Problem 2:**

A 150-kVA wye-delta connected step down transformer has an input line-voltage of 4160-V and an output line voltage of 240-V

- Draw the winding arrangements and its equivalent wye-wye representation
- Determine the transformer ratio
- Determine the rated line and phase currents for the high side
- Determine the rated line and phase currents for the low side

a)

b)

$$a = \frac{V_{\phi P}}{V_{\phi S}} = \frac{4160/\sqrt{3}}{240} = 10$$

c)

$$S = \sqrt{3} V_{LP} I_{LP}$$

$$I_{LP} = \frac{150 \text{ kVA}}{\sqrt{3} \times 4160} = 20.8 \text{ A}$$

$$I_{\phi P} = I_{LP} = 20.8 \text{ A}$$

d)

$$S = \sqrt{3} V_{LS} I_{LS}$$


$$I_{LS} = \frac{150 \text{ kVA}}{\sqrt{3} \times 240} = 360.8 \text{ A}$$

$$I_{\phi S} = \frac{I_{LS}}{\sqrt{3}} = \frac{360.8}{\sqrt{3}} = 208.3 \text{ A}$$

**Problem 3:**

A 20 hp, 240 V shunt DC motor has an armature resistance of 0.1 Ω. The motor's field resistance is 240 Ω. At no load, the motor draws 5 A from the source and produces a no-load speed of 1800 rpm. When delivering the rated horse power, the motor draws 69.1 A from the source.

- Calculate the motor speed regulation.
- Calculate the converted power and the corresponding induced torque.
- Find the rotational losses and the motor efficiency

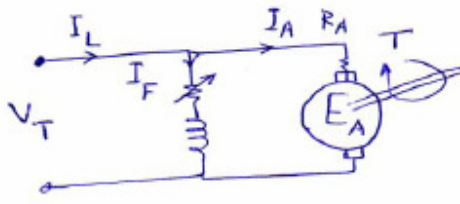a) 

$$P_{out} = 20 \text{ hp} = 14.92 \text{ kW}$$

$$V_T = 240 \text{ V}$$

$$R_A = 0.1 \Omega$$

$$R_F = 240 \Omega$$

$$n_{nL} = 1800 \text{ rpm}$$

$$I_{L_{nL}} = 5 \text{ A}$$

$$I_{L_{fl}} = 69.1 \text{ A}$$

b) 
$$SR = \frac{n_{nL} - n_{fl}}{n_{fl}} \times 100\%$$
 At no load  $I_{L_{nL}} = 5 \text{ A}$   

$$I_F = \frac{240}{240} = 1 \text{ A}, I_{A_{nL}} = 5 - 1 = 4 \text{ A}$$

$$E_{A_{nL}} = V_T - I_{A_{nL}} R_A = 240 - (4)(0.1) = 239.6 \text{ V}$$
 At rated load  $E_{A_{fl}} = V_T - I_{A_{fl}} R_A, I_{A_{fl}} = 69.1 - 1 = 68.1 \text{ A}$   
 so 
$$E_{A_{fl}} = 240 - (68.1)(0.1) = 240 - 6.81 = 233.19 \text{ V}$$

$$n_{fl} = \frac{E_{A_{fl}}}{E_{A_{nL}}} n_{nL} = \frac{233.19}{239.6} \times 1800 = 1752 \text{ rpm}$$

$$SR = \frac{1800 - 1752}{1752} \times 100\% = 2.74\%$$

c) 
$$P_{con} = E_{A_{fl}} \times I_{A_{fl}} = 233.19 \times 68.1 = 15.88 \text{ kW}$$

$$T_{in} = \frac{P_{con}}{\omega_{fl}} = \frac{15.88 \times 10^3}{\frac{2\pi(1752)}{60}} = 86.55 \text{ N.m}$$


$$P_{rot} = P_{con} - P_{out} = 15.88 - 14.92 \text{ kW} = 960 \text{ W}$$

$$\eta = \frac{P_{out}}{P_{in}} \times 100\% = \frac{14.92 \times 10^3}{240 \times 69.1} \times 100 = 90\%$$

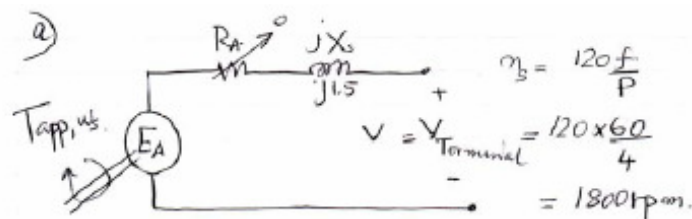**Problem 4:**

A 25-kVA, 230-V, three-phase, 60-Hz, four-pole, Y-connected synchronous generator has a synchronous reactance of  $1.5 \Omega$  per phase and negligible armature resistance

- Draw the single phase equivalent circuit and determine the synchronous speed
- Find the excitation voltage ( $E_A$ ) and the power angle ( $\delta$ ) if the generator is delivering rated kVA at 0.8 PF lagging
- The field current is increased by 20 % without changing the input power from the prime mover. Find the armature current, the power factor, and the reactive power supplied by the machine



$$b) P_{\text{out}} = 25 \times 0.8 = 20 \text{ kW}$$

$$I_a = \frac{P}{\sqrt{3} V \cos \phi} \angle -\cos^{-1} \text{PF} = \frac{20 \times 10^3}{\sqrt{3} \times 230 \times 0.8} \angle -\cos^{-1} 0.8$$

$$= 62.76 \angle -36.9^\circ \text{ A}$$

$$E_a = V + I_a * jX_s = \frac{230}{\sqrt{3}} + 62.76 \angle -36.9^\circ * 1.5 \angle 90^\circ$$

$$= 132.8 + 94.14 \angle 53.1^\circ = 189.3 + j75.28$$

$$= 203.7 \angle 21.69^\circ \text{ V}$$

$$E_{\text{apt}} = 203.7 \text{ V}, \quad \delta = 21.69^\circ$$

$$c) |E_{a2}| = 1.2 * |E_a| = 244.44 \text{ V}$$

$$E_{a2} \sin \delta_2 = E_a \sin \delta \Rightarrow \delta_2 = 17.94^\circ$$

$$I_a = \frac{244.44 \angle 17.94^\circ - 132.8}{j1.5} = 50.2 - j66.5$$

$$= 83.3 \angle -52.95^\circ, \quad \text{PF} = 0.6 \text{ lagging}$$

$$Q = \sqrt{3} V I_a \sin \phi = 26.55 \text{ KVAR}$$

$$\text{or } Q = \frac{3V}{X_s} (E_{\text{cos} \delta} - V) = 26.5 \text{ KVAR}$$