

Three-phase circuits

Problem 4 :


$$\bar{V}_{an} = 120 \angle 0^\circ \Rightarrow V_{ab} = \sqrt{3} 120 \angle 30^\circ$$

$$\bar{V}_{ab} = 208 \angle 30^\circ \text{ V}$$

$$\bar{V}_{bc} = 208 \angle -90^\circ \text{ V}$$

$$\bar{V}_{ca} = 208 \angle +150^\circ \text{ V}$$

Phase
Voltages

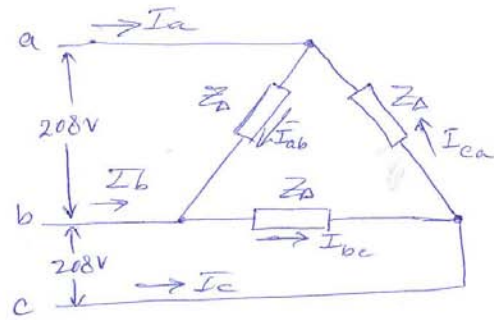

$$(a) \left. \begin{aligned} \bar{I}_{ab} &= \frac{\bar{V}_{ab}}{Z_p} = \frac{208 \angle 30^\circ}{20 \angle -30^\circ} = 10.4 \angle 60^\circ \text{ A} \\ \bar{I}_{bc} &= \frac{\bar{V}_{bc}}{Z_p} = \frac{208 \angle -90^\circ}{20 \angle -30^\circ} = 10.4 \angle -60^\circ \text{ A} \\ \bar{I}_{ca} &= \frac{\bar{V}_{ca}}{Z_p} = \frac{208 \angle 150^\circ}{20 \angle -30^\circ} = 10.4 \angle 180^\circ \text{ A} \end{aligned} \right\} \text{ phase currents}$$

$$(b) \left. \begin{aligned} \bar{I}_a &= \sqrt{3} \bar{I}_{ab} \angle -30^\circ = \sqrt{3} 10.4 \angle 60^\circ - 30^\circ = 18 \angle 30^\circ \text{ A} \\ \bar{I}_b &= 18 \angle -90^\circ \text{ A} \\ \bar{I}_c &= 18 \angle 150^\circ \text{ A} \end{aligned} \right\} \text{ line currents}$$

$$(c) \text{ PF} = \cos(-30^\circ) = 0.866 \text{ (leading)}$$

$$(d) S_{3\phi} = 3 V_{ph} \cdot I_{ph} = \sqrt{3} V_L I_L = \sqrt{3} 208 \times 18 = 6485 \text{ VA}$$

$$P_{3\phi} = 3 V_{ph} \cdot I_{ph} \cdot \cos \phi = \sqrt{3} V_L I_L \cos \phi = 3 \times 208 \times 10.4 \times 0.866$$

$$P_{3\phi} = 5.616 \text{ kW}$$

$$Q_{3\phi} = \sqrt{S_{3\phi}^2 - P_{3\phi}^2} = 3.243 \text{ kVAR}$$

Problem 2

$$\text{Load \#1} \\ \underline{Z}_{\Delta} = 10 \angle 30^{\circ} \Omega/\text{ph} = 8.66 + j5 \Omega/\text{ph}$$

$$\Delta-Y \text{ trans.} \quad \underline{Z}_{Y1} = 2.887 + j1.667 = 3.333 \angle 30^{\circ} \Omega/\text{ph}$$

$$\text{Load \#2} \quad \underline{Z}_{Y2} = 5 \angle -36.87^{\circ} = 4 - j3 \Omega/\text{ph}$$

$$\underline{Z}_t = \underline{Z}_{Y1} \parallel \underline{Z}_{Y2} = \frac{16.665 \angle -6.87}{6.887 - j1.333} = \frac{16.665 \angle -6.87}{7.015 \angle -10.954} \\ = 2.376 \angle 4.084 \Omega/\text{ph}$$

a) the overall power factor = $\cos(4.084) = 0.997$ lagging

b) the total current supplied = $\frac{V_{\text{ph}}}{Z_t} = \frac{480/\sqrt{3}}{2.376} = 116.64 \text{ A}$

c) $P_t = \sqrt{3} V_L I_L \cos \phi = \sqrt{3} * 480 * 116.64 * 0.997$
 $= 9.668 \text{ KW}$

$$Q_t = \sqrt{3} V_L I_L \sin \phi = \sqrt{3} * 480 * 116.64 * \sin(4.084) =$$

 $= 6.906 \text{ KVAR}$

$$S_t = \sqrt{3} V_L I_L = \sqrt{3} * 480 * 116.64$$

 $= 9.697 \text{ KVA}$

Problem 3

$$Z_{ph} = 20 + j15 \Omega = 25 \angle 36.87^\circ$$

$$V_{ph} = \frac{400}{\sqrt{3}} \angle 0^\circ = 231 \angle 0^\circ$$

$$a) I_{ph} = I_L = \frac{V_{ph}}{Z_{ph}} = \frac{231 \angle 0^\circ}{25 \angle 36.87^\circ} = 9.24 \angle -36.87^\circ$$

$$b) P = \sqrt{3} * V_L I_L \cos 36.87^\circ = \sqrt{3} * 400 * 9.24 * 0.8 = 5120 \text{ W}$$

$$Q = \sqrt{3} V_L I_L \sin 36.87^\circ = \sqrt{3} * 400 * 9.24 * 0.6 = 3840 \text{ VAR}$$

When the capacitor bank is connected

$$P_{new} = 0.95 ; \phi_{new} = 18.19^\circ ; \tan \phi_{new} = 0.3286$$

real Power remains constant

$$Q_{new} = P \tan \phi_{new} = 1682 \text{ VAR}$$


$$Q_c = Q - Q_{new}$$

$$Q_c = 3840 - 1682 = 2158 \text{ VAR}$$

$$Q_{cph} = \frac{2158}{3} = 719.3 \text{ VAR}$$

$$Q_{cph} = \frac{V_L^2}{X_c} \rightarrow X_c = \frac{V_L^2}{Q_{cph}} = \frac{(400)^2}{719.3} = 222.44 \Omega = \frac{1}{\omega C}$$


$$C = \frac{1}{2\pi * 50 * 222.44} = 14.31 \mu\text{F}$$

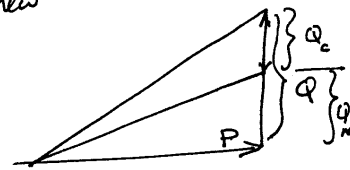

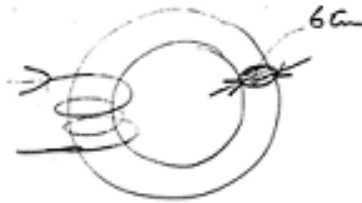Problem 4

$$l = \pi d_m = \pi \times 25 = 78.64 \text{ cm}$$

$$A = \pi \times \frac{(6)^2}{4} = 28.27 \text{ cm}^2$$



a) $B = \frac{1.7 \times 10^{-3}}{28.27 \times 10^{-4}} = 0.6 \text{ T}$

From table $H = 600 \text{ AT/m}$

so $NI = Hl$ $I = \frac{600 \times 78.64 \times 10^{-2}}{600}$

$I = \underline{\underline{0.7864 \text{ A}}}$

b) Same Φ and B
 $H_c = 600 \text{ AT/m}$

$l_c = 78.64 \text{ cm}$

$H_g = \frac{B}{\mu_0} = \frac{0.6}{4\pi \times 10^{-7}} = 477.5 \times 10^3 \text{ AT/m}$

$l_g = 2 \times 10^{-3} \text{ m}$

$NI = H_g l_g + H_c l_c = 1427 \text{ AT}$

$I = \underline{\underline{2.378 \text{ A}}}$



Problem 5

$$\phi_c = 0.36 \text{ mWb}$$

$$B_c = \frac{\phi_c}{A} = \frac{0.36 \times 10^{-3}}{4 \times 10^{-4}} = 0.9 \text{ Wb/m}^2$$

$$H_c = 150 \text{ AT/m (From B-H Curve)}$$

$$\begin{aligned} \therefore AT_{ab} &= H_c l_c = 150 \times 0.06 = 9 \text{ AT} \quad (l_c = 4+1+1 = 6 \text{ cm}) \\ &= H_r l_r = H_r \times (6+6+6) \times 10^{-2} \end{aligned}$$

$$\therefore H_r = \frac{9}{18 \times 10^{-2}} = 50 \text{ AT/m}$$

$$\therefore B_r \text{ (Corresponding Value from B-H Curve)} = 0.35 \text{ Wb/m}^2$$

$$\therefore \phi_r = B_r A_r = 0.35 \times 4 \times 10^{-4} = 0.14 \text{ mWb}$$

$$\therefore \phi_2 = \phi_c + \phi_r = 0.36 + 0.14 = 0.5 \text{ mWb}$$


$$\therefore B_2 = \frac{\phi_2}{A} = \frac{0.5 \times 10^{-3}}{4 \times 10^{-4}} = 1.25 \text{ Wb/m}^2$$

$$\therefore H_2 = 500 \text{ AT/m (from B-H Curve) .}$$

$$\therefore H_2 l_2 = 500 \times (6+6+6) \times 10^{-2} = 90 \text{ ATs}$$

$$\begin{aligned} \therefore \sum \mathcal{F} &= H_2 l_2 + H_c l_c = 90 + 9 = 99 \text{ ATs} \\ &= NI \end{aligned}$$

$$\therefore I = \frac{99}{300} = 0.33 \text{ Amps}$$

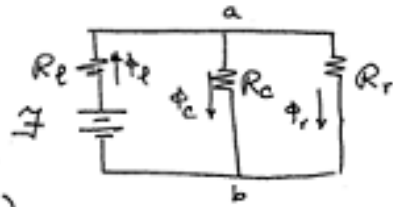

Problem 6

$$g_c = 1 \text{ mm} ; g_A = 2 \text{ mm}, A = (5 \times 5) = 25 \text{ cm}^2 = 25 \times 10^{-4} \text{ m}^2$$

$$N = 200 \text{ turns}, R = 2.5 \Omega$$

$$\textcircled{a} R_c = \frac{g_c}{\mu_0 A} = \frac{1 \times 10^{-3}}{(4\pi \times 10^{-7})(25 \times 10^{-4})} = 318,310 \text{ At/Wb}$$

$$\phi_c = BA = (0.75)(25 \times 10^{-4}) = 1.875 \times 10^{-3} \text{ Wb}$$

$$NI = R_c \phi_c = (318,310)(1.875 \times 10^{-3}) = 596.83 \text{ At}$$

$$I = \frac{596.83}{200} = 2.984 \text{ A}$$

$$V = RI = (2.5)(2.984) = 7.46 \text{ V}$$

$$\textcircled{b} R_A = \frac{g_A}{\mu_0 A} = \frac{2 \times 10^{-3}}{(4\pi \times 10^{-7})(25 \times 10^{-4})} = 636,620 \text{ At/Wb}$$

$$\phi_A = \frac{NI}{R_A} = \frac{596.83}{636,620} = 9.375 \times 10^{-4} \text{ Wb}$$

$$\phi_B = \phi_A + \phi_c = 9.375 \times 10^{-4} + 1.875 \times 10^{-3} = 2.8125 \times 10^{-3} \text{ Wb}$$