

# KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

## ELECTRICAL ENGINEERING DEPARTMENT

Dr. Ibrahim Omar Habiballah

EE-306 (141)

### Key Solutions

Quiz 1      Sec.: 3      Serial:      I.D.:      Name:

Q.1 Three-phase 230-V source is connected to a delta-connected load. The per-phase impedance of the load is  $3 + j4$  Ohm. The phase and line currents of the load are

- a.  $I_{ph} = 46.0 \angle -23.13^\circ \text{ A}$  ;  $I_{Line} = 79.7 \angle -53.13^\circ \text{ A}$
- b.  $I_{ph} = 46.0 \angle -23.13^\circ \text{ A}$  ;  $I_{Line} = 46.0 \angle -23.13^\circ \text{ A}$
- c.  $I_{ph} = 79.7 \angle -53.13^\circ \text{ A}$  ;  $I_{Line} = 79.7 \angle -53.13^\circ \text{ A}$
- d.  $I_{ph} = 46.0 \angle -53.13^\circ \text{ A}$  ;  $I_{Line} = 79.7 \angle -83.13^\circ \text{ A}$

Q.2 Three-phase 230-V source is connected to a delta-connected load. The per-phase impedance of the load is  $3 + j4$  Ohm. The phase and line voltages of the load are

- a.  $V_{ph} = 132.7 \angle 0^\circ \text{ V}$  ;  $V_{Line} = 230 \angle 30^\circ \text{ V}$
- b.  $V_{ph} = 132.7 \angle 0^\circ \text{ V}$  ;  $V_{Line} = 132.7 \angle 0^\circ \text{ V}$
- c.  $V_{ph} = 230 \angle 30^\circ \text{ V}$  ;  $V_{Line} = 230 \angle 30^\circ \text{ V}$
- d. none of the above