

Q1)

$$0 < t < \frac{1}{60} \text{ sec}$$

$$e = N \frac{d\Phi}{dt} = 400 \times \frac{1.2 \times 10^{-3}}{\frac{1}{60}} = 28.8 \text{ V}$$

$$\frac{1}{60} < t < \frac{2}{60} \text{ sec}$$


$$e = N \times 0 = 0$$

$$\frac{2}{60} < t < \frac{4}{60} \text{ sec}$$

$$e = -400 \times \frac{2 \times 1.2 \times 10^{-3}}{\frac{2}{60}} = -28.8 \text{ V}$$

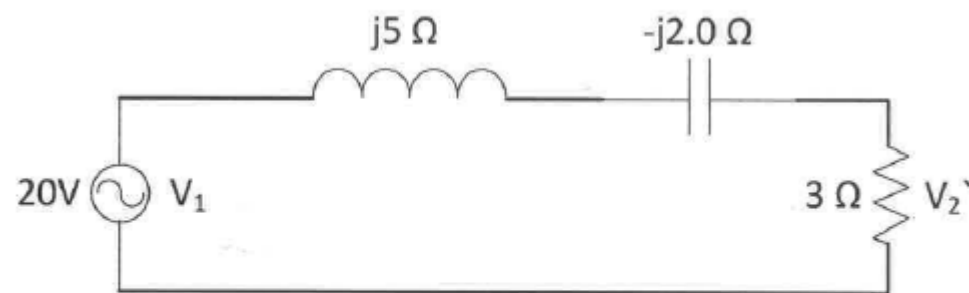Q2)

The equivalent circuit referred to the primary side is:



Impedance of the circuit,

$$Z = 3 + j5 - j20 = 3 + j3 = 4.24 \Omega$$

$$I_1 = \frac{20}{4.24} = 4.72 \text{ A}$$

$$V_2' = 4.72 \times 3 = 14.15 \text{ V}$$

$$\text{Actual load voltage } V_2 = 100 \times 14.15 = 1415 \text{ V}$$

Q3)

$$\begin{aligned} \text{(a) } V_H(\text{rated}) &= 1000\text{V}, \quad I_H(\text{rated}) = \frac{100 \times 10^3}{1000} = 100\text{A}. \\ V_L(\text{rated}) &= 100\text{V}, \quad I_L(\text{rated}) = \frac{100 \times 10^3}{100} = 1000\text{A} \end{aligned}$$

(b) From open circuit test,

$$R_{CL} = \frac{100^2}{400} = 25\ \Omega.$$

$$I_{CL} = \frac{100}{25} = 4\text{A}.$$

$$I_{mL} = \sqrt{6^2 - 4^2} = 4.47\text{A}$$

$$X_{mL} = \frac{100}{4.47} = 22.37\ \Omega$$

$$\text{Turns ratio } a = \frac{1000}{100} = 10$$

Refer to high voltage side,

$$R_{CH} = 25 \times 10^2 = 2500\ \Omega, \quad X_{mH} = 2237\ \Omega$$


From short circuit test,

$$R_{eqH} = \frac{1800}{100^2} = 0.18\ \Omega.$$

$$Z_{eqH} = \frac{50}{100} = 0.5 \Omega$$

$$X_{eqH} = \sqrt{0.5^2 - 0.18^2} = 0.4665 \Omega$$

Equivalent circuit referred to H.V. side

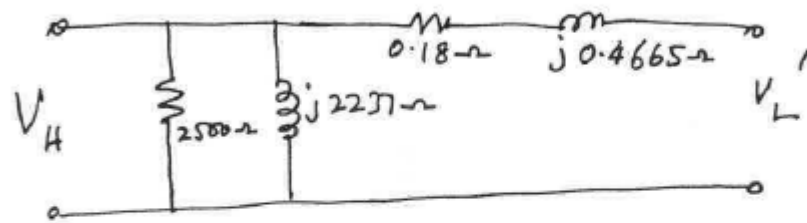


$$(c) V_1 = V_2' + I_2' Z_{eqH}$$


$$= 1000 \angle 0^\circ + 100 \angle 53^\circ (0.18 + j0.4665)$$

$$= 974.4 \angle 2.5^\circ$$
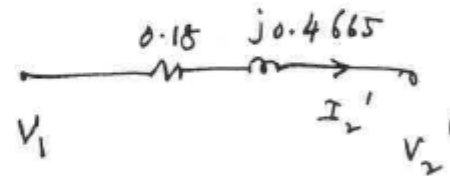
$$V.R = \frac{974.4 - 1000}{1000} \times 100 \% = -2.56 \%$$



(d)

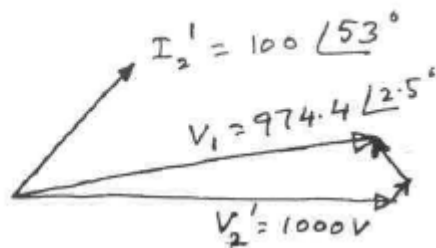

Q4)


$$(a) n = \frac{11}{2.2} = 5$$

$$R_{HV} = 1.3 \Omega, R'_{LV} = 0.05 \times 5^2 = 1.25 \Omega$$

$$X_{HV} = 4.5 \Omega, X'_{LV} = 0.16 \times 5^2 = 4.0 \Omega$$

$$R_{eq(HV)} = 1.3 + 1.25 = 2.55 \Omega, X_{eq(HV)} = 4.5 + 4 = 8.5 \Omega$$
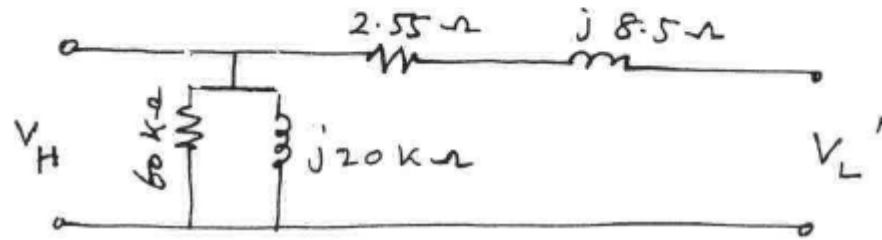
$$R_C(HV) = 2.4 \times 5^2 = 60 k\Omega, X_m(HV) = 0.8 \times 5^2 = 20 k\Omega$$



$$(b) I_0(HV) = \frac{11000}{60000} + \frac{11000}{j20000} = 0.5797 A$$

$$I_{HV(rated)} = \frac{250 \times 10^3}{11 \times 10^3} = 22.73 A$$


$$I_0(HV) = \frac{0.5797}{22.73} pu = 0.0255 pu$$

$$(c) Z_{eq(HV)} = 2.55 + j8.5 = 8.8743 \Omega$$

$$V_{HV} = 22.73 \times 8.8743 = 201.7 V$$

Q5)

(a)

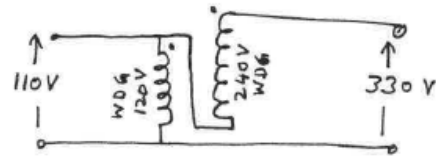

$$(b) I_{HV} = \frac{3000}{240} = 12.5 A$$

$$Rating = (120 + 240) \times 12.5 = 4500 VA = 4.5 kVA$$

Q6)

(a)

$$S_{3\phi} = 3 \times 830 = 2.49 \text{ kVA}$$

$$V_{LP(\Delta)} = V_{\phi\phi} = 240 \text{ V}$$

$$V_{LS(Y)} = \sqrt{3} V_{\phi\phi} = \sqrt{3} \times 120 = 208 \text{ V}$$

