

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

ELECTRICAL ENGINEERING DEPARTMENT

Dr. Ibrahim O. Habiballah

EE-360


Key Solution

Quiz # 7 Serial #

Name:

I.D.#

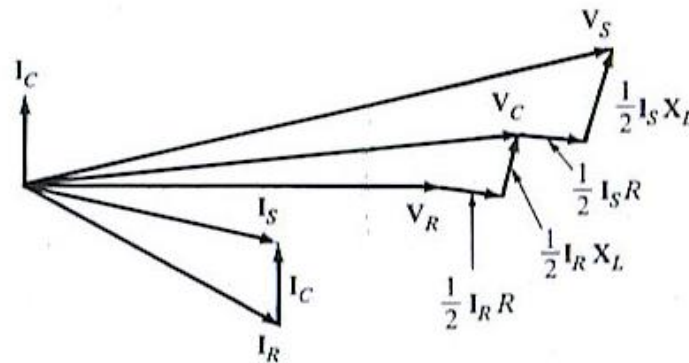1) The figure below shows the phasor diagram of



- a) a short transmission line with lagging power factor load.
- b) a pi-nominal transmission line with lagging power factor load.
- c) a T-nominal transmission line with lagging power factor load.**
- d) a long transmission line with lagging power factor load .

(5 Marks)

2) A 60 Hz, 3-phase, transmission line is 40 miles long with a total series impedance of $(35 + j 140)$ Ohm. It delivers 40 MW at 220 kV and 0.9 power factor lagging. The power factor at the sending end is :

- a. 0.86 leading
- b. 0.48 leading
- c. 0.86 lagging**
- d. 0.48 lagging

(5 Marks)