

# King Fahd University of Petroleum & Minerals

Electrical Engineering Department

Semester-162

EE 306: Electromechanical Devices

## Homework-III (Single-Phase Transformers)

### Problem 1:

A 25-kVA, 2400/240 V, 60 Hz single-phase distribution transformer has been tested for open and short circuit tests as shown in the table below.

Test	Voltage (V)	Current (A)	Power (W)
Open-Circuit (HV Open)	240	3.2	165
Short-Circuit (LV shorted)	55	10.4	375

- Draw the approximate equivalent circuit of this transformer referred to the high-voltage side showing all given and calculated variables.
- When the transformer is delivering full rated KVA at 0.85 power factor lagging determine the voltage regulation and transformer efficiency.
- Determine the maximum efficiency

### Problem-2:

A single-phase power distribution system is shown in Figure 1. The power source feeds a 100-kVA, 14/2.4-kV transformer through a feeder impedance of  $38.2 + j 140 \Omega$ . The transformer's equivalent series impedance referred to its low-voltage side is  $0.10 + j0.40 \Omega$ . The load on the transformer is 90 kW at 0.8 PF lagging and 2400 V.

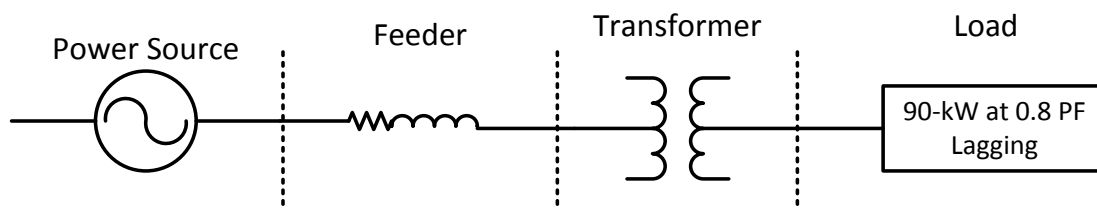


Figure 1: Single-Phase Distribution System

- (a) Deduce and draw single phase equivalent circuit for the power system.
- (b) What is the voltage at the power source of the system?
- (c) What is the voltage regulation of the transformer?
- (d) How efficient is the overall power system?

**Problem-3:**

A 30-kVA, 8000/230-V distribution transformer has equivalent series impedance referred to the primary of  $20 + j100 \Omega$ . The components of the excitation branch referred to the primary side are  $R_c = 100 k\Omega$  and  $X_m = 20 k\Omega$ .

- (a) If the primary voltage is 7967 V and the load impedance is  $Z_L = 2.0 + j0.7 \Omega$ , what is the secondary voltage of the transformer? What is the voltage regulation of the transformer?
- (b) If the load is disconnected and a capacitor of  $-j3.0 \Omega$  is connected in its place, what is the secondary voltage of the transformer? What is the voltage regulation under these conditions?

**Problem-4:**

The resistance and leakage reactance of a 10-KVA, 50-Hz, 2200/220- V distribution transformer are as follows:

$$R_1 = 4 \Omega \quad R_2 = 0.04 \Omega \quad X_1 = 5.0 \Omega \quad X_2 = 0.05 \Omega$$

- (a) Find the total equivalent series impedance referred to, (i) HV side (ii) LV side
- (b) Consider the transformer to deliver its rated KV A at 0.8 PF lagging to a load at rated voltage. Find the HV terminal voltage and percent voltage regulation.
- (c) Repeat part (b) for a PF of 0.8 leading.
- (d) Consider the core loss to be 80 W. Find the efficiency under the conditions of part (b). Will it be different for the conditions under part (c)?