

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

ELECTRICAL ENGINEERING DEPARTMENT

Dr. Ibrahim O. Habiballah

EE-463 - 161

Key Solutions

Quiz 3


ser#:

I.D.:

Name:

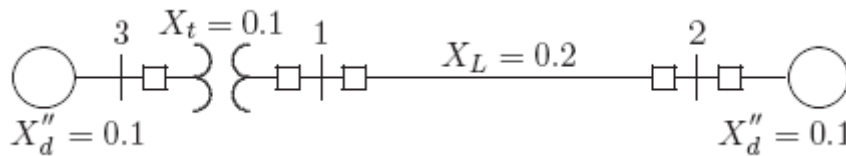Problem # 1

The one-line diagram of a simple power system is shown below. All impedances are expressed in per unit on a common MVA base. The generators are operating on no load at their rated voltage with their emfs in phase. A three-phase fault occurs at bus 1. Assume pre-fault bus voltages as $1.0 \angle 0^\circ$ per-unit. In order to limit the faulted current to $-j5$ pu, the impedance from bus one to the ground must be



- $0.08 \angle 90^\circ$
- $0.08 \angle -90^\circ$
- $0.0 \angle 0^\circ$ (i.e., solidly grounded)
- Cannot be found unless the connection types (wye/delta) are provided for all components.

Problem # 2

A solidly wye-connected generator has its terminal "a" open and the other two terminals are connected to each other with a short circuit to ground. The typical values for the symmetrical components of phase "a" current are $I_{a1} = 600 \angle -90^\circ$ A, $I_{a2} = 250 \angle 90^\circ$ A, and $I_{a0} = 350 \angle 90^\circ$ A. The current that flow in the generator's neutral is.

- a. $904.1 \angle 144.5^\circ$
- b. $904.1 \angle 35.5^\circ$
- c. $1050 \angle 90^\circ$**
- d. $0.0 \angle 0^\circ$