

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
ELECTRICAL ENGINEERING DEPARTMENT
Dr. Ibrahim O. Habiballah
EE-465

Key Solution


Quiz # 2 Serial #

Name:

I.D.#

Circle the correct answer.

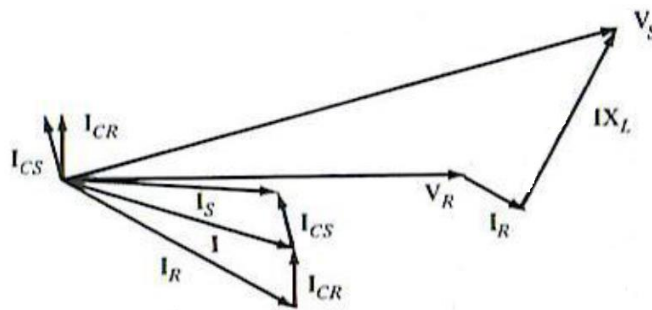1) The phasor diagram below is for: (1 point)



- a. short T.L. connected to an inductive load.
- b. medium Pi-model T.L. connected to an inductive load.**
- c. medium T-model T.L. connected to an inductive load.
- d. long T.L. connected to a capacitive load

2) An important feature of ABCD constants in any T.L. modeling is: (1 point)

- a. $A*B - C*D = 1$.
- b. $A*B - C*D = 0$.
- c. $A*D - B*C = 1$.**
- d. $A*D - B*C = 0$.

3) The no-load receiving-end voltage for short T.L. is the sending-end voltage: (1 point)

- a. True**
- b. False

4) The no-load receiving-end voltage for medium T.L. is the sending-end voltage: (1 point)

- a. True**
- b. False

5) The thermal limit of a 4-bundled 1,272,000 cmil ACSR with 54/3 stranding is: (2 points)

- a. 0.3 kA
- b. 1.2 kA
- c. 4.8 kA**

6) The equivalent Pi-model of long T.L. is similar in structure to the Pi-model of medium T.L., but their ABCD constants are different. (1 point)

- a. True
- b. False

7) The value of maximum power of lossy lines is larger than the maximum power of lossless lines (1 point)

- a. True
- b. False

8) The distance between a 3-phase source with $V_S=1.0\angle 35^\circ$ pu and a load with $V_R=0.95\angle 0^\circ$ pu is 500 km. It is required to deliver 9000 MW on a lossless line between the source and the load. How many 3-phase, 60-Hz lines required to transmit this power (**with one line out of service**) when the line is 500 kV, $Z_c = 277$ Ohm. (2 points)

- a. 10.
- b. 11.
- c. 12.