

## **Homework 4 - SOLUTION KEY**

**EE-306 – Electromechanical Devices - Semester 162**

## Problem 1

A four-pole DC machine has a wave winding of 300 turns. The flux per pole is 0.025 Wb. The DC machine rotates at 1000 rpm.

- Determine the machine constant,
- Determine the generated voltage,
- Determine the kW rating if the rated current through the turn is 25 A.

### Solution

Handwritten solution for Problem 1:

Given:  $N = 300$ ,  $p = 4$ ,  $a = 2$ ,  $\phi = 0.025 \text{ Wb}$

(a) 
$$K_a = \frac{NP}{\pi a} = \frac{300 \times 4}{\pi \times 2} = 190.99$$

(b) 
$$E_a = 190.99 \times 0.025 \times \frac{1000}{60} \times 2\pi$$
  
$$E_a = 500 \text{ V}$$

(c) 
$$I_a = 2 \times 25 = 50 \text{ A}$$
  
$$P = 500 \times 50 = 25 \text{ kW}$$

## Problem 2

A separately excited DC generator has six poles and is running at 1150 rpm. The armature has 120 slots with 8 conductors per slot and is connected as **wave winding**. The generated voltage in each conductor is 1.5 V and each conductor can carry a full load current of 4 A. Determine the following:

- The terminal voltage at no load,
- The output current at full load,
- The required flux per pole,
- The power developed by the armature on full load.

## Solution

$$P = 6, Z = 120 \times 8 = 960$$

$$E_g = 1.5 \text{ V/Conductor}$$

$$I_{\text{Conductor}} = 4 \text{ A}, N = 1150 \text{ rpm}$$

$$a = 2 \text{ (Wave winding)}$$

$$\text{No. of conductors per path} = \frac{960}{2} = 480$$

$$\text{Induced emf per path} = 480 \times 1.5 = 720 \text{ V}$$

(a) No-load terminal voltage = 720V

(b) The output current at full load = 8A

(c) 
$$\phi = \frac{E_a \times 60 \times a}{P Z N} = \frac{720 \times 60 \times 2}{6 \times 960 \times 1150}$$

$$\phi = 13.04 \text{ mWb}$$

(d) 
$$P_d = E_a I_a = 720 \times 8$$

$$P_d = 5.76 \text{ kW}$$

## Problem 3

### Part (a)

A self excited DC shunt generator (20 kW, 200 V, 1800 rpm) has  $R_a = 0.1 \Omega$ ,  $R_{fw} = 150 \Omega$ . Assume that  $E_a = V_t$  at no load. Data for the magnetization curve at 1800 rpm are:

$I_f$ (A)	0.0	0.125	0.25	0.5	0.625	0.75	0.857	1.0	1.25	1.5
$E_a$ (V)	5	33.5	67	134	160	175	190	200	214	223

- Determine the maximum generated voltage,
- At full-load condition,  $V_t = V_t(\text{rated})$ ,  $I_a = I_a(\text{rated})$ , If  $I_f = 1.25 \text{ A}$ . Determine the value of the field control resistance  $R_{fc}$ ,
- Determine the electromagnetic power and torque developed at full-load condition.


**Solution**

(a)  $E_a|_{\max}$  will occur at  $R_{fc} = 0$

Draw field resistance line for

$$R_f = R_{fw} = 150 \Omega$$

$$E_a(\max) = 222 \text{ V}$$

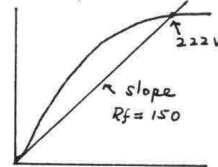


(b)  $I_a(\text{rated}) = \frac{20,000}{200} = 100 \text{ A}$

$$V_t(\text{rated}) = 200 \text{ V}$$

$$R_f = \frac{200}{1.25} = 160 \Omega$$

$$R_{fc} = 160 - 150 = 10 \Omega$$

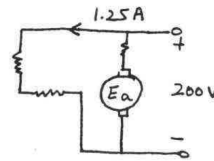

(c)  $E_a = V_t + I_a R_a = 200 + 100 \times 0.1 = 210 \text{ V}$

$$P_{dc} = E_a I_a = 210 \times 100 = 21000 \text{ W}$$

$$\omega_m = \frac{1800}{60} \times 2\pi = 188.5 \text{ rad./sec.}$$

$$T = \frac{E_a I_a}{\omega_m} = \frac{21000}{188.5} = 111.41 \text{ N.m}$$

**Part (b)**

Suppose that the shunt generator is now connected as a long-shunt compound generator. If the full-load terminal voltage,  $V_t = 200 \text{ V}$ , and resistance of the series field windings is  $0.04 \Omega$ .

- (a) Determine the generated voltage,
- (a) Draw the long-shunt generator circuit diagram and label it.

**Solution**


(a)

$$E_a = V_t + I_a(R_a + R_{sr})$$

$$E_a = 200 + 100(0.1 + 0.04)$$

$$E_a = 214 \text{ V}$$

(b)

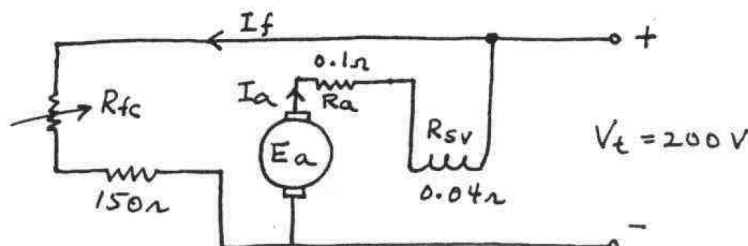

## Problem 4

A 240 V DC shunt motor has an armature resistance of  $0.05 \Omega$ . When the motor is connected to its supply, the armature current is 20 A, the field current is 12 A, and the speed is 1200 rpm. Now, a load is applied to the shaft, and the armature current increases to 300 A and the speed drops to 1150 rpm. Determine the following for the loaded condition,

- (a) Rotational loss,
- (b) Field circuit loss,
- (c) Efficiency at the loaded condition.

### Solution

(a) From no-load condition, rotational loss is:

$$P_{rot} = E_a I_a = (240 - 20 \times 0.05) \times 20 = 4780 \text{ W}$$

This can be assumed constant if the speed variation is small.

(b)  $P_f = 240 \times 12 = 2880 \text{ W}$

(c)  $P_a = E_a I_a = (240 - 300 \times 0.05) \times 300 = 67500 \text{ W}$

$$P_{out} = 67500 - 4780 = 62720 \text{ W}$$
$$P_a = 240 \times 300 = 72000 \text{ W}$$
$$P_{in} = P_a + P_f = 74880 \text{ W}$$
$$\eta = \frac{62720}{74880} \times 100$$

$$\eta = 83.8 \%$$



**Solution**

Given:-  $V_t = 220V$  DC shunt motor


$$R_a = 0.2\Omega \quad R_{sh} = 110\Omega$$

No-load Data:-  $n_{m,NL} = 1000 \text{ rpm}$


$$I_{L,NL} = 7A$$

Full-load Data:-  $P_{in,FL} = 11 \text{ kW}$

Equivalent circuit

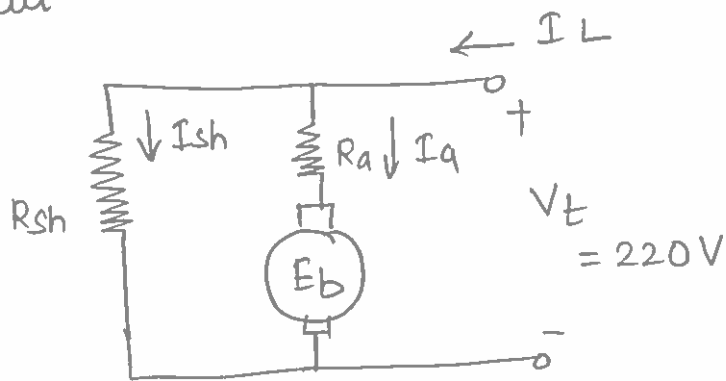

Power-flow diagram under No-load

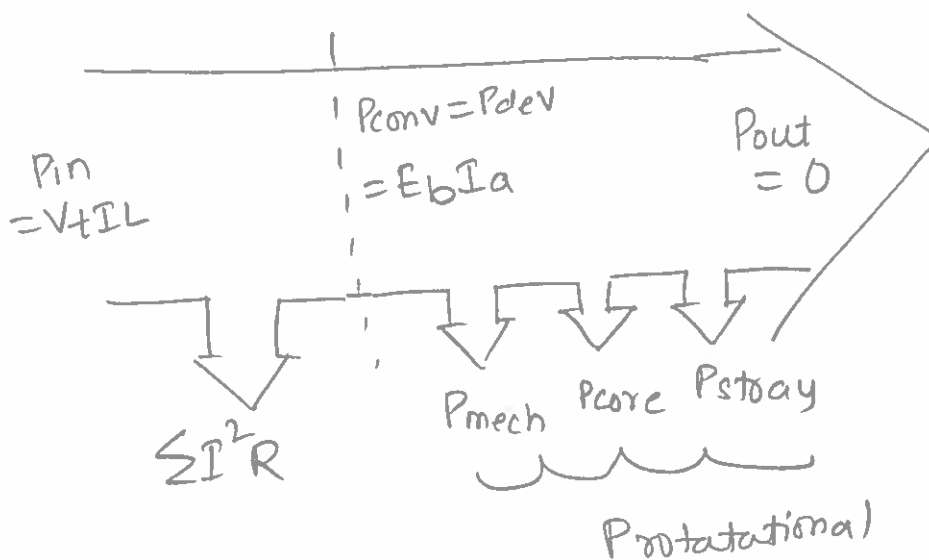

From the Power-flow diagram,

$$P_{\text{rotational}} = P_{\text{in, NL}} - \sum I^2 R \text{ losses} \quad (\text{OR})$$

$$P_{\text{rotational}} = P_{\text{conv}} = P_{\text{dev}} = E_{b, \text{NL}} I_{a, \text{NL}}$$

∴ To find  $E_{b, \text{NL}}$

$$I_{L, \text{NL}} = 7 \text{ A}$$

$$I_{\text{sh, NL}} = \frac{V_t}{R_{\text{sh}}} = \frac{220}{110} = 2 \text{ A}$$

$$I_{a, \text{NL}} = I_{L, \text{NL}} - I_{\text{sh, NL}} = 7 - 2 = 5 \text{ A}$$

Now by KVL,

$$E_{b, \text{NL}} = V_t - I_{a, \text{NL}} R_a - V_{B\beta 1} - V_{B\beta 2}$$

$$= 220 - 5(0.2) - 0$$

$$E_{b, \text{NL}} = 219 \text{ V}$$

$$\text{Now } P_{\text{rotational}} = E_{b, \text{NL}} \cdot I_{a, \text{NL}}$$

$$= 219 \times 5$$

$$P_{\text{rotational}} = 1095 \text{ W}$$



To find Speed under full-load condition

At Full-load :- given  $P_{in,FL} = 11 \text{ kW}$

$$\text{From, } I_{L,FL} = \frac{P_{in,FL}}{V_t}$$

$$I_{L,FL} = \frac{11 \times 10^3}{220} = 50 \text{ A}$$

$$I_{sh,FL} = \frac{V_t}{R_{sh}} = \frac{220}{110} = 2 \text{ A}$$

$$I_a,FL = I_{L,FL} - I_{sh,FL} = 50 - 2 = 48 \text{ A}$$

Now,

$$\begin{aligned} E_{b,FL} &= V_t - I_a,FL \cdot R_a - V_{B71} - V_{B72} \\ &= 220 - 48 \times 0.2 - 0 \end{aligned}$$

$$E_{b,FL} = 210.4 \text{ V}$$

From the induced emf equation,

$$E_b = K_a \phi \omega_m$$

For no-load condition,  $E_{b,NL} = K_a \phi_{NL} \omega_{m,NL}$

For full-load condition,  $E_{b,FL} = K_a \phi_{FL} \omega_{m,FL}$

In a DC shunt machine, since the field current remains constant thereby the flux in the machine also remain constant.

$$\therefore \phi_{NL} = \phi_{FL}$$

Now,

$$\frac{E_{b,FL}}{E_{b,NL}} = \frac{\omega_{m,FL}}{\omega_{m,NL}}$$

$$\Rightarrow \omega_{m,FL} = \omega_{m,NL} \cdot \frac{E_{b,FL}}{E_{b,NL}}$$

$$= 1000 \times \frac{210.4}{219}$$

$$\boxed{n_{m,FL} = 960.73 \text{ rpm}}$$

Now, Speed regulation,

$$= \frac{n_{m,NL} - n_{m,FL}}{n_{m,FL}} \times 100$$

$$= \frac{1000 - 960.73}{960.73} \times 100$$

$$\boxed{SR = 4.1\%}$$