

# KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

## ELECTRICAL ENGINEERING DEPARTMENT

Dr. Ibrahim O. Habiballah

EE520 -171

Quiz 1            ser#:            I.D.:            Name:

Q.1 A 40-MVA, 400-kV/20-kV, single-phase transformer has the following series impedances:  $0.9 + j1.8$  Ohm (referred to the low-voltage side) and  $40 + j80$  Ohm (referred to the high-voltage side). Using the transformer ratings as the selected bases, determine the per unit equivalent impedance of the transformer referred to the low-voltage side.            (3 points)

- a.  $400 + j 800$
- b.  $4.0 + j 8.0$
- c.  $1.0 + j 2.0$
- d.  $0.10 + j 0.20$

Q.2 A 40-MVA, 400-kV/20-kV, single-phase transformer has the following series impedances:  $0.9 + j1.8$  Ohm (referred to the low-voltage side) and  $40 + j80$  Ohm (referred to the high-voltage side). Using the transformer ratings as the selected bases, determine the per unit equivalent impedance of the transformer referred to the high-voltage side.            (3 points)

- a.  $400 + j 800$
- b.  $4.0 + j 8.0$
- c.  $1.0 + j 2.0$
- d.  $0.10 + j 0.20$

Q.3 A 40-MVA, 400-kV/20-kV, single-phase transformer has the following series impedances:  $0.9 + j1.8$  Ohm (referred to the low-voltage side) and  $40 + j80$  Ohm (referred to the high-voltage side). Using the transformer voltage ratings as the voltage base, and 400-MVA as the MVA base; determine the per unit equivalent impedance of the transformer referred to the low-voltage side.            (4 points)

- a.  $400 + j 800$
- b.  $4.0 + j 8.0$
- c.  $1.0 + j 2.0$
- d.  $0.10 + j 0.20$