

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

ELECTRICAL ENGINEERING DEPARTMENT

Dr. Ibrahim O. Habiballah

EE520 -171

Quiz 4

ser#:

I.D.:

Name:

Q.1 The phase “a” zero and positive sequence components of an unbalanced set of voltages are

$$\mathbf{V}^0 = 0.5 - j 0.866$$


$$\mathbf{V}^1 = 2.0$$

The phase “a” voltage is

$$\mathbf{V}_a = 3.0$$

Obtain the negative sequence component and the “b” and “c” phase voltages.

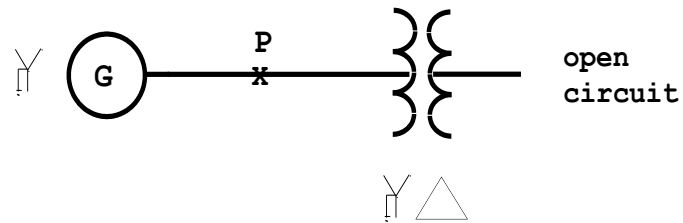Q.2 Consider the one-line diagram of a line connected between a generator and a transformer as shown below. For a line-to-ground fault at point P (in the middle of the line), find the faulted current. (Use the impedance method for fault analysis.) All numbers on the one-line diagram indicate the values of the reactances in per unit on a common system base.



$$X^1 = X^2 = j 0.1 \text{ pu}, X^0 = j 0.05 \text{ pu} \quad (\text{for the Generator})$$

$$X^1 = X^2 = j 0.4 \text{ pu}, X^0 = j 0.8 \text{ pu} \quad (\text{for the Line})$$

$$X^1 = X^2 = X^0 = j 0.05 \text{ pu} \quad (\text{for the Transformer})$$