

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

ELECTRICAL ENGINEERING DEPARTMENT

EE 306 – Term 171


HW # 1: Three-Phase Circuits

Due Date: October 2nd, 2017

Problem # 1:

Three impedances of $4 + j3 \Omega$ are Δ -connected and tied to a three-phase 208-V power line. Find I_ϕ , I_L , P , Q , S , and the power factor of this load.

Solution of Problem # 1:

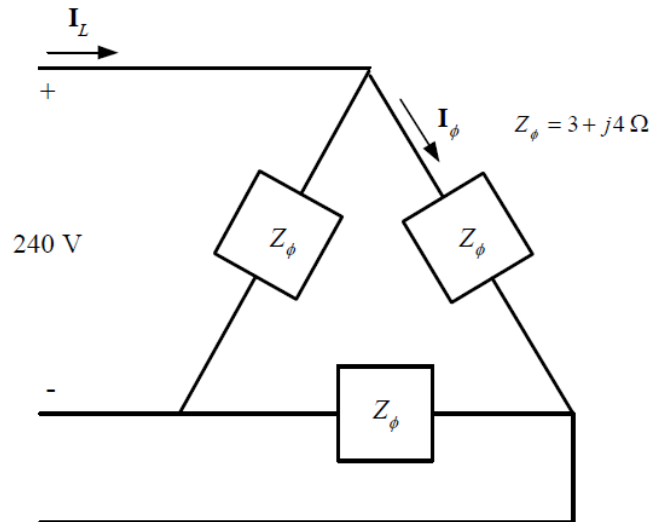

$V_L = V_\phi = 208 \text{ V}$, and $Z_\phi = 4 + j3 \Omega = 5 \angle 36.87^\circ \Omega$, so

$$I_\phi = \frac{V_\phi}{Z_\phi} = \frac{208 \text{ V}}{5 \Omega} = 41.6 \text{ A}$$

$$I_L = \sqrt{3} I_\phi = \sqrt{3} (41.6 \text{ A}) = 72.05 \text{ A}$$

$$P = 3 \frac{V_\phi^2}{Z} \cos \theta = 3 \frac{(208 \text{ V})^2}{5 \Omega} \cos 36.87^\circ = 20.77 \text{ kW}$$

$$Q = 3 \frac{V_\phi^2}{Z} \sin \theta = 3 \frac{(208 \text{ V})^2}{5 \Omega} \sin 36.87^\circ = 15.58 \text{ kvar}$$

$$S = \sqrt{P^2 + Q^2} = 25.96 \text{ kVA}$$

$$\text{PF} = \cos \theta = 0.8 \text{ lagging}$$

Problem # 2:

Prove that the line voltage of a Y-connected generator with an *acb* phase sequence lags the corresponding phase voltage by 30° . Draw a phasor diagram showing the phase and line voltages for this generator.

Solution of Problem # 2:

If the generator has an *acb* phase sequence, then the three phase voltages will be

$$\mathbf{V}_{an} = V_\phi \angle 0^\circ$$

$$\mathbf{V}_{bn} = V_\phi \angle -240^\circ$$

$$\mathbf{V}_{cn} = V_\phi \angle -120^\circ$$

The relationship between line voltage and phase voltage is derived below. By Kirchhoff's voltage law, the line-to-line voltage \mathbf{V}_{ab} is given by

$$\mathbf{V}_{ab} = \mathbf{V}_a - \mathbf{V}_b$$


$$\mathbf{V}_{ab} = V_\phi \angle 0^\circ - V_\phi \angle -240^\circ$$

$$\mathbf{V}_{ab} = V_\phi - \left(-\frac{1}{2}V_\phi + j\frac{\sqrt{3}}{2}V_\phi \right) = \frac{3}{2}V_\phi - j\frac{\sqrt{3}}{2}V_\phi$$

$$\mathbf{V}_{ab} = \sqrt{3}V_\phi \left(\frac{\sqrt{3}}{2} - j\frac{1}{2} \right)$$

$$\mathbf{V}_{ab} = \sqrt{3}V_\phi \angle -30^\circ$$

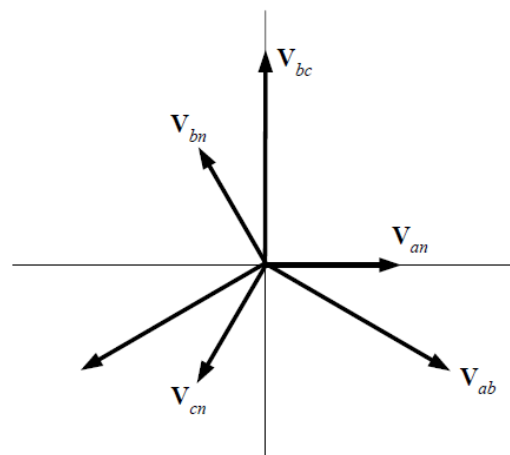Thus the line voltage *lags* the corresponding phase voltage by 30° . The phasor diagram for this connection is shown below.



Problem # 3:

A balanced 3-phase, 173-V, 60-Hz source supplies the two following loads:

- ❖ A Δ -connected load with a phase impedance of $(18+j24) \Omega$,
- ❖ A Y-connected load with a phase impedance of $10\angle 53.13^\circ \Omega$.

Find:

- a. The power factor of the entire load.
- b. The total line current supplied.
- c. The total real, reactive, and apparent powers.

Solution of Problem # 3:

Convert Δ to Y
$$Z_y = \frac{18 + j24}{3} = 6 + j8$$

Parallel combination of the 2 loads (per phase)

$$Z_T = \frac{(6 + j8)(10\angle 53.1^\circ)}{6 + j8 + 10\angle 53.1^\circ} = 5\angle 53.1^\circ$$

- a. Power factor = $\cos(53.1^\circ) = 0.6$ lag
- b. $I_L = I_{ph} = \frac{173/\sqrt{3}\angle 0^\circ}{5\angle 53.1^\circ} = 20\angle -53.1^\circ \text{ A}$
- c.


$$P_T = \sqrt{3} \times 173 \times 20 \times 0.6 = 3.596 \text{ kW}$$

$$Q_T = \sqrt{3} \times 173 \times 20 \times 0.8 = 4.794 \text{ kVAR}$$

$$|S_T| = \sqrt{3} \times 173 \times 20 = 5.993 \text{ kVA}$$

Problem # 4:


Consider the three-phase circuit below

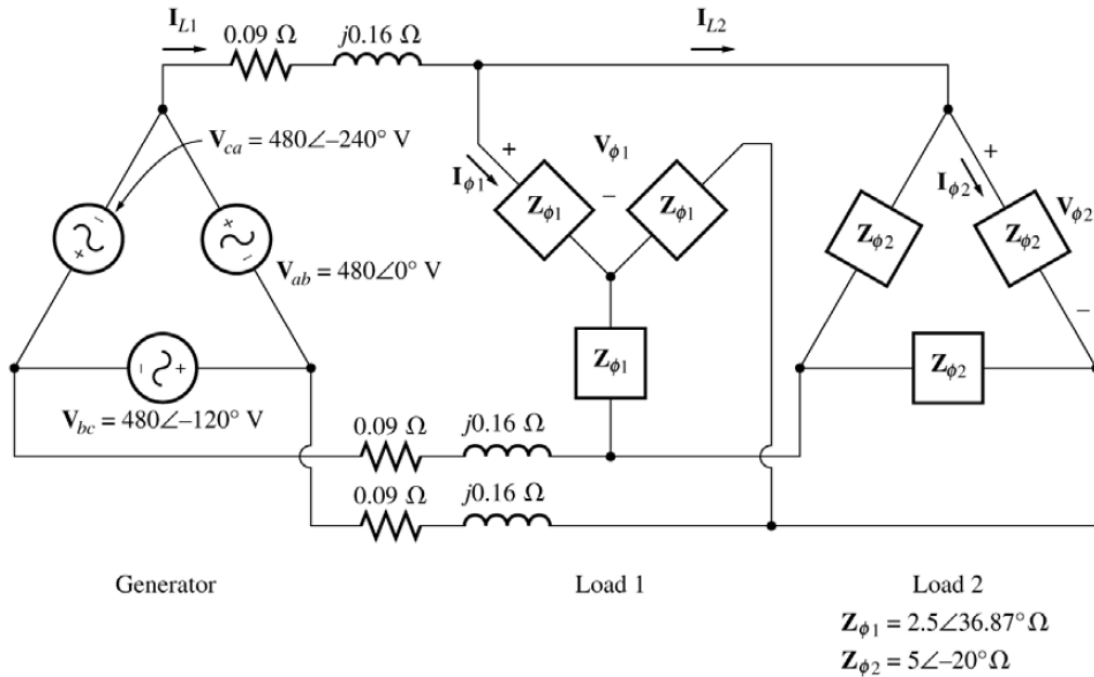

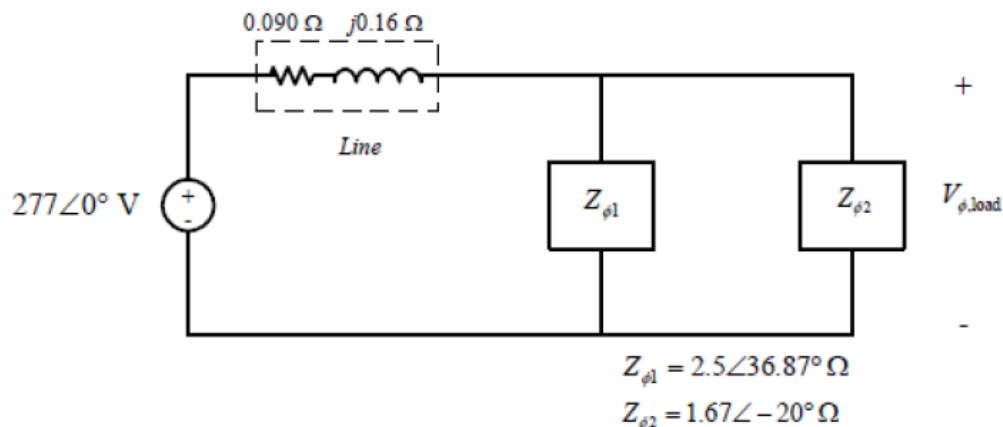- (a) What is the line voltage of the two loads?
- (b) What is the voltage drop on the transmission lines?
- (c) Find the real and reactive powers supplied to each load.
- (d) Find the real and reactive power losses in the transmission line.
- (e) Find the real power, reactive power, and power factor supplied by the generator.

Solution of Problem # 4:

To solve this problem, first convert the delta-connected load 2 to an equivalent wye (by dividing the impedance by 3), and get the per-phase equivalent circuit.



(a) The phase voltage of the equivalent Y-loads can be found by nodal analysis.

$$\frac{V_{\phi,\text{load}} - 277\angle 0^\circ \text{ V}}{0.09 + j0.16 \Omega} + \frac{V_{\phi,\text{load}}}{2.5\angle 36.87^\circ \Omega} + \frac{V_{\phi,\text{load}}}{1.67\angle -20^\circ \Omega} = 0$$

$$(5.443\angle -60.6^\circ) (V_{\phi,\text{load}} - 277\angle 0^\circ \text{ V}) + (0.4\angle -36.87^\circ) V_{\phi,\text{load}} + (0.6\angle 20^\circ) V_{\phi,\text{load}} = 0$$

$$(5.955\angle -53.34^\circ) V_{\phi,\text{load}} = 1508\angle -60.6^\circ$$

$$V_{\phi,\text{load}} = 253.2\angle -7.3^\circ \text{ V}$$

Therefore, the line voltage at the loads is $V_L \sqrt{3} V_\phi = 439 \text{ V}$.

(b) The voltage drop in the transmission lines is

$$\Delta V_{\text{line}} = V_{\phi,\text{gen}} - V_{\phi,\text{load}} = 277\angle 0^\circ \text{ V} - 253.2\angle -7.3^\circ = 41.3\angle 52^\circ \text{ V}$$

(c) The real and reactive power of each load is

$$P_1 = 3 \frac{V_\phi^2}{Z} \cos \theta = 3 \frac{(253.2 \text{ V})^2}{2.5 \Omega} \cos 36.87^\circ = 61.6 \text{ kW}$$

$$Q_1 = 3 \frac{V_\phi^2}{Z} \sin \theta = 3 \frac{(253.2 \text{ V})^2}{2.5 \Omega} \sin 36.87^\circ = 46.2 \text{ kvar}$$

$$P_2 = 3 \frac{V_\phi^2}{Z} \cos \theta = 3 \frac{(253.2 \text{ V})^2}{1.67 \Omega} \cos (-20^\circ) = 108.4 \text{ kW}$$

$$Q_2 = 3 \frac{V_\phi^2}{Z} \sin \theta = 3 \frac{(253.2 \text{ V})^2}{1.67 \Omega} \sin (-20^\circ) = -39.5 \text{ kvar}$$

(d) The line current is

$$I_{\text{line}} = \frac{\Delta V_{\text{line}}}{Z_{\text{line}}} = \frac{41.3\angle 52^\circ \text{ V}}{0.09 + j0.16 \Omega} = 225\angle -8.6^\circ \text{ A}$$

Therefore, the losses in the transmission line are

$$P_{\text{line}} = 3I_{\text{line}}^2 R_{\text{line}} = 3 (225 \text{ A})^2 (0.09 \Omega) = 13.7 \text{ kW}$$

$$Q_{\text{line}} = 3I_{\text{line}}^2 X_{\text{line}} = 3 (225 \text{ A})^2 (0.16 \Omega) = 24.3 \text{ kvar}$$

(e) The real and reactive power supplied by the generator is

$$P_{\text{gen}} = P_{\text{line}} + P_1 + P_2 = 13.7 \text{ kW} + 61.6 \text{ kW} + 108.4 \text{ kW} = 183.7 \text{ kW}$$

$$Q_{\text{gen}} = Q_{\text{line}} + Q_1 + Q_2 = 24.3 \text{ kvar} + 46.2 \text{ kvar} - 39.5 \text{ kvar} = 31 \text{ kvar}$$

The power factor of the generator is

$$\text{PF} = \cos \left[\tan^{-1} \frac{Q_{\text{gen}}}{P_{\text{gen}}} \right] = \cos \left[\tan^{-1} \frac{31 \text{ kvar}}{183.7 \text{ kW}} \right] = 0.986 \text{ lagging}$$

Problem # 5:

A single phase electrical load draws 10 MW at 0.6 power factor lagging.

- Find the real and reactive power absorbed by the load
- Draw the power triangle.
- Determine the kVAR of a capacitor to be connected across the load to raise the power factor to 0.95.

Solution of Problem # 5:

$$P = 10 \text{ MW}, \quad \text{PF} = 0.6 \text{ lagging}$$

$$\theta = \cos^{-1} 0.6 = 53.1^\circ$$

$$\text{(a)} \quad P = 10 \text{ MW}$$

$$Q = P \tan \theta = 10 \tan 53.1^\circ = 13.33 \text{ MVAR}$$

$$\text{(c)} \quad \theta_{\text{new}} = \cos^{-1} 0.95 = 18.2^\circ$$

$$Q_{\text{new}} = P \tan \theta_{\text{new}} = 10 \tan 18.2^\circ$$

$$= 3.29 \text{ MVAR}$$

$$= Q_{\text{old}} + Q_{\text{cap}}$$

$$Q_{\text{cap}} = 3.29 - 13.33 = -10 \text{ MVAR} = -10,000 \text{ kVAR}$$

