

Homework 3

EE-306 – Electromechanical Devices - Semester 171

Note: You must submit this cover page along with your solution

Student Name	ID	Sr. #	Section

Total Marks Obtained	/
----------------------	---

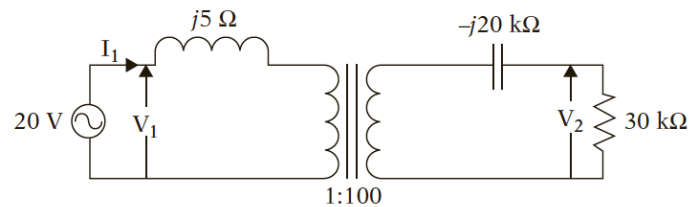


Figure 1: Figure of Problem 1.

Problem 1

An **ideal transformer** with the turns ratio 1:100 is connected in an electrical circuit as shown in Fig. 1. Calculate the following:

- (a) Actual load voltage V_2
- (b) Supply current I_1

Problem 2

The **peak** terminal voltage ($v_s(t)$) of secondary winding of a 100/200 V, 60 Hz transformer is:

$$v_s(t) = 282.8 \sin 377t \text{ V.}$$

If the **peak** secondary current of the transformer is:

$$i_s(t) = 7.07 \sin(37736.87 - 36^\circ) \text{ A.}$$

and if the impedances of this transformer **referred to the primary side** are:

$$R_{eq} = 0.20 \Omega \text{ and } X_{eq} = 0.75 \Omega$$

$$R_C = 300 \Omega \text{ and } X_M = 80 \Omega$$

Determine the primary current of this transformer using the approximate equivalent circuit referred to the primary side?

Problem 3

A single-phase transformer of 1000 VA, 230/115 V, 60 Hz has been tested to determine its equivalent circuit. The results of the tests are shown in Table 1.

Test	Voltage (V)	Current (A)	Power (W)
Open-Circuit (Primary Side)	230	0.45	30
Short-Circuit (Secondary Side)	19.1	8.7	42.3

Table 1: Table of Problem 3

- Find the equivalent circuit parameters referred to the **low-voltage side** of the transformer
- Draw the corresponding equivalent circuit and label it clearly.

Problem 4

A single-phase, 300 kVA, 11 kV/2.2 kV, 60 Hz transformer has the following equivalent circuit parameters referred to the high-voltage side:

$$R_{eq}(HV) = 2.784 \Omega \text{ and } X_{eq}(HV) = 8.45 \Omega$$

$$R_C(HV) = 57.6k \Omega \text{ and } X_M(HV) = 16.34k \Omega$$

- Determine
 - No-load current as a percentage of full load current
 - No-load power loss (i.e., core loss)
 - No-load power factor
 - Full-load copper loss
- If the load impedance on the low-voltage side is $Z_{load} = 16\angle 60^\circ \Omega$, determine the **voltage regulation (VR)** using the approximate equivalent circuit.

Problem 5

A single-phase, 25 kVA, 2300/230 V transformer has the following parameters:

$$Z_{eq,HV} = 4 + j5 \ \Omega$$

$$R_{C,LV} = 450 \ \Omega$$

$$X_{M,LV} = 300 \ \Omega$$

- The transformer is connected to a load whose power factor varies. Determine the **worst-case voltage regulation** for full-load output. Draw a phaser diagram to explain.
- Determine transformer's efficiency when it delivers full load at rated voltage and 0.85 power factor lagging.
- Determine the percentage loading of the transformer at which the **maximum efficiency** occurs, and calculate this **maximum efficiency** if the power factor is 0.85 and load voltage is 230 V.

Problem 6

A single-phase, 10 kVA, 2400/240 V, 60 Hz distribution transformer has the following characteristics:

Core loss at **full voltage** = 100W

Copper loss at **half load** = 60W

Determine the efficiency of the transformer when it delivers full load at 0.8 power factor lagging.

!End of Homework Problems!