

Homework 4

EE-306 – Electromechanical Devices - Semester 171

Submission Deadline: ST Classes (21 Nov 2017)

: MW Classes (22 Nov 2017)

Note: You must submit this cover page along with your solution

Student Name	ID	Sr. #	Section

Total Marks Obtained ||

/

Problem 1

A four pole DC machine has a flux per pole of 15 mWb. The armature has 330 conductors connected as a **wave winding** such that the rated conductor current remains the same. The DC machine runs at 1150 rpm and it delivers a rated armature current of 250 A to a load connected to its terminals.

- (a) Determine the machine constant, K_a
- (b) Determine the generated voltage, E_a
- (c) The conductor current, I_c
- (d) Electromagnetic torque, T_e
- (d) Power developed, P_{dev} , by the armature

Problem 2

Consider a self excited DC shunt generator (12 kW, 100 V, 1000 rpm) as shown in Fig. 1. It has armature resistance $R_a = 0.1 \Omega$, shunt field winding resistance $R_{fw} = 80 \Omega$, and $N_f = 1200$ turns per pole. The rated field current is 1 A. The magnetization characteristic of the machine at 1000 rpm are shown in Fig. 2. Determine the following assuming that the generator is operating at no load (for clarity, a curve with field resistor line is also shown in Fig. 3):

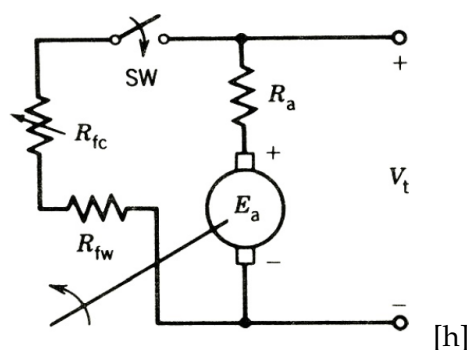


Figure 1: A self excited (shunt) generator (Problem 2).

- (a) The maximum value of the generated voltage
- (b) The value of the field circuit control resistance (R_{fc}) required to generate rated terminal voltage

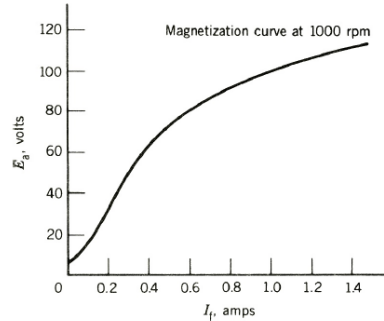


Figure 2: The magnetization curve of machine (Problem 2).

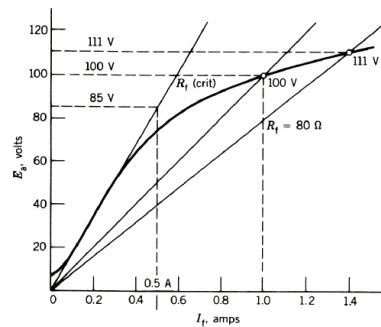


Figure 3: The magnetization curve of machine including field resistance lines (Problem 2).

Problem 3

A six poles short shunt compound DC generator running at 1200 rpm delivers 25 KW to a load resistance at a terminal voltage of 250 V. The resistance of the armature, shunt field resistance and the series field resistance are 0.12Ω , 125Ω and 0.05Ω respectively. The efficiency of the machine at the given load is 82%.

- (a) Draw the equivalent circuit
- (b) Estimate the input power and the corresponding applied input torque
- (c) Find the developed power and the corresponding developed torque

Problem 4

A 120 V DC shunt motor has armature and field resistances of 0.1Ω and 120Ω respectively, and a total brush voltage drop of 2V. The motor operates at rated load and draws a line current of 41 A at an angular speed of 200 rad/sec. Calculate

- (a) The field and armature current
- (b) The developed power and developed torque

Problem 5

Suppose a 600 V DC series motor with equal armature and field winding resistance of 0.5Ω is operating at 500 rpm and taking 75 A when connected to a 600 V supply. If the load torque is reduced to half, determine the following:

- The armature current
- The speed at which it will operate

Problem 6

A 240 V DC shunt motor has an armature resistance of 0.3Ω and a field resistance of 120Ω . At no-load, the motor runs at 1000 rpm and it draws a line current of 9 A.

- Draw the equivalent circuit with proper labeling
- Find the efficiency of motor assuming that the input to the motor is 12 kW at full load conditions.

Problem 7

A DC shunt motor (see Fig. 4) has the following parameters:

$$P_{rated} = 30 \text{ hp}, V_T = 240 \text{ V}, R_A = 0.19 \Omega, R_F = 75 \Omega, I_L(rated) = 110 \text{ A}$$

Magnetization curve of the given DC motor is shown in Fig. 5.

- If the resistor R_{adj} in Fig. 4 is adjusted to 175Ω , what is the rotational speed of the motor at no-load conditions?
- Assuming no armature reaction, what is the speed of the motor at full load? What is the speed regulation of the motor?

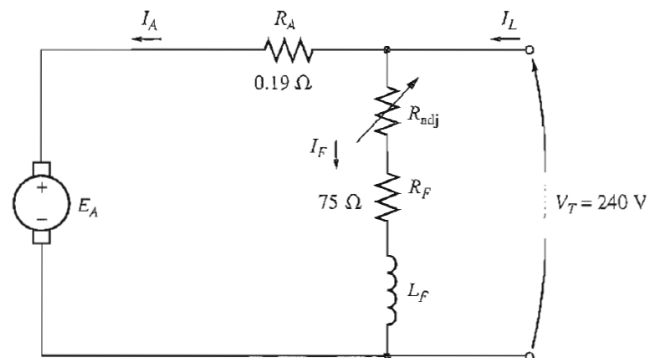


Figure 4: The equivalent circuit of the shunt motor (Problem 7).

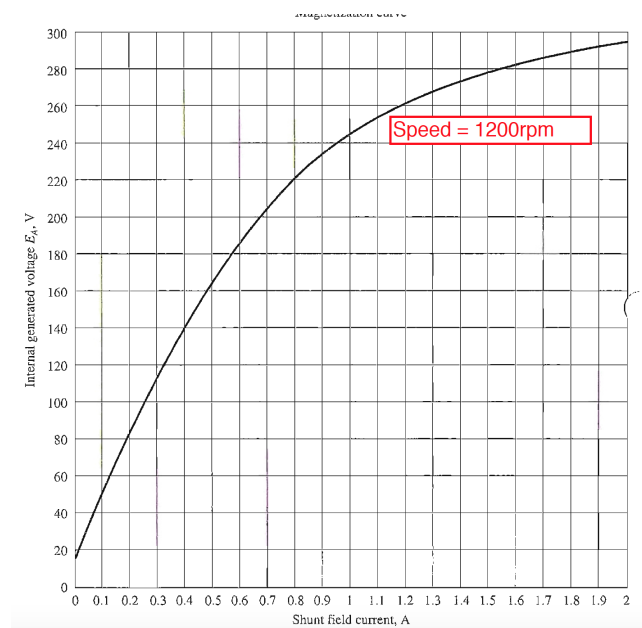


Figure 5: The magnetization curve for the DC motor (Problem 7).

!End of Homework Problems!