

EE 306 – Term 172
Solution HW # 4: DC Machines

Solution P1:

$$P = 6, \quad Z = 120 \times 8 = 960$$

$$E_g = 1.5 \text{ V / conductor}$$

$$I_{\text{conductor}} = 4 \text{ A}, \quad N = 1150 \text{ rpm}$$

$$a = 2 \text{ (Wave winding)}$$

$$\text{No. of conductors per path} = \frac{960}{2} = 480$$

$$\begin{aligned} \text{Induced emf per path} &= 480 \times 1.5 \\ &= 720 \text{ V} \end{aligned}$$

(a) No-load terminal voltage = 720 V

(b) The output current at full load = 8 A

$$(c) \quad \phi = \frac{E_a \times 60 \times a}{P Z N} = \frac{720 \times 60 \times 2}{6 \times 960 \times 1150}$$

$$\phi = 13.04 \text{ mWb}$$

(d) $P_d = E_a I_a = 720 \times 8$

$$\boxed{P_d = 5.76 \text{ kW}}$$

Solution P2:

4.8 (a) $I_a |_{\text{rated}} = \frac{6000}{120} = 50 \text{ A}$

At $I_f = 1.0 \text{ A}$ and $1200 \text{ rpm} \rightarrow E_a = 120 \text{ V}$.

$V_t = 120 - 50 \times 0.2 = 110 \text{ V}$.

$P_o = 110 \times 50 = 5500 \text{ W}$, $P_{in} = 120 \times 50 + 400 = 6400 \text{ W}$

$\text{Eff.} = \frac{5500}{6400} \times 100\% = 85.94\%$

(b) At $I_f = 1.0 \text{ A}$ and $1500 \text{ rpm} \rightarrow E_a = 120 \times \frac{1500}{1200} = 150 \text{ V}$

$V_t = 150 - 50 \times 0.2 = 140 \text{ V}$.

$P_o = 140 \times 50 = 7000 \text{ W}$

$P_{in} = 150 \times 50 + 400 \times \frac{1500}{1200} = 8000 \text{ W}$

$\text{Eff.} = \frac{7000}{8000} \times 100\% = 87.5\%$


Solution P3:

4.13 (a) $E_a |_{\text{max}}$ will occur at $R_{fc} = 0$

Draw field resistance line for

$R_f = R_{fw} = 150 \Omega$

$E_a(\text{max}) = 222 \text{ V}$

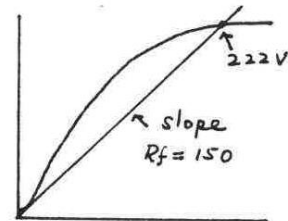


(b) $I_a(\text{rated}) = \frac{20,000}{200} = 100 \text{ A}$

$V_t(\text{rated}) = 200 \text{ V}$

$R_f = \frac{200}{1.25} = 160 \Omega$

$R_{fc} = 160 - 150 = 10 \Omega$

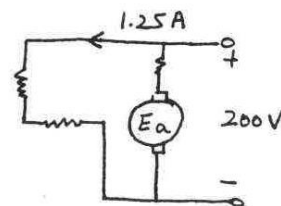

(c) $E_a = V_t + I_a R_a = 200 + 100 \times 0.1 = 210 \text{ V}$

$P_{dc} = E_a I_a = 210 \times 100 = 21000 \text{ W}$

$\omega_m = \frac{1800}{60} \times 2\pi = 188.5 \text{ rad./sec.}$

$T = \frac{E_a I_a}{\omega_m} = \frac{21000}{188.5} = 111.41 \text{ N.m}$

Solution P4:

A six poles **short shunt** compound DC generator running at 1200 rpm delivers 25 kW to a load resistance at a terminal voltage of 250 V. The resistance of the armature, shunt field resistance and the series field resistance are 0.12 Ω , 125 Ω and 0.05 Ω respectively. The efficiency of the machine at the given load is 82%.

- Draw the equivalent circuit
- Estimate the input power and the corresponding applied input torque
- Find the developed power and the corresponding developed torque

$p = 6$, Short Shunt Compound Generator
 $\omega = 1200 \text{ rpm}$, $R_f = 125 \Omega$, $V_t = 250 \text{ V}$, $R_a = 0.12 \Omega$,
 $R_s = 0.05 \Omega$, $R_{se} = 0.05 \Omega$, $\eta = 82\%$, $P_{out} = 25 \text{ kW}$

a)

$P_{out} = 25 \text{ kW}$
 $\omega = \frac{2\pi \times 1200}{60} = 125.66 \text{ rad/s}$

b)

$$\eta = \frac{P_{out}}{P_{in}} \times 100\% \Rightarrow P_{in} = \frac{P_{out}}{\eta} = \frac{25}{0.82} = 30.488 \text{ kW}$$

$$P_{in} = T_{in} \times \omega \Rightarrow T_{in} = \frac{P_{in}}{\omega} = \frac{30.488 \times 10^3}{125.66} = 242.65 \text{ N.m}$$

c)

$$P_{dev} = E_a I_a$$

$$E_a = V_f + I_a R_a$$

$$I_f = \frac{V_f}{R_f} = \frac{255}{125} = 2.04 \text{ A}$$

$$I_a = I_f + I_L = 2.04 + 100 = 102.04 \text{ A}$$

$$E_a = 255 + (102.04)(0.12) = 267.2448 \text{ V}$$

$$P_{dev} = (267.2448)(102.04) = 27.26965 \text{ kW}$$

$$T_{dev} = \frac{P_{dev}}{\omega} = \frac{27.26965}{125.66} = 217.011 \text{ N.m}$$

Solution P5:

- 4.26 (i) From no-load condition, rotational loss is
 $P_{\text{rot}} = E_a I_a = (240 - 20 \times 0.5) \times 20 = (240 - 10) \times 20 = 4780 \text{ W}$
This can be assumed constant if the speed variation is small
- (ii) $P_f = 240 \times 120 = 2880 \text{ W}$
- (iii) $P_a = E_a I_a = (240 - 300 \times 0.05) \times 300 = 67500 \text{ W}$
 $P_{\text{out}} = 67500 - 4780 = 62720 \text{ W}$
 $P_{\text{arm}} = 240 \times 300 = 72000 \text{ W}$
 $P_{\text{in}} = P_{\text{arm}} + P_f = 72000 + 2880 = 74880 \text{ W}$
 $\text{Eff} = \frac{62720}{74880} \times 100\% = 83.8\%$

Solution P6:

4.27 $E_a|_{1100} = 500 - 100 \times 0.25 = 475 \text{ V}$
 $E_a|_{900} = 475 \times \frac{900}{1100} = 388.6 \text{ V}$
 $I_a|_{1100} = 100 \text{ A}$
 $I_a|_{900} = 100 \times \frac{900}{1100} = 81.8 \text{ A}$
 $IR = V - E_a = 500 - 388.6 = 111.4 \text{ V}$
 $R = \frac{111.4}{81.8} = 1.36 \Omega$
 $R_{\text{series}} = 1.36 - 0.25 = 1.11 \Omega$

~~~~~