

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

ELECTRICAL ENGINEERING DEPARTMENT


Dr. Ibrahim O. Habiballah

EE-306

Key Solution

Quiz 4 Sec.: 4 I.D.: Ser#: Name:

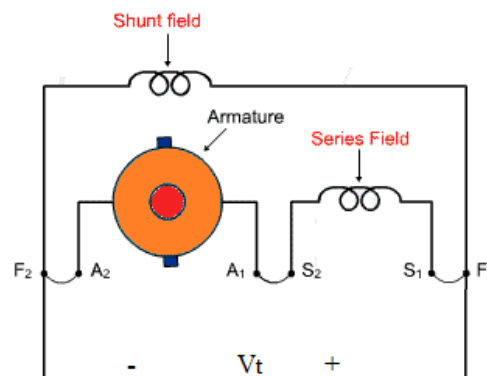Q.1 The figure below is for a short-shunt self-excited compound DC machine. (3-points)



a. True.

b. **False.**

Q.2 In self-excited DC generators, the sequence of actions for building up the terminal voltage is (4-points)

$$R_F \downarrow \rightarrow I_F \uparrow = \frac{V_T}{R_F \downarrow} \rightarrow \phi \uparrow = \frac{N}{\mathfrak{R}} I_F \uparrow \rightarrow$$

$$E_A \uparrow = K' \phi \uparrow n_m \rightarrow V_T \uparrow = E_A \uparrow - R_A I_A$$

a. True.

b. **False.**

Q.3 The speed regulation for any type of DC motors is always positive value, because the speed at no-load is larger than the speed at full-load. (3-points)

a. True.

b. **False.**