

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
ELECTRICAL ENGINEERING DEPARTMENT

EE 306 – Term 182

HW # 6: Induction Motors

Due Date: (UT-Classes, April 14th, 2019; MW-Classes, April 15th, 2019)

Key Solutions

Problem # 1:

A three-phase, four-pole, 30-hp, 220-V, 60-Hz, Y-connected induction motor draws a current of 77-A from the supply line at a power factor of 0.88. At this operating condition, the motor losses are known to be the following:

Stator copper losses = 1033 W ; Rotor copper losses = 1299 W

Core loss = 485 W ; Mechanical losses (friction & windage) = 540 W

Determine:

- a) the power transferred across the air gap
- b) the internally developed torque in Newton-meters
- c) the slip expressed in percentage
- d) the mechanical power developed in watts
- e) the horsepower output
- f) the motor speed in rpm
- g) the torque at the output shaft
- h) the efficiency of operation

$$\begin{aligned} V_{\phi} &= \frac{220}{\sqrt{3}} = 127 \text{ V} \\ P_{in} &= 3 V_{\phi} I_{\phi} \cos \phi = 3 \times 127 \times 77 \times 0.88 \\ P_{in} &= 25.8 \text{ kW} \\ P_{cu1} &= 1033 \text{ W} \\ P_{cu2} &= 1299 \text{ W} \\ P_{core} &= 485 \text{ W} \\ P_{fw} &= 540 \text{ W} \\ P_g &= P_{in} - P_{cu1} - P_{core} = 25.8 \times 10^3 - 1033 - 485 \\ P_g &= 24.3 \text{ kW} \end{aligned}$$

$$\textcircled{b} \quad T_d = \frac{P_g}{\omega_s}, \quad \omega_s = \frac{2\pi n_s}{60}, \quad n_s = \frac{120 \text{ kV}}{P} = \frac{120 \times 60}{4} = 1800 \text{ rpm}$$

$$\omega_s = \frac{2\pi \times 1800}{60} = 188.5 \text{ rad/sec}$$

$$T_d = \frac{24.3 \times 10^3}{188.5}$$

$$\boxed{T_d = 128.9 \text{ N-m}}$$

$$\textcircled{c} \quad S = \frac{P_{\text{core}}}{P_g} = \frac{1299}{24.3 \times 10^3} \Rightarrow S = 0.0534$$

$$\boxed{S = 5.34\%}$$

$$\textcircled{d} \quad P_d = (1-S) \times P_g = (1-0.0534) \times 24.3 \times 10^3$$

$$\boxed{P_d = 23.0 \text{ kW}}$$

$$\textcircled{e} \quad P_o = P_d - P_{\text{fric}} = 23 \times 10^3 - 540 = 22.46 \text{ kW}$$

$$P_o = \frac{22.46 \times 10^3}{746} \Rightarrow \boxed{P_o = 30 \text{ hp}}$$

$$\textcircled{f} \quad n_m = (1-S) \times n_s = (1-0.0534) \times 1800 \Rightarrow \boxed{n_s = 1704 \text{ rpm}}$$

$$\textcircled{g} \quad T_o = \frac{P_o}{\omega} = \frac{22.46 \times 10^3}{1704} \Rightarrow \boxed{T_o = 132 \text{ N-m}} \quad \textcircled{h} \quad \eta = \frac{P_o}{P_{\text{in}}} = \frac{22.46}{25.8}$$


Problem # 2:

A 3-phase, Y-connected, 220-V, 10-HP, 60-Hz, 6-pole induction motor has the following parameters in ohms.

$$R_1 = 0.294 \Omega, R_2 = 0.144 \Omega, X_1 = 0.503 \Omega, X_2 = 0.209 \Omega, X_m = 13.25 \Omega$$

The total friction, windage and core losses may be assumed to be constant at 403 W, independent of load. For a slip of 3%, determine:

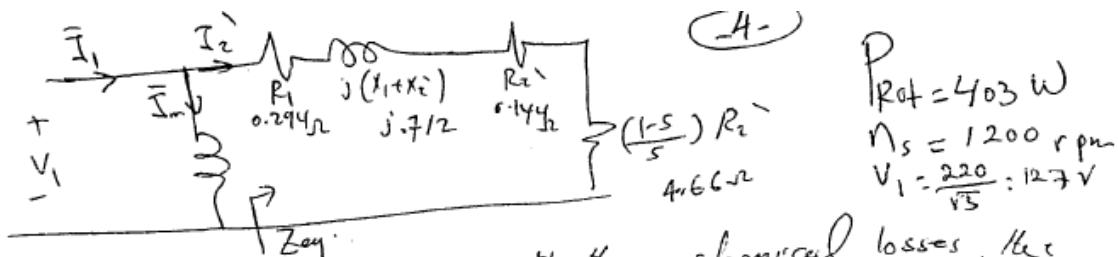- the rotor current, developed torque and developed power.
- the maximum developed torque and the corresponding speed.
- the starting torque and starting current.
- How much resistance must be inserted in the rotor circuit to bring the motor speed at maximum torque down to 900 rpm?
- the new starting torque.



Since the core loss is lumped with the mechanical losses, the core resistance will be removed from the equivalent circuit.

$$s = 0.03 \Rightarrow \frac{1-s}{s} \times R_2 = \frac{1-0.03}{0.03} \times 0.144 = 4.66 \Omega$$

$$Z_{eq} = (R_1 + \frac{R_2}{s}) + j(X_1 + X_2) = (0.294 + \frac{0.144}{0.03}) + j(0.503 + 0.209)$$

$$Z_{eq} = 5.14 \angle 7.95^\circ \Omega$$

$$V_1 = \frac{220}{\sqrt{3}} = 127 \text{ V}$$

$$\textcircled{a} \quad \bar{I}_2 = \frac{V_1}{Z_{eq}} = \frac{127 \angle 0^\circ}{5.14 \angle 7.95^\circ} \Rightarrow$$

$$\bar{I}_2 = 24.7 \angle -7.95^\circ \text{ A}$$

$$P_d = 3 I_2^2 \left(\frac{1-s}{s} \right) R_2' = 3 (24.7)^2 (4.66) \Rightarrow P_d = 8.52 \text{ kW}$$

$$n = (1-s) n_s = (1-0.03) \times 1200 \Rightarrow n = 1164 \text{ rpm}$$

$$T_d = \frac{P_d}{\omega_m} = \frac{P_d}{\frac{2\pi n}{60}} = \frac{8.52 \times 10^3}{\frac{2\pi (1164)}{60}} \Rightarrow T_d = 69.9 \text{ N}\cdot\text{m}$$

$$\textcircled{b} T_{\max} = \frac{3 V_1^2}{2\omega_s} \cdot \frac{1}{[R_1 + \sqrt{R_1^2 + (X_1 + X_2')^2}]} = \frac{3 \times (127)^2}{2 \left(\frac{2\pi \times 1200}{60} \right)} \times \frac{1}{[0.294 + \sqrt{0.294^2 + (0.712)^2}]}$$

$$T_{\max} = 181 \text{ N}\cdot\text{m}$$

$$S_{\max} = \frac{R_2'}{\sqrt{R_1^2 + (X_1 + X_2')^2}} = \frac{0.144}{\sqrt{(0.294)^2 + (0.712)^2}} = 0.187$$

$$\textcircled{c} |I_{2 \text{ start}}| = \frac{V_1}{\sqrt{(R_1 + R_2')^2 + (X_1 + X_2')^2}} = \frac{127}{\sqrt{(0.438)^2 + (0.712)^2}} \quad -5^\circ$$

$$I_{2 \text{ start}} = 151.9 \angle -58.5^\circ \text{ A}$$

$$\alpha = \tan^{-1} \frac{(X_1 + X_2')}{R_1 + R_2'} = 58.5^\circ$$

$$I_m = \frac{\bar{V}_1}{jX_m} = \frac{127 \angle 0^\circ}{13.25 \angle 90^\circ} = -j9.6 \text{ A}$$

$$I_{1 \text{ start}} = I_m + I_2 = 9.6 \angle -90^\circ + 151.9 \angle -58.5^\circ$$

$$I_1 = 159.6 \angle -60.3^\circ \text{ A}$$

$$T_{d \text{ starting}} = \frac{3 I_{2 \text{ start}}^2 R_2'}{\omega_s} = \frac{3 V_1^2}{\omega_s} \cdot \frac{R_2'}{(R_1 + R_2')^2 + (X_1 + X_2')^2}$$

$$T_{d \text{ starting}} = \frac{3 (127)^2 \times (0.144)}{(0.438)^2 + (0.712)^2} \times \frac{1}{\frac{2\pi \times 1200}{60}}$$

$$T_{\text{starting}} = 79 \text{ N}\cdot\text{m}$$

$$\textcircled{d} \quad \frac{n}{T_{\text{max}}} = 900 \text{ rpm} \Rightarrow s_{\text{max}} = \frac{n_s - n}{n_s} = \frac{1200 - 900}{1200} = 0.25$$

$$\textcircled{2} \text{ max. Torque} \Rightarrow s_{\text{max}} = \frac{R_{z\text{new}}}{\sqrt{R_1^2 + (X_1 + X_2)^2}} = 0.25$$

$$R_{z\text{new}} = 0.25 \times \sqrt{(0.294)^2 + (0.712)^2} = 0.193 \Omega$$

$$R_{z\text{added}} = R_{z\text{new}} - R_1 = 0.193 - 0.144$$

$$R_{z\text{added}} = 0.0486 \Omega$$

$\approx 0.05 \Omega$ $R_{z\text{new}}$

$$\Rightarrow T_{\text{starting}} = 100 \text{ N}\cdot\text{m}$$

Problem 3

A 3-phase, 460 V, 60 Hz, 20 kW induction machine draws 25 A at a power factor of 0.9 lagging when connected to a 3-phase, 460 V, 60 Hz power supply. The core loss is 900 W, stator copper loss is 1100 W, rotor copper loss is 550 W, and friction and winding loss is 300 W. Calculate

- (a) The air gap power, P_{ag} .
- (b) The mechanical power developed, P_{mech} .
- (c) The output horse power.
- (d) The efficiency.

Solution:

$$(a) \quad P_{ag} = P_{in} - P_{core} - P_{cu, stator} = \sqrt{3} \times 460 \times 25 \times 0.9 - 900 - 1100 \\ = 17926.2 - 900 - 1100 = 15926.2 \text{ W}$$

$$(b) \quad P_{mech} = P_{ag} - P_{cu, rotor} = 15926.2 - 550 = 15376.2 \text{ W}$$

$$(c) \quad P_{out} = 15376.2 - 300 = 15076.2 \text{ W}$$

$$HP = \frac{15076.2}{746} = 20.2$$

$$(d) \quad \text{Eff} = \frac{15076.2}{17926.2} \times 100\% = 84.1\%$$