

# KING FAHD UNIVERSITY OF PETROLEUM & MINERALS

## ELECTRICAL ENGINEERING DEPARTMENT

EE 306 – Term 191

HW # 1: Three-Phase Circuits

Due Date: (Sep. 16<sup>th</sup>, 2019)

### Problem # 1:


Determine the phase sequence of the set of voltages

$$v_{an} = 200 \cos(\omega t + 10^\circ)$$

$$v_{bn} = 200 \cos(\omega t - 110^\circ) , \quad v_{cn} = 200 \cos(\omega t - 230^\circ)$$
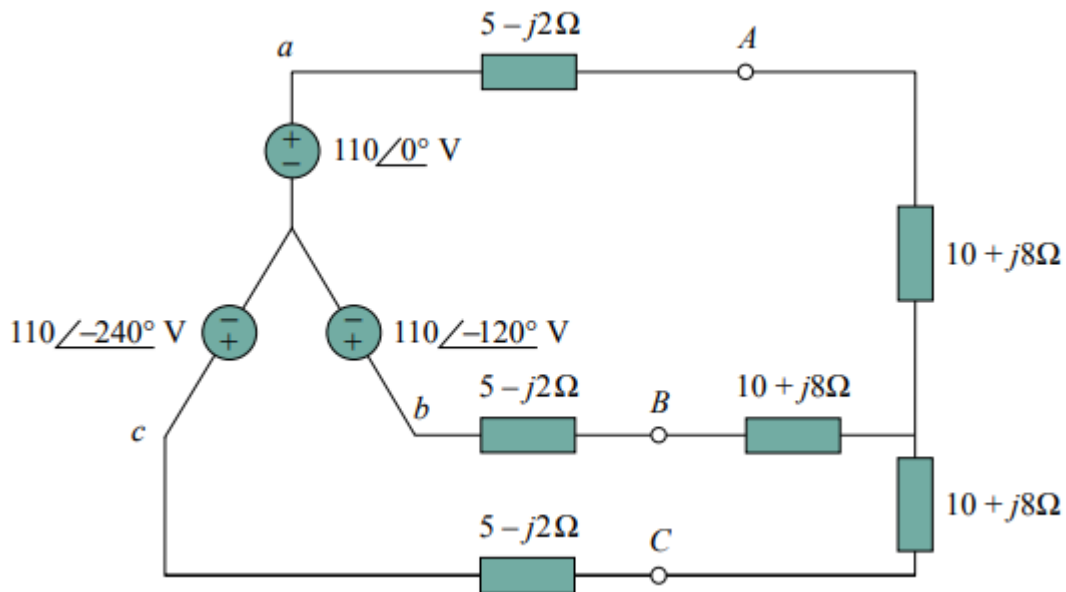
### Problem # 2:

Calculate the line currents in the three-wire Y-Y system shown below.



**Problem # 3:**

A balanced  $abc$ -sequence Y-connected source with  $V_{an} = 100 \angle 10^\circ \text{ V}$  is connected to a  $\Delta$ -connected balanced load  $(8 + j4) \Omega$  per phase.

Calculate the phase and line currents at the load side.

**Problem # 4:**

Three impedances of  $4 + j3 \Omega$  are  $\Delta$ -connected and tied to a three-phase 208-V power line.

Find  $I_\phi$ ,  $I_L$ ,  $P$ ,  $Q$ ,  $S$ , and the power factor of this load.

**Problem # 5:**

Figure below shows a one-line diagram of a simple power system containing a single 480 V generator and three loads. Assume that the transmission lines in this power system are lossless, and answer the following questions.

- Assume that Load 1 is Y-connected. What are the phase voltage and currents in that load?
- Assume that Load 2 is  $\Delta$ -connected. What are the phase voltage and currents in that load?
- What real, reactive, and apparent power does the generator supply when the switch is open?
- What is the total line current  $I_L$  when the switch is open?
- What real, reactive, and apparent power does the generator supply when the switch is closed?
- What is the total line current  $I_L$  when the switch is closed?

