

Due Date Oct. 16th 2019

Homework 3 Solution

Question 1)

A single-phase, 10 kVA, 2200/220V 60 Hz transformer has:
 $R_1 = 1 \Omega$, $L_1 = 7.96 \text{ mH}$, $R_2 = 0.1 \Omega$ and $L_2 = 0.796 \text{ mH}$.

A load of 6 kW, 0.8 pf lagging is connected to its secondary side. Using transformer approximated equivalent circuit without excitation branch shown in Figure 1, find:

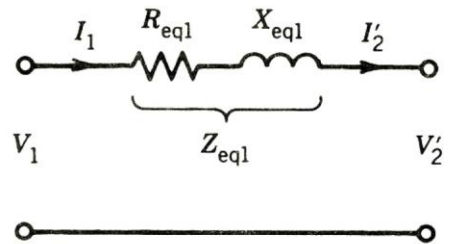


Figure 1: Approximated equivalent circuit

- 1- Transformer input current.
- 2- Input power factor
- 3- Draw the phasor diagram

Solution:

1) transformer input current

$$Z_1 = R_1 + j2\pi f L_1 = 1 + j2\pi * 60 * 7.96 * 10^{-3} = 1 + j3 \Omega$$

$$Z_2 = R_2 + j2\pi f L_2 = 0.1 + j2\pi * 60 * 0.796 * 10^{-3} = 0.1 + j0.3 \Omega$$

$$\text{So, } Z_2' = a^2 Z_2 = 10 + j30 \Omega$$

Connecting the 6 kW load and referring to primary side, then

$$I_2' = \frac{P}{V_2' \text{ pf}} = \frac{6,000}{2200 * 0.8} = 3.4 \text{ A}$$

As the magnetization branch is neglected here, the transformer input current equals the $I_2' = 3.4 \text{ A}$


2) input power factor:

The power factor is calculated by cosine the angle between the input voltage and current vectors. Therefore,

$$V_1 = V_2' + I_2' Z_{eq-1} = 2200 \angle 0 + 3.4 \angle -\cos^{-1}(0.8) * (11 + j33) = 2298 \angle 1.6^\circ \text{ V}$$

Then, the input power factor equals $\cos(1.6 - (-\cos^{-1} 0.8)) = 0.78 \text{ Lagging}$.

3) Phasor diagram:

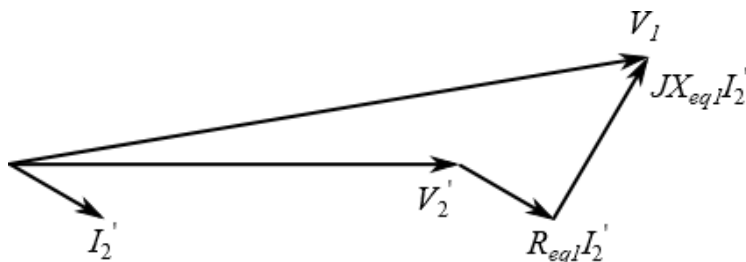

King Fahd University of Petroleum and Minerals

EE-306 – Electromechanical Devices - Semester 191

Question 2)

A single-phase, 20 kVA, 2200/220V 60 Hz transformer has equivalent impedance $5 + j25 \Omega$ referred to its primary side. Find the voltage regulation if the transformer is loaded by:

- 1- Full load, 0.8 lagging pf.
- 2- 70% of its full load with 0.8 leading pf.

Solution:

$$VR \% = \frac{|V_1| - |V_2'|}{|V_2'|} * 100.$$

1) Full load means that the current and the apparent power are rated values. Therefore,

$$I_2' = \frac{S}{V_2'} = \frac{20,000}{2200} = 9 \text{ A}$$

$$V_1 = V_2' + I_2' Z_{eq-1} = 2200 \angle 0 + 9 \angle -\cos^{-1}(0.8) * (5 + j25) = 2377 \angle 3.7^\circ \text{ V}$$

$$VR \% = \frac{2377 - 2200}{2200} * 100 = 8.08\%$$

2) at 70% of rated, the current is $0.7 * 9 = 6.36 \text{ A}$, power factor is 0.8 leading

$$V_1 = V_2' + I_2' Z_{eq-1} = 2200 \angle 0 + 6.36 \angle \cos^{-1}(0.8) * (5 + j25) = 2135 \angle 3.93^\circ \text{ V}$$

$$VR \% = \frac{2135 - 2200}{2200} * 100 = -2.95 \%$$

Question 3)

A 10 kVA, 2300/230 V, single-phase transformer has been tested while keeping the meters are connected at the HV side. The tests data are as follows:

- OCT at rated voltage: 0.45 A and 70 W (Measurements at HV side)
 - SCT at rated current: 120 V, 240 W (Measurements at HV side)
- 1- Determine the approximate equivalent with excitation branch circuit referred to HV side.

King Fahd University of Petroleum and Minerals

EE-306 – Electromechanical Devices - Semester 191

2- Determine the transformer efficiency at full load, 0.8 pf lagging

Solution:

Since the meters are connected in the HV side, the parameters can be calculated referred to HV side without transferring.

1) Approximate equivalent with excitation branch referred to HV side.

→ From the open circuit test,

$$R_c = \frac{V_{oc}^2}{P_{oc}} = \frac{2300^2}{70} = 75,571.4 \Omega$$

$$I_c = \frac{V_{oc}}{R_c} = \frac{2300}{75,571.4} = 0.03 \text{ A} \quad \text{and} \quad I_m = \sqrt{(I_{oc}^2 - I_c^2)} = 0.448 \text{ A}$$



$$\text{Then, } X_m = \frac{V_{oc}}{I_m} = \frac{2300}{0.448} = 5,123 \Omega$$

→ For the short circuit test, the current is rated which is $I_2' = \frac{S}{V_2'} = \frac{10,000}{2300} = 4.3478 \text{ A}$

$$R_{eq-1} = \frac{P_{sc}}{I_{sc}^2} = \frac{240}{4.3478^2} = 12.696 \Omega$$

$$Z_{eq-1} = \frac{V_{sc}}{I_{sc}} = \frac{120}{4.3478} = 27.6 \Omega$$
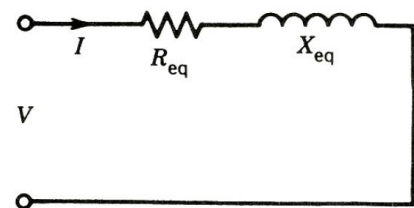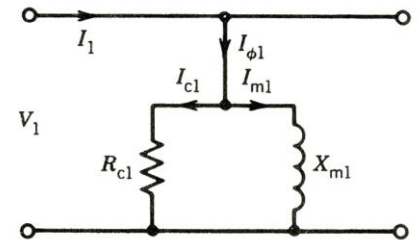
$$X_{eq-1} = \sqrt{(Z_{eq-1}^2 - R_{eq-1}^2)} = 24.5 \Omega$$



2) Transformer efficiency at full load, 0.8 pf lagging ($X = 1$ for full load)

$$\eta = \frac{X \cdot S_{rat} \cdot pf}{P_{core} + X^2 P_{cu-rated} + X \cdot S_{rat} \cdot pf}$$

$$\eta_{\%} = \frac{10,000 * 0.8}{70 + 240 + 10,000 * 0.8} * 100 = 96.26 \%$$

King Fahd University of Petroleum and Minerals

EE-306 – Electromechanical Devices - Semester 191

Question 4)

For the transformer of Question 3,

- 1- Determine the percentage loading of the transformer at which the efficiency is a maximum at a load pf of 0.8
- 2- Calculate the maximum efficiency

Solution:

For maximum efficiency at a definite power factor, the copper loss equals core losses. Hence,

1) The loading factor X is

$$X = \sqrt{\left(\frac{P_c}{P_{cu-rate}}\right)} = \sqrt{\left(\frac{70}{240}\right)} = 0.54$$

2)

$$\eta_{\%max} = \frac{X \cdot S_{rat} \cdot pf}{2 \cdot P_{core} + X \cdot S_{rat} \cdot pf} = \frac{0.54 \cdot 10,000 \cdot 0.8}{70 \cdot 2 + 0.54 \cdot 10,000 \cdot 0.8} * 100 = 96.86 \%$$

Question 5)

The efficiency of a 400 kVA, 60 Hz single-phase transformer is 98.77% when delivering full load current of 0.8 pf, and 99.13 % while delivering half rated current at unity power factor. Find:

- 1- core losses
- 2- full-load copper losses

Solution:

$$\eta = \frac{X \cdot S_{rat} \cdot pf}{P_{core} + X^2 P_{cu-rated} + X \cdot S_{rat} \cdot pf}$$

$$\text{Case-1: } 0.9877 = \frac{1 \cdot 400,000 \cdot 0.8}{P_{core} + 1^2 \cdot P_{cu-rated} + 1 \cdot 400,000 \cdot 0.8} \rightarrow P_{core} + P_{cu-rated} = 3936 \text{ W (Eq-1)}$$

$$\text{Case-2: } 0.9913 = \frac{0.5 \cdot 400,000}{P_{core} + 0.5^2 \cdot P_{cu-rated} + 0.5 \cdot 400,000} \rightarrow P_{core} + \frac{1}{4} P_{cu-rated} = 1740 \text{ W (Eq-2)}$$

Solving Eq-1 and Eq-2,

$$P_{core} = 1008 \text{ W and } P_{cu-rated} = 2928 \text{ W}$$

King Fahd University of Petroleum and Minerals

EE-306 – Electromechanical Devices - Semester 191

Best Regards