

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
ELECTRICAL ENGINEERING DEPARTMENT
Dr. Ibrahim O. Habiballah
EE-306
Key Solution

Quiz 4 Sec.: 8 I.D.: Ser#: Name:

Circle the correct answer.


1) The back EMF (i.e., E_A) of a series DC motor is (3 Marks)
 (A = armature; L = load; S = series-field; T = terminal)

- a- $E_A = V_T - I_L R_L$
- b- $E_A = V_T - I_A R_A$
- c- $E_A = V_T - I_S R_S$
- d- **None of above**

2) The terminal voltage of a shunt DC generator can be controlled as follows: (3 Marks)

- a- $n \uparrow \Rightarrow E_A \downarrow \Rightarrow V_T \uparrow$
- b- $R_F \downarrow \Rightarrow I_F \uparrow \Rightarrow E_A \downarrow \Rightarrow V_T \uparrow$
- c- $R_F \uparrow \Rightarrow I_F \downarrow \Rightarrow E_A \downarrow \Rightarrow V_T \downarrow$
- d- "a" and "b" above

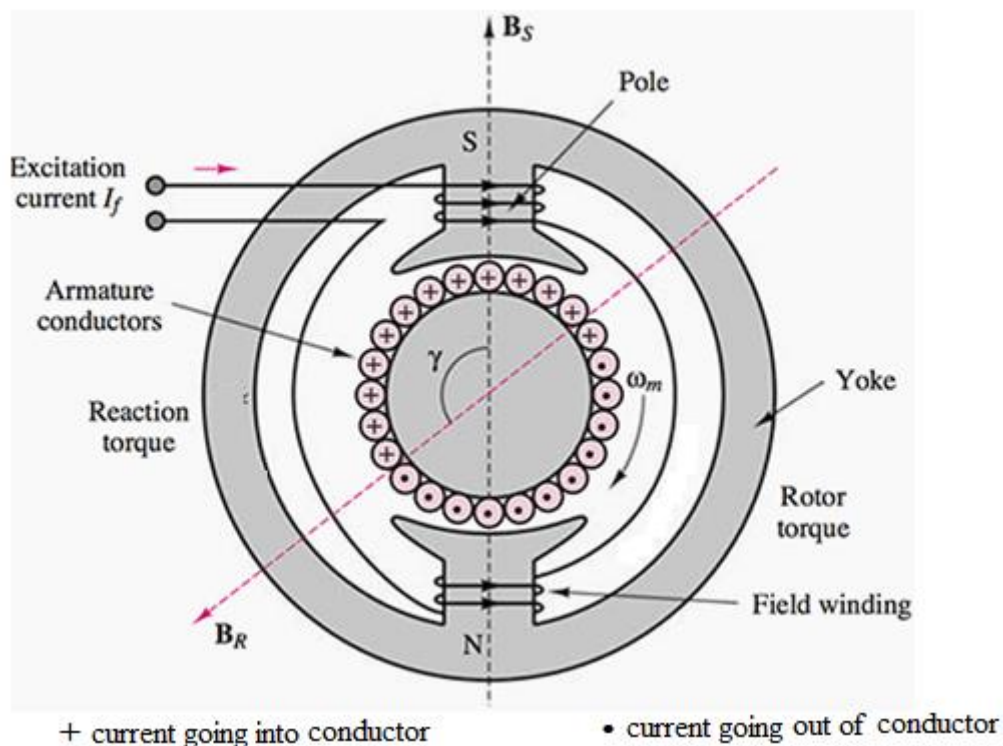3) The machine shown below is operating as (4 Marks)



- a. **a motor.**
- b. a generator.