

**KING FAHD UNIVERSITY OF PETROLEUM & MINERALS  
ELECTRICAL ENGINEERING DEPARTMENT**

**EE 306 – Term 192**

**HW # 1: Three-Phase Circuits**

**Due Date: (Feb. 2<sup>nd</sup> for UT Classes and Feb. 3<sup>rd</sup> for MW Classes)**

**Problem # 1:**

Given the number  $A_1 = 5\angle 30^\circ$  (in polar form) and  $A_2 = -3 + j4$  (in rectangular form). Calculate the following, given the answers in both rectangular and polar forms:

- a.  $A_1 + A_2$
- b.  $A_1 * A_2$
- c.  $A_1 / (A_2)^*$

**Problem # 2:**

A load with an impedance of  $Z = 25\angle 53.1^\circ \Omega$  is fed from a single-phase source of 220V.

- a. Find the resistance and reactance of the load.
- b. Find the real (active) and imaginary (reactive) power of the load.
- c. Find the power factor of the load, and state whether it is lagging or leading.

**Problem # 3:**

Prove that the line voltage of a Y-connected generator with an *acb* phase sequence lags the corresponding phase voltage by  $30^\circ$ . Draw a phasor diagram showing the phase and line voltages for this generator.

**Problem # 4:**

A balanced 3-phase Y-connected load with phase impedance of  $20 + j15 \Omega$  is connected to a 400-V, 3-phase, 50-Hz supply. Calculate:

- a. the line current.
- b. the real and reactive power supplied.

If a 3-phase  $\Delta$ -connected capacitor bank is connected parallel to the above load, calculate the capacitance per phase to obtain a resultant power factor of 0.95 lagging.

**Problem # 5:**

A balanced 3-phase, 173-V, 60-Hz source supplies the two following loads:

- A  $\Delta$ -connected load with a phase impedance of  $(18 + j24) \Omega$ ,
- A Y-connected load with a phase impedance of  $10\angle 53.13^\circ \Omega$ .

Find:

- a. The power factor of the entire load.
- b. The total line current supplied.
- c. The total real, reactive, and apparent powers.