

KING FAHD UNIVERSITY OF PETROLEUM & MINERALS
ELECTRICAL ENGINEERING DEPARTMENT

EE 306 – Term 192

HW # 1: Three-Phase Circuits

Due Date: (Feb. 2nd for UT Classes and Feb. 3rd for MW Classes)

Key Solutions

Problem # 1:

Given the number $A_1 = 5\angle 30^\circ$ (in polar form) and $A_2 = -3 + j4$ (in rectangular form). Calculate the following, given the answers in both rectangular and polar forms:

- a. $A_1 + A_2$
- b. $A_1 * A_2$
- c. $A_1 / (A_2)^*$

Solution:

$$A_1 = 5 \angle 30^\circ = 4.33 + j2.50$$

$$A_2 = -3 + j4 = 5 \angle 126.9^\circ$$

$$\textcircled{a} A_1 + A_2 = 1.33 + j6.5 = 6.63 \angle 78.4^\circ$$

$$\textcircled{b} A_1 A_2 = 25 \angle 156.9^\circ = -23 + j9.8$$

$$\textcircled{c} A_1 / A_2^* = 1 \angle 156.9^\circ = -0.92 + j0.39$$

Problem # 2:

A load with an impedance of $Z = 25\angle 53.1^\circ \Omega$ is fed from a single-phase source of 220V.

- Find the resistance and reactance of the load.
- Find the real (active) and imaginary (reactive) power of the load.
- Find the power factor of the load, and state whether it is lagging or leading.

Solution:

$$\textcircled{a} \quad Z = 15 + j20$$

$$R = 15 \, \Omega$$

$$X = 20 \, \Omega$$

$$\textcircled{b} \quad I = \frac{V}{Z} = \frac{220 \angle 0^\circ}{25 \angle 53.1^\circ} = 8.8 \angle -53.1^\circ$$

$$\textcircled{c} \quad S = VI^* = (220 \angle 0^\circ)(8.8 \angle -53.1^\circ)^* = 1936 \angle 53.1^\circ = 1162 + j1549 \text{ VA}$$

$$P = 1162 \text{ W}$$

$$Q = 1549 \text{ VAR}$$

$$\textcircled{c} \quad \text{PF} = \cos 53.1^\circ = 0.6 \text{ lagging}$$

Problem # 3:

Prove that the line voltage of a Y-connected generator with an *acb* phase sequence lags the corresponding phase voltage by 30° . Draw a phasor diagram showing the phase and line voltages for this generator.

Solution:

If the generator has an *acb* phase sequence, then the three phase voltages will be

$$\mathbf{V}_{an} = V_\phi \angle 0^\circ$$

$$\mathbf{V}_{bn} = V_\phi \angle -240^\circ$$

$$\mathbf{V}_{cn} = V_\phi \angle -120^\circ$$

The relationship between line voltage and phase voltage is derived below. By Kirchhoff's voltage law, the line-to-line voltage \mathbf{V}_{ab} is given by

$$\mathbf{V}_{ab} = \mathbf{V}_a - \mathbf{V}_b$$


$$\mathbf{V}_{ab} = V_\phi \angle 0^\circ - V_\phi \angle -240^\circ$$

$$\mathbf{V}_{ab} = V_\phi - \left(-\frac{1}{2}V_\phi + j\frac{\sqrt{3}}{2}V_\phi \right) = \frac{3}{2}V_\phi - j\frac{\sqrt{3}}{2}V_\phi$$

$$\mathbf{V}_{ab} = \sqrt{3}V_\phi \left(\frac{\sqrt{3}}{2} - j\frac{1}{2} \right)$$

$$\mathbf{V}_{ab} = \sqrt{3}V_\phi \angle -30^\circ$$

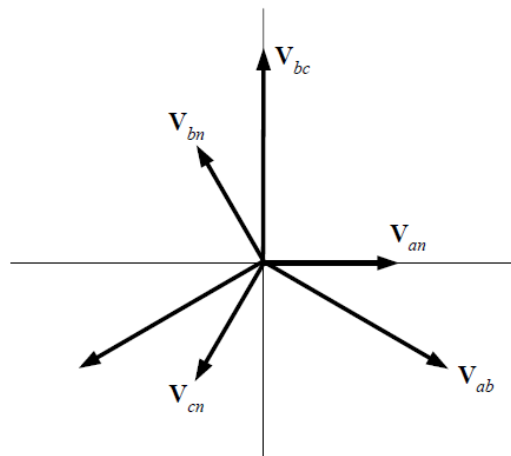Thus the line voltage *lags* the corresponding phase voltage by 30° . The phasor diagram for this connection is shown below.



Problem # 4:

A balanced 3-phase Y-connected load with phase impedance of $20+j15 \Omega$ is connected to a 400-V, 3-phase, 50-Hz supply. Calculate:

- a. the line current.
- b. the real and reactive power supplied.

If a 3-phase Δ -connected capacitor bank is connected parallel to the above load, calculate the capacitance per phase to obtain a resultant power factor of 0.95 lagging.

Solution:

$$Z_{ph} = 20 + j15 \Omega = 25 \angle 36.87^\circ$$

$$V_{ph} = \frac{400}{\sqrt{3}} \angle 0^\circ = 231 \angle 0^\circ$$

$$a) I_{ph} = I_L = \frac{V_{ph}}{Z_{ph}} = \frac{231 \angle 0^\circ}{25 \angle 36.87^\circ} = 9.24 \angle -36.87^\circ$$

$$b) P = \sqrt{3} * V_L I_L \cos 36.87^\circ = \sqrt{3} * 400 * 9.24 * 0.8 = 5120 \text{ W}$$

$$Q = \sqrt{3} V_L I_L \sin 36.87^\circ = \sqrt{3} * 400 * 9.24 * 0.6 = 3840 \text{ VAR}$$

When the capacitor bank is connected

$$P_{f_{new}} = 0.95 ; \phi_{new} = 18.19^\circ ; \tan \phi_{new} = 0.3286$$

real Power remains constant

$$Q_{new} = P \tan \phi_{new} = 1682 \text{ VAR}$$


$$Q_c = Q - Q_{new}$$

$$Q_c = 3840 - 1682 = 2158 \text{ VAR}$$

$$Q_{cph} = \frac{2158}{3} = 719.3 \text{ VAR}$$

$$Q_{cph} = \frac{V_L^2}{X_c} \rightarrow X_c = \frac{V_L^2}{Q_{cph}} = \frac{(400)^2}{719.3} = 222.44 \Omega = \frac{1}{\omega C}$$
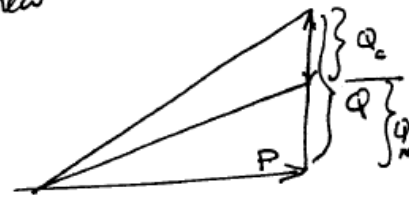
$$C = \frac{1}{2\pi * 50 * 222.44} = 14.31 \mu\text{F}$$



Problem # 5:

A balanced 3-phase, 173-V, 60-Hz source supplies the two following loads:

- A Δ -connected load with a phase impedance of $(18+j24) \Omega$,
- A Y-connected load with a phase impedance of $10\angle 53.13^\circ \Omega$.

Find:

- a. The power factor of the entire load.
- b. The total line current supplied.
- c. The total real, reactive, and apparent powers.

Solution:

- Convert Δ to Y $Z_y = \frac{18 + j24}{3} = 6 + j8$
- Parallel combination of the 2 loads (per phase)

$$Z_T = \frac{(6 + j8)(10\angle 53.1^\circ)}{6 + j8 + 10\angle 53.1^\circ} = 5\angle 53.1^\circ$$

a. Power factor = $\cos(53.1^\circ) = 0.6$ lag

b. $I_L = I_{ph} = \frac{173/\sqrt{3}\angle 0^\circ}{5\angle 53.1^\circ} = 20\angle -53.1^\circ \text{ A}$

c.

$$P_T = \sqrt{3} \times 173 \times 20 \times 0.6 = 3.596 \text{ kW}$$

$$Q_T = \sqrt{3} \times 173 \times 20 \times 0.8 = 4.794 \text{ kVAR}$$

$$|S_T| = \sqrt{3} \times 173 \times 20 = 5.993 \text{ kVA} \quad \text{P}$$